
 
 
 


1. a) Design a minimal NAND/NAND circuit with three inputs S, A, B and one output F that has the following function table.

S	F
0	$A \text{ AND } B$
1	$A \text{ OR } B$

- b) Implement F in part (a) with a minimal NOR/NOR circuit

SOLUTION :


 


2. The following process is part of the architecture of an entity with inputs X, Y, Z and outputs S and R . Plot the waveforms of S and R corresponding to given X, Y and Z . Indicate the time instants at which an event is scheduled together with the scheduled event.


```

process (X, Y)
begin
    S  $\leftarrow$  X or Y;
    R  $\leftarrow$  S and Z;
end process;

```

  


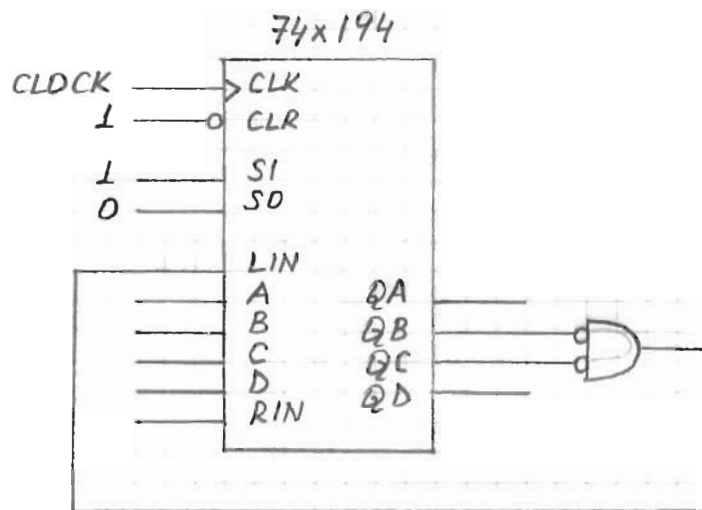
3. Draw the state diagram of the following sequential circuit whose states are coded as $Q_A Q_B Q_C Q_D$. The function table of the shift register 74x194 is as given.




SI	SD	Q_A^*	Q_B^*	Q_C^*	Q_D^*
0	0	Q_A	Q_B	Q_C	Q_D
0	1	RIN	Q_A	Q_B	Q_C
1	0	Q_B	Q_C	Q_D	LIN
1	1	A	B	C	D

SOLUTION :

 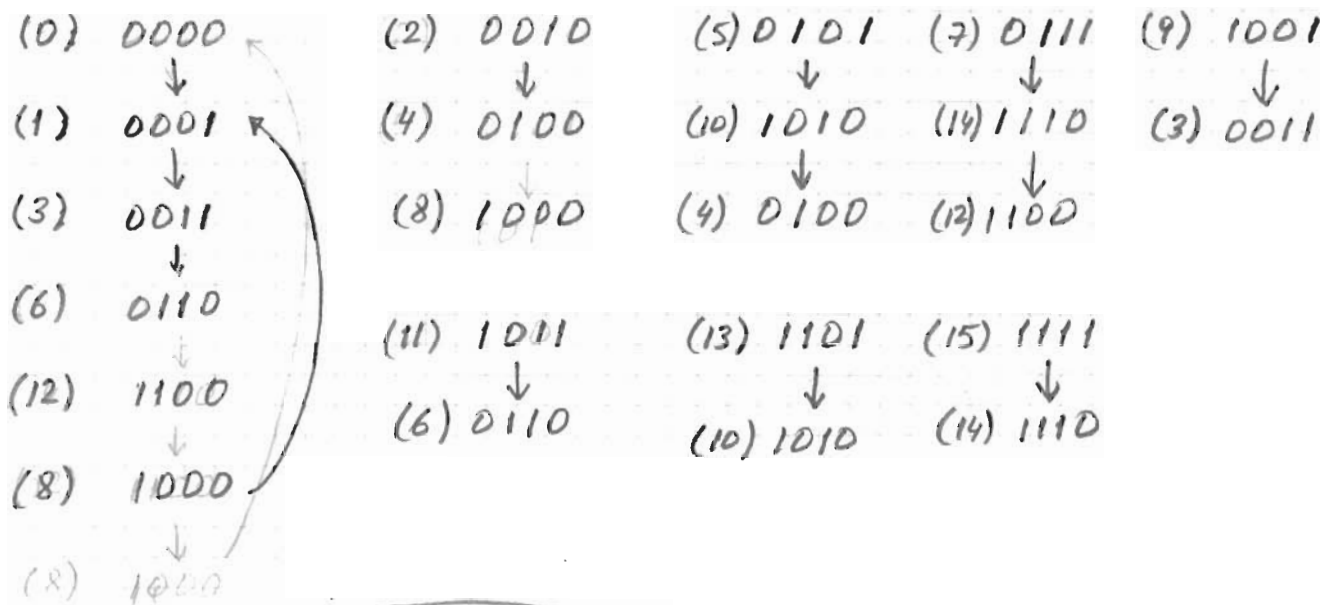Wired as left-shift register with $LIN = (Q_B + Q_C)'$



 4. a) Design a 2-bit counter that has the following state diagram. Use D flip flops.



- b) Use the counter in part (a) and a generic 4-to-1 multiplexer (but nothing else) to construct a Mealey machine with four inputs A, B, C, D and one output Y such that Y is A at the first tick of the clock, B at the next tick, C at the third tick, D at the fourth tick, A again at the fifth and so on.


SOLUTION :

a)

Q_B	Q_A	Q_B^*	Q_A^*
0	0	0	1
0	1	1	1
1	0	0	0
1	1	1	0

$$D_B = Q_A$$

$$D_A = Q_B'$$

 

b)

