


**EEE 102**  
**INTRODUCTION TO DIGITAL CIRCUIT DESIGN**  
**RECITATION PROBLEM SET 5**

ARASH ASHRAFNEJAD

1. JK-FLIPFLOP REVIEW

**Problem:** Verify the behavior of JK-flipflop discussed in class by filling out the tables below. Make comment on each case in terms of whether there is a state change, if so, whether it is a set ( $Q=1$ ) or reset ( $Q=0$ ).

Clock	J	K	$Q_t$	$\overline{Q}_t$	$\overline{set}$	$\overline{reset}$	$Q_{t+1}$	$\overline{Q}_{t+1}$	comment
0	x	x	x	x					
1	0	0	x	x					
1	0	1	0	1					
1	0	1	1	0					
1	1	0	0	1					
1	1	0	1	0					
1	1	1	0	1					
1	1	1	1	0					

 

Here  $\overline{set}$  and  $\overline{reset}$  are the outputs of the two NAND gates on the left with input J and K, respectively.

**Solution:**

Clock	J	K	$Q_t$	$\overline{Q}_t$	$\overline{set}$	$\overline{reset}$	$Q_{t+1}$	$\overline{Q}_{t+1}$	
0	x	x	x	x	1	1	$Q$	$\overline{Q}$	(no change)
1	0	0	x	x	1	1	$Q$	$\overline{Q}$	(no change)
1	0	1	0	1	1	1	0	1	(no change)
1	0	1	1	0	1	0	0	1	(reset)
1	1	0	0	1	0	1	1	0	(set)
1	1	0	1	0	1	1	1	0	(no change)
1	1	1	0	1	0	1	1	0	(set)
1	1	1	1	0	1	0	0	1	(reset)

□

2. CONVERT FLIP-FLOPS

**Problem:**

- (1) Convert a given D-flipflop to a JK-flipflop with minimal additional logic gates.
- (2) Convert a T Flip-Flop to a JK Flip-Flop.
- (3) Convert a RS Flip-Flop to a T Flip-Flop.
- (4) Build a JK-flipflop using a D-flipflop (of master-slave type) and a 4x1 MUX. No additional gates are allowed.

**Solution:**

(1)

$$D = Q'J + K'Q$$

(2)

$$T = Q'J + QK$$

$Q_t$	$Q_{t+1}$	J	K	T
0	0	0	x	0
0	1	1	x	1
1	0	x	1	1
1	1	x	0	0

(3)

$$S = Q'T, \quad R = QT$$

$Q_t$	$Q_{t+1}$	T	S	R
0	0	0	0	x
0	1	1	1	0
1	0	1	0	1
1	1	0	x	0

(4) use Q, 0, 1 and Q' as the 4 inputs and J,K as the selections of MUX.


□

### 3. EVEN PARITY CHECKER

**Problem:** An *even parity checker* is a sequential logic circuit that counts the number of 1's in a bit serial input stream and outputs 1 whenever this number is even (including 0). For example, if the input stream is 0110100101..., the corresponding output stream is 1011000110.... Implement such an even parity checker as a finite state machine using (1) RS-FFs, (2) JK-FF's, (3) D-FFs, and (4) T-FF's. Draw the logic diagram for each of the implementations. Which one requires minimum combinational logic?

**Solution:**

The state diagram:

 


The state table:

Present State (PS)	Input I	Next State (NS)	S	R	J	K	D	T
even 1	0	even 1	0	x	0	x	0	0
even 1	1	odd 0	1	0	1	x	1	1
odd 0	0	odd 0	x	0	x	0	1	0
odd 0	1	even 1	0	1	x	1	0	1

The next state decoder:

 - **D-FF:**  $D = PS' I + PS I' = PS \oplus I$
- **RS-FF:**  $S = PS' I, \quad R = PS I$
- **JK-FF:**  $J = K = I$
- **T-FF:**  $T = I$



□

#### 4. FSM COMBINATIONAL LOCK

**Problem:** Design a digital combination lock which will set the output signal “unlock” to 1 only after receiving a key, a specific serial binary pattern 101. (Of course for the lock to be practically useful, the binary pattern need to be much longer).

**Hint:** This lock can be designed as a finite state machines with one input (which receives a bit in the binary sequence at a time) and one output (which is 1 only if the pattern 101 is detected). A sample input sequence and the corresponding output sequence of this FSM are shown below.

Input	0	1	0	0	1	0	1	0	0	1	1	0	1	1
Output	0	0	0	0	0	0	1	0	0	0	0	0	1	0
State	A						A						A	

This FSM has the following 4 states:

- state A (00): the initial state of the FSM and it should always be in this state when more than one 0 in a sequence is received (impossible to be part of the key).
- state B (01): the FSM should be in this state whenever a 1 is detected as it could be the first 1 of the key.
- state C (10): when the partial pattern 10 is detected;
- state D (11): when the complete pattern 101 is detected, then the FSM is reset so that the next state is the initial state A (independent of the input).

Design this single-input, single-output, 4-state FSM using D-FF's in the following steps:

- (1) Fill out the 3rd row of the table above to show the state transition corresponding to the current input;
- (2) Draw the state diagram;
- (3) Complete the state transition table below;
- (4) Implement the next state decoder and the output decoder. (Hint: this could be designed as a Moore machine and no output decoder is needed.)

The state transition table:

	Present State $Q_1 Q_0$	Input	Next State $Q_1 Q_0$	Output
A	0 0	0		
	0 0	1		
B	0 1	0		
	0 1	1		
C	1 0	0		
	1 0	1		
D	1 1	0		
	1 1	1		

**Solution:**

Input	0	1	0	0	1	0	1	0	0	1	1	0	1	1
Output	0	0	0	0	0	0	1	0	0	0	0	0	1	0
State (key)	A	A	B	C	A	B	C	D	A	A	B	B	C	A

$$D_1 = Q'_1 Q_0 I' + Q_1 Q'_0 I, \quad D_0 = I(Q'_1 + Q'_0), \quad \text{Output1} = Q_1 Q'_0 I, \quad \text{Output2} = Q_1 Q_0,$$

	Present State		Input		Next State		Output
	$Q_1$	$Q_0$		$Q_1$	$Q_0$		
A	0	0	0	A	0	0	0
	0	0	1	B	0	1	0
B	0	1	0	C	1	0	0
	0	1	1	B	0	1	0
C	1	0	0	A	0	0	0
	1	0	1	D	1	1	0 (1)
D	1	1	0	A	0	0	1 (0)
	1	1	1	A	0	0	1 (0)

□

## 5. MODULO 4 UP-DOWN COUNTER

**Problem:** Design a modulo 4 non-ripple up-down counter as a finite state machine. The counter counts down when input  $I = 0$ , and it counts up when  $I = 1$ . Use four T-type flipflops to encode the four states of the FSM (“one-hot” encoding).

- (1) Fill out the state table below for the next state and the signals needed to trigger the T-FFs.

	Present state				Input	Next state				signals needed			
	$Q_3$	$Q_2$	$Q_1$	$Q_0$	I	$Q'_3$	$Q'_2$	$Q'_1$	$Q'_0$	$T_3$	$T_2$	$T_1$	$T_0$
0	0	0	0	1	0								
0	0	0	0	1	1								
1	0	0	1	0	0								
1	0	0	1	0	1								
2	0	1	0	0	0								
2	0	1	0	0	1								
3	1	0	0	0	0								
3	1	0	0	0	1								

- (2) Give the logic expression for each of the four signals  $T_i$  ( $i = 0, 1, 2, 3$ )  
 (3) Draw the complete diagram of the FSM in terms of the four FFs and additional logic gates needed for the next state decoder.

**Solution:**

	Present state				Input	Next state				signals needed			
	$Q_3$	$Q_2$	$Q_1$	$Q_0$	I	$Q'_3$	$Q'_2$	$Q'_1$	$Q'_0$	$T_3$	$T_2$	$T_1$	$T_0$
0	0	0	0	1	0	1	0	0	0	1	0	0	1
0	0	0	0	1	1	0	0	1	0	0	0	1	1
1	0	0	1	0	0	0	0	0	1	0	0	1	1
1	0	0	1	0	1	0	1	0	0	0	1	1	0
2	0	1	0	0	0	0	0	1	0	0	1	1	0
2	0	1	0	0	1	1	0	0	0	1	1	0	0
3	1	0	0	0	0	0	1	0	0	1	1	0	0
3	1	0	0	0	1	0	0	0	1	1	0	0	1

$$T_3 = Q_0I' + Q_2I + Q_3, \quad T_2 = Q_1I + Q_2 + Q_3I', \quad T_1 = Q_0I + Q_1 + Q_2I', \quad T_0 = Q_0 + Q_1I' + Q_3I,$$

□