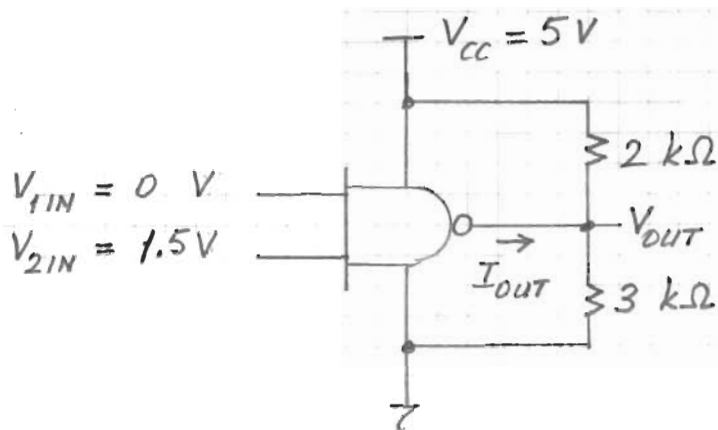


1. Find V_{OUT} and I_{OUT} in the following circuit. The internal resistances of the transistors associated with each input are as given.





INTERNAL RESISTANCES

$$R_{1DN} = 200\ \Omega \quad R_{1OFF} = 1\ \text{M}\Omega$$

$$R_{2DN} = 400\ \Omega \quad R_{2OFF} = 5\ \text{k}\Omega$$

SOLUTION



Equivalent circuit :

  

$$V_{OUT} = \frac{3}{3 + \frac{1}{8}} \times 5 = 4.8\ \text{V}$$

$$I_{OUT} = \frac{5 - 4.8}{\frac{2}{15}} = 1.5\ \text{mA}$$

 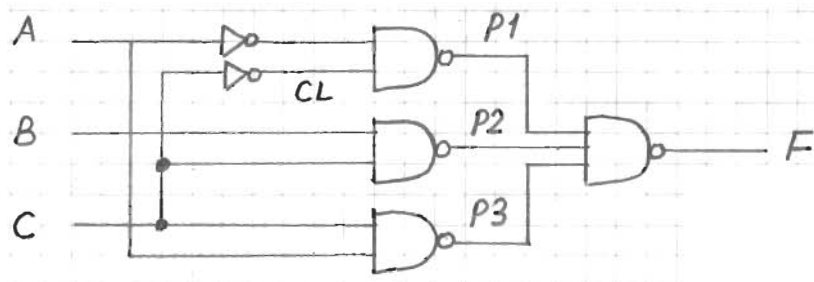2. In the following circuit inverters have a 5 nsec propagation delay and the NAND gates 10 nsec. Plot the output waveform if $A=0$, $B=1$ and C changes from 1 to 0 at $t=0$.




3. Obtain a minimal S.O.P representation (F_1) and a minimal P.O.S. representation (F_2) of


$$F(A,B,C) = \sum m(0,2,3) + \sum d(6,7)$$

Are F_1 and F_2 equal? Explain.

SOLUTION

 

$$F_1 = B + A'C'$$

 


$$F_2 = A'(B+C')$$

$$A=B=1 \Rightarrow F_1=1, F_2=0 \Rightarrow F_1 \neq F_2$$

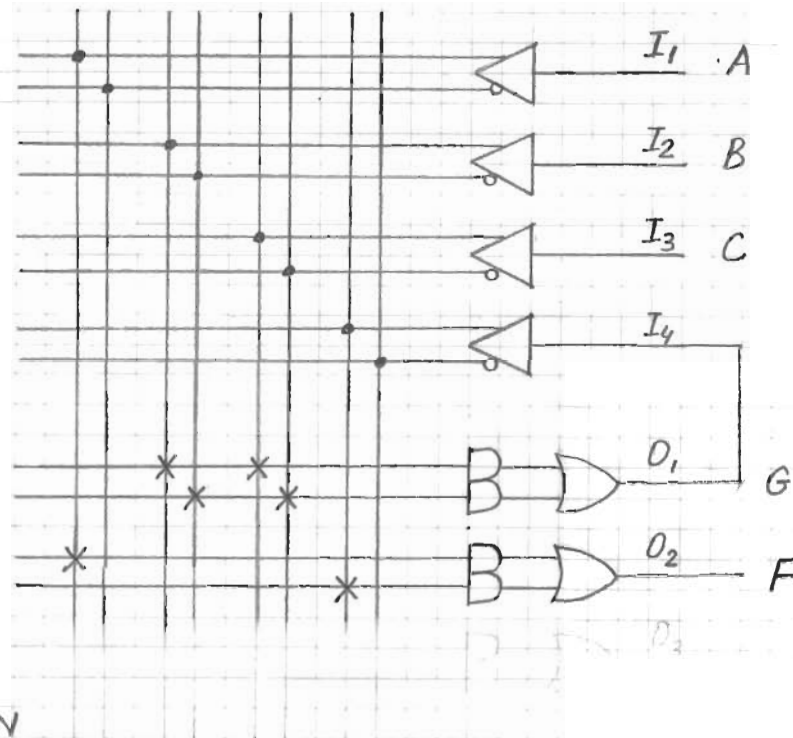
4. Implement $F = A + BC + B'C'$

- using a two-level NAND/NAND circuit plus inverters
- using the following PAL



SOLUTION

a)

 

b) $F = A + G$, $G = BC + B'C'$

Implementation above.

5. Draw the block diagram and write down the truth table of the circuit implemented by the following VHDL code.

```

library IEEE;
use IEEE.std_logic.1164.all;

entity BDX is
    port ( G: in STD_LOGIC;
          X: in STD_LOGIC_VECTOR (1 downto 0);
          Y: out STD_LOGIC_VECTOR (0 to 3));
end BDX;


```

```

architecture ABDX of entity BDX is
    signal Z: STD_LOGIC_VECTOR (0 to 3);
begin
    with X select
        Z <= "1000" when "00",
             "0100" when "01",
             "0010" when "10",
             "0001" when "11",
             "0000" when others;
    Y <= Z when G = '1' else "0000";
end ABDX;

```

SOLUTION

 

G	X(1)	X(0)	Y(0)	Y(1)	Y(2)	Y(3)
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1