

# Latches

VOLKAN KURSUN

*Some material from McGraw Hill*

## Outline

- Storage Elements
- Basic Latch
- Gated SR Latch
- Gated D Latch

## Storage Elements

- ❑ In combinational circuits, the value of each output depends solely on the present values of signals applied to the inputs
- ❑ In sequential circuits, the values of outputs depend not only on the present values of the inputs but also on the **past behavior** of the circuit (past inputs and outputs)
- ❑ Sequential circuits include **storage elements** that store the values of logic signals: the contents of storage elements represent the state of the circuit

## Sequence of States


- ❑ When the inputs change values, the new inputs either leave the circuit in the same state or cause the circuit to change to a new state
- ❑ Over time, a circuit with storage elements moves through a **sequence of states** in response to the changes in the inputs: **sequential circuits (state machines)**

## Outline

- Storage Elements
- Basic Latch**
- Gated SR Latch
- Gated D Latch

 
## Simple Memory Element

- Consists of a loop with two inverters (cross-coupled inverter pair)
- Circuit will maintain its state as long as the power supply is applied
- The circuit has two states ( $AB = 0b01$  or  $AB = 0b10$ )
- The simple memory element does NOT provide the means to control these two states: circuit needs to be expanded to provide the capability to change state


 
## Basic Latch


- A memory element built with two NOR gates: inputs Set and Reset provide the means to change state



R	S	R	Q <sub>a</sub>	Q <sub>b</sub>
0	0	0	0/1	1/0
0	1	0	0	1
1	0	1	1	0
1	1	1	0	0
 
## Basic Latch

- When Set and Reset are both 0, the latch maintains its state




R	S	R	Q <sub>a</sub>	Q <sub>b</sub>
0	0	0	0/1	1/0
0	1	0	0	1
1	0	1	1	0
1	1	1	0	0

(no change of state)
 
# Basic Latch

- When Set = 0 and Reset = 1, the latch is reset ( $Q_a = 0$ )




R	S	R	$Q_a$	$Q_b$
0	0	0/1	1/0	
0	1	0	1	Reset
1	0	1	0	
1	1	0	0	

A more common way to draw the basic latch  
EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN
 
# Basic Latch

- When Set = 1 and Reset = 0, the latch is set ( $Q_a = 1$ )




R	S	R	$Q_a$	$Q_b$
0	0	0/1	1/0	
0	1	0	1	
1	0	1	0	Set
1	1	0	0	

A more common way to draw the basic latch  
EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN
 
# Basic Latch

- When Set and Reset are both 1, both outputs are zero:  $Q_a = Q_b = 0$




R	S	R	$Q_a$	$Q_b$
0	0	0/1	1/0	
0	1	0	1	
1	0	1	0	
1	1	0	0	Both outputs are 0

A more common way to draw the basic latch  
EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN
 
# Basic Latch Oscillation and Uncertainty

- After Set and Reset are both 1 and both outputs are zero:  $Q_a = Q_b = 0$ , what if both Set and Reset transition to 0 at the same time?




R	S	R	$Q_a$	$Q_b$
0	0	0/1	1/0	
0	1	0	1	
1	0	1	0	
1	1	0	0	

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

- VOLKAN KURSUN Bilkent University
- ## Basic Latch Oscillation and Uncertainty
- Qa and Qb oscillate between  $Q_a = Q_b = 1$  and  $Q_a = Q_b = 0$
  - If the delays through the two NOR gates are identical, the oscillation will continue indefinitely
  - In a real circuit, the delays of the two NOR gates will be different and the latch will eventually settle down to one of its two stable states: however, the final state would be unknown (uncertain)

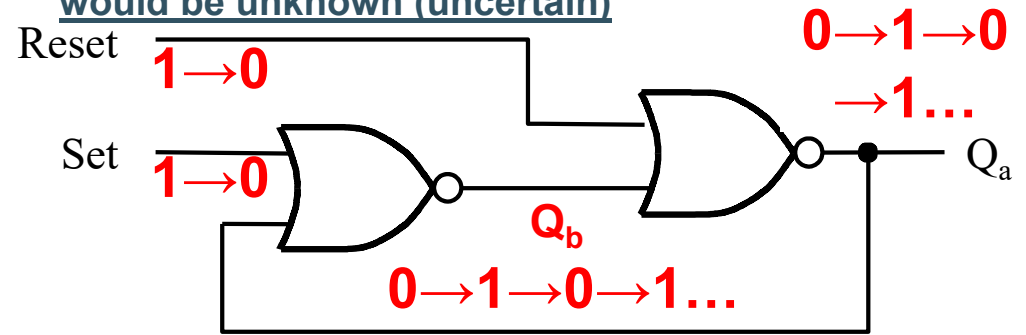

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN



Bilkent University

## Outline

- Storage Elements
- Basic Latch
- Gated SR Latch
- Gated D Latch

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

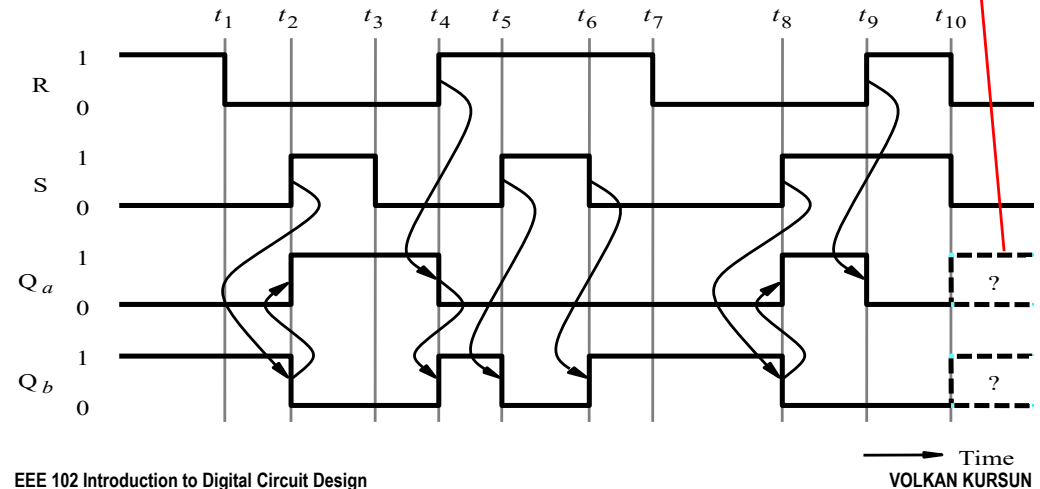 


EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

Bilkent University

 
## Gated SR Latch

- In the basic SR latch, the state changes occur anytime that the set and reset inputs change
- Add an **enable signal** that would allow **controlling when** the latch would respond to the changes in its set and reset inputs: **when disabled, the changes in the set and reset signals would be ignored** by the latch and the existing state would be maintained



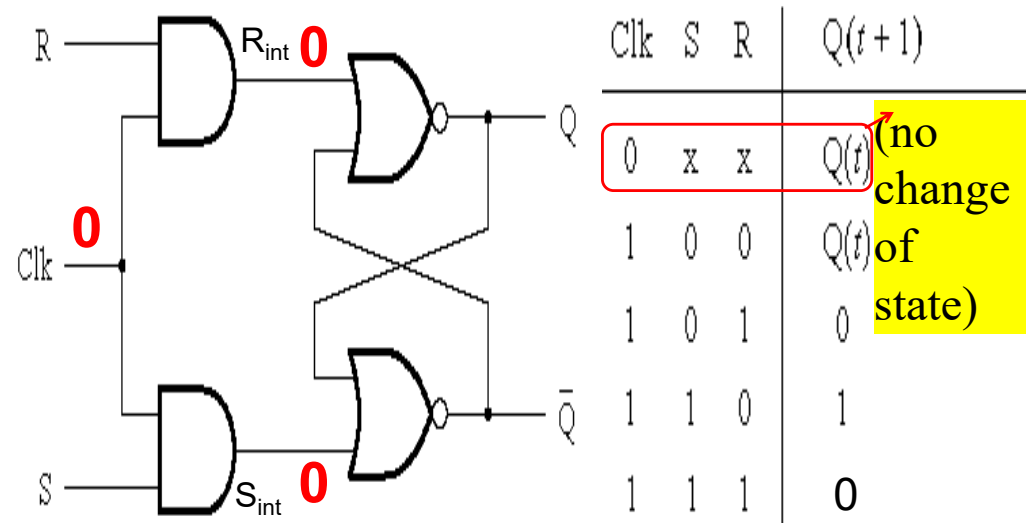
# Gated SR Latch

- When **clk = 0**, the latch is disabled: the changes in the **set and reset signals** would be **ignored** by the latch and the **existing state** would be **maintained**



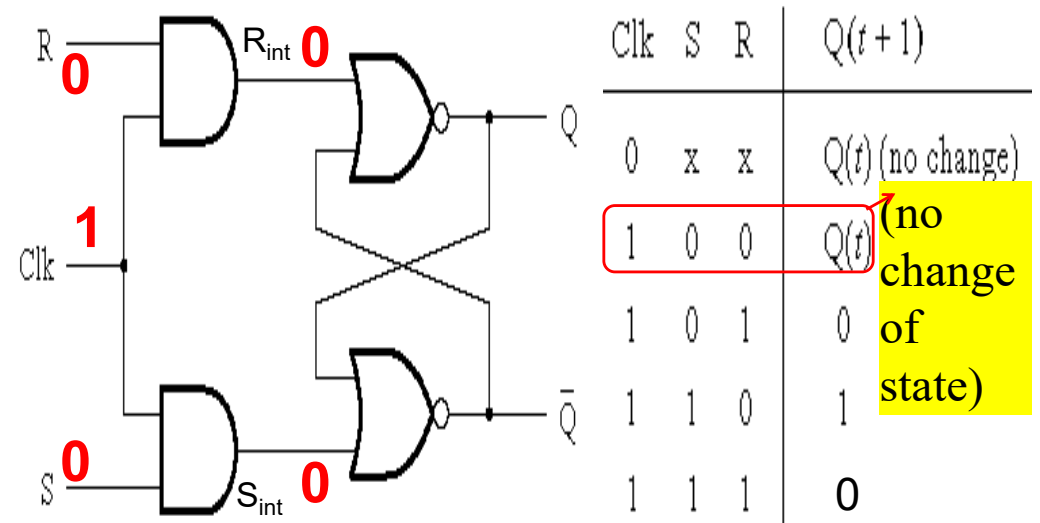
# Gated SR Latch: Level-Sensitive

- When **clk = 1**, the latch is enabled:  $R_{int} = R$  and  $S_{int} = S$  and the latch behaves like the basic SR latch
- If **S = R = 0**, the latch **maintains** its **state**



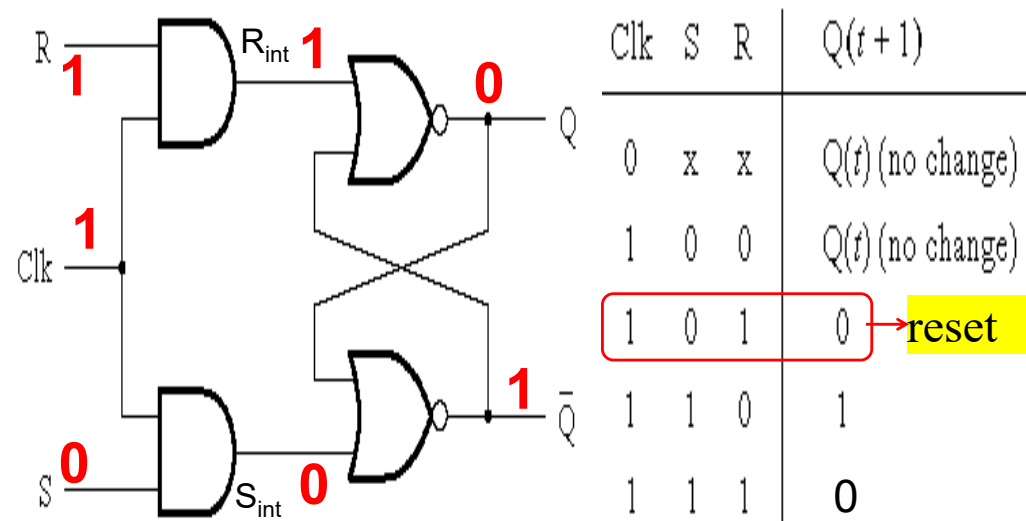
# Gated SR Latch: Level-Sensitive

- When **clk = 1**, the latch is enabled:  $R_{int} = R$  and  $S_{int} = S$  and the latch behaves like the basic SR latch
- If **S = 0** and **R = 1**, the latch is **reset**



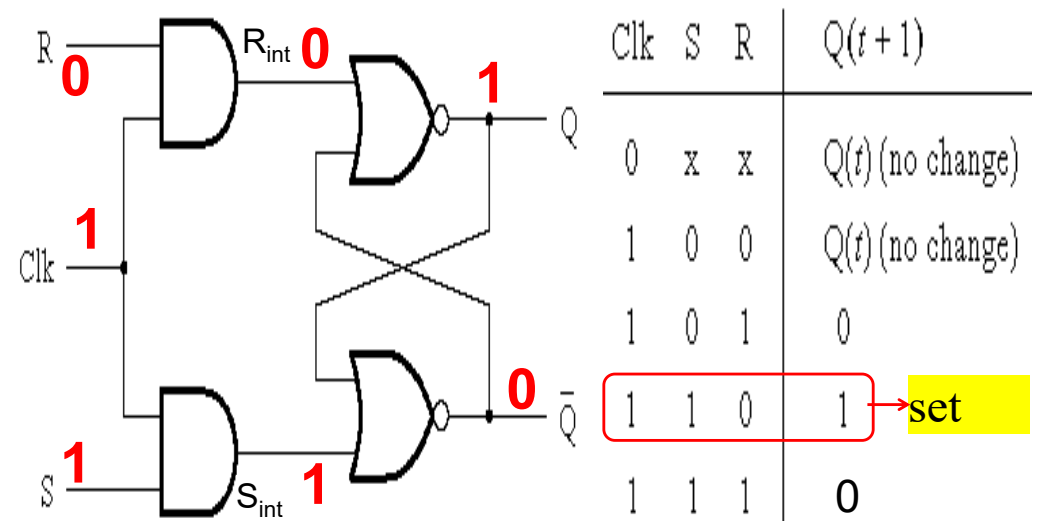
# Gated SR Latch: Level-Sensitive

- When **clk = 1**, the latch is enabled:  $R_{int} = R$  and  $S_{int} = S$  and the latch behaves like the basic SR latch
- If **S = 1** and **R = 0**, the latch is **set**



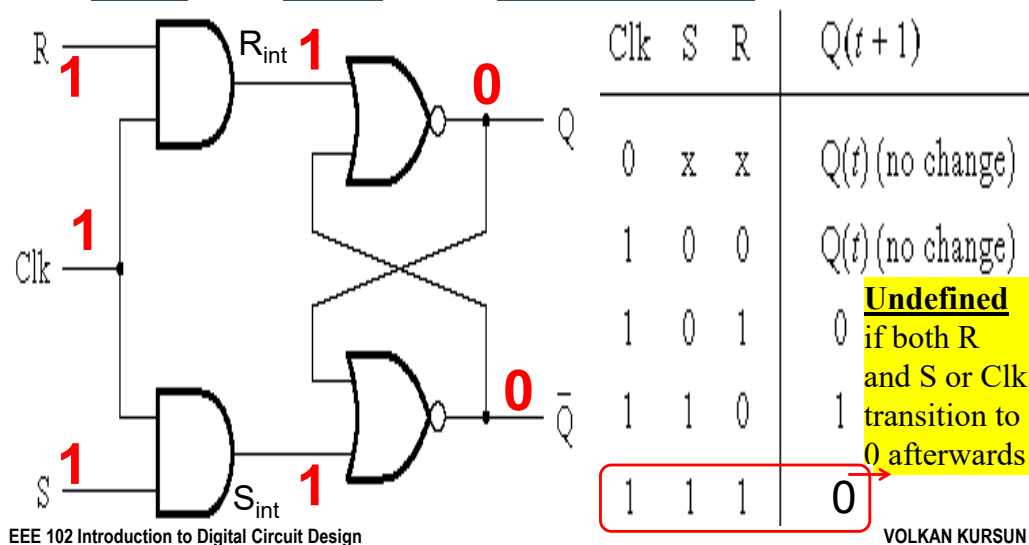
## Gated SR Latch: Level-Sensitive

- When  $\text{clk} = 1$ , the latch is enabled:  $R_{\text{int}} = R$  and  $S_{\text{int}} = S$  and the latch behaves like the basic SR latch
- If  $S = 1$  and  $R = 1$ , both **outputs are 0**



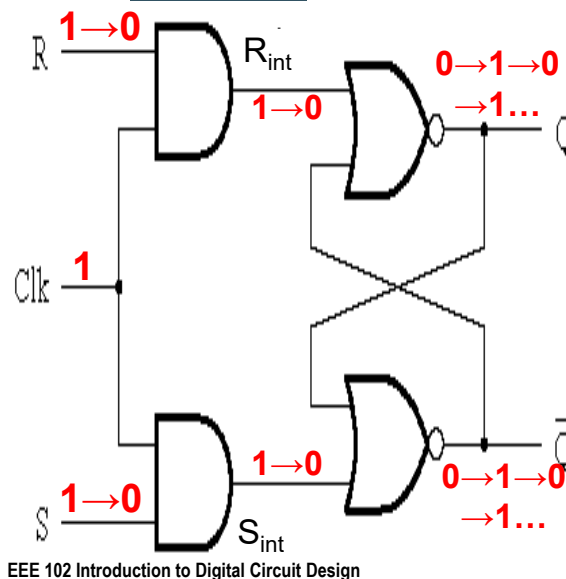
## SR Latch Oscillation

- If  $S = R = 1, Q = Q' = 0$ . If S and R transition from 1 to 0 at the same time, Q and Q' oscillate between  $Q = Q' = 0$  and  $Q = Q' = 1$



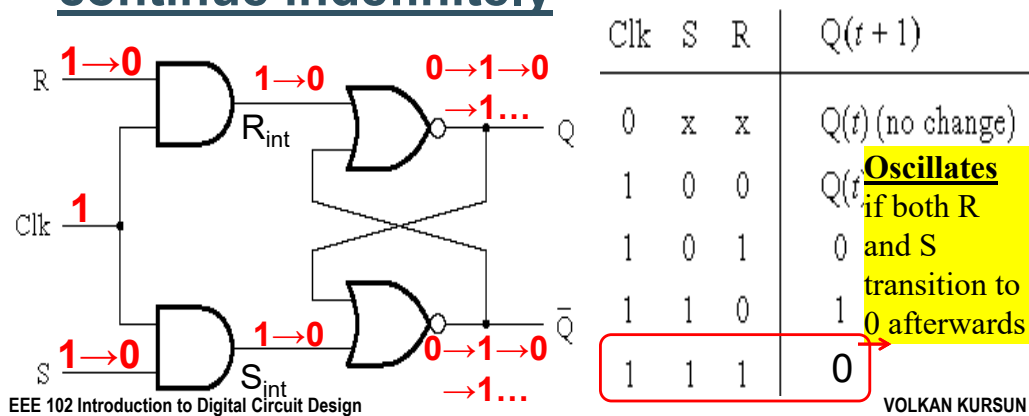
## SR Latch Oscillation

- Q and Q' oscillate between  $Q = Q' = 1$  and  $Q = Q' = 0$
- If the delays through the two NOR gates are identical, the **oscillation will continue indefinitely**



 
## SR Latch Oscillation

- Similarly, if Clk transitions from 1 to 0 while  $S = R = 1$ , Q and Q' oscillate between  $Q = Q' = 0$  and  $Q = Q' = 1$



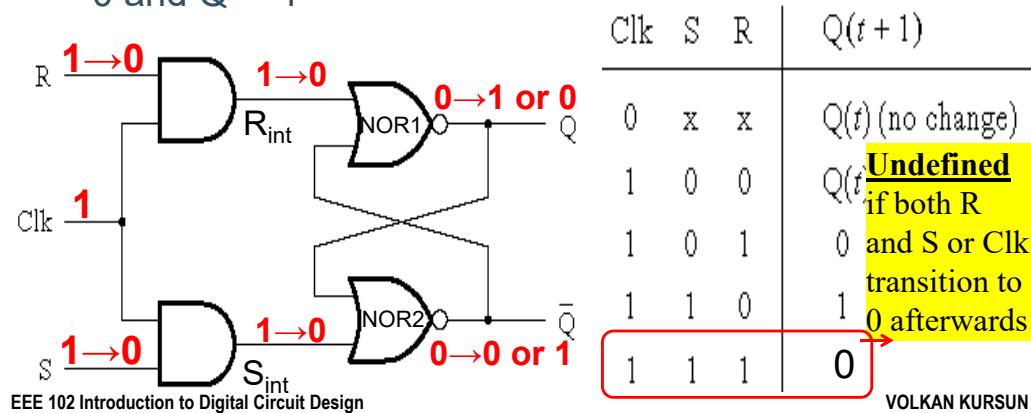
# SR Latch Uncertainty

- In a real circuit, the delays of the two NOR gates will be different and the latch will eventually settle down to one of its two stable states: **however, the final state would be unknown (uncertain)**
- If  $\text{Delay}_{\text{NOR1}} < \text{Delay}_{\text{NOR2}}$ : will stabilize to  $Q = 1$  and  $Q' = 0$
- Alternatively, if  $\text{Delay}_{\text{NOR2}} < \text{Delay}_{\text{NOR1}}$ : will stabilize to  $Q = 0$  and  $Q' = 1$




# SR Latch Timing Diagram

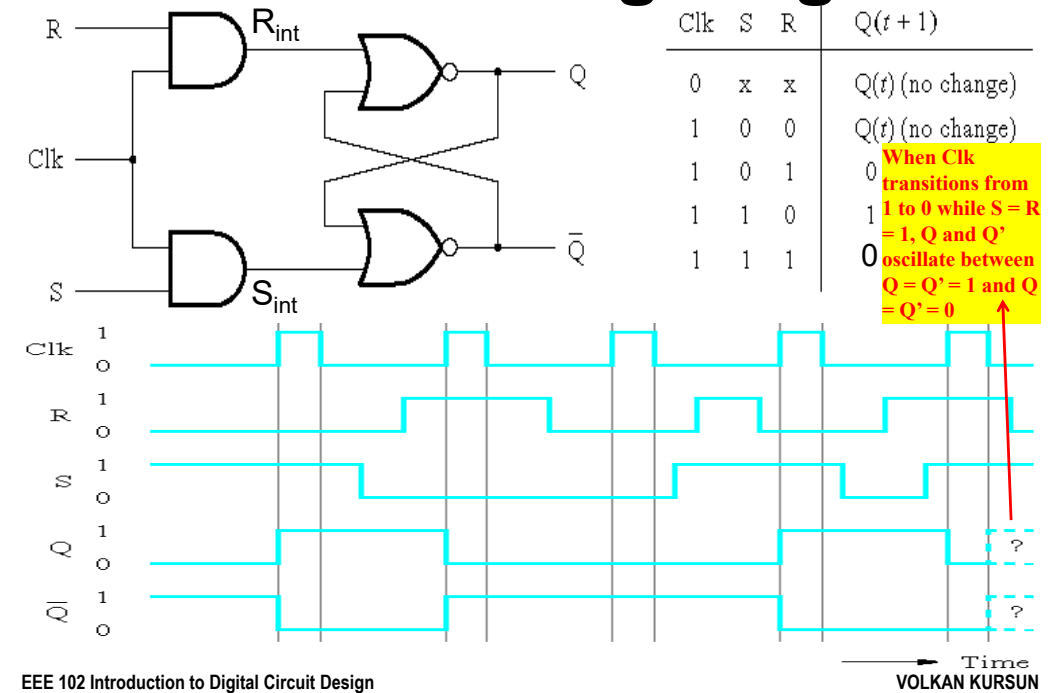

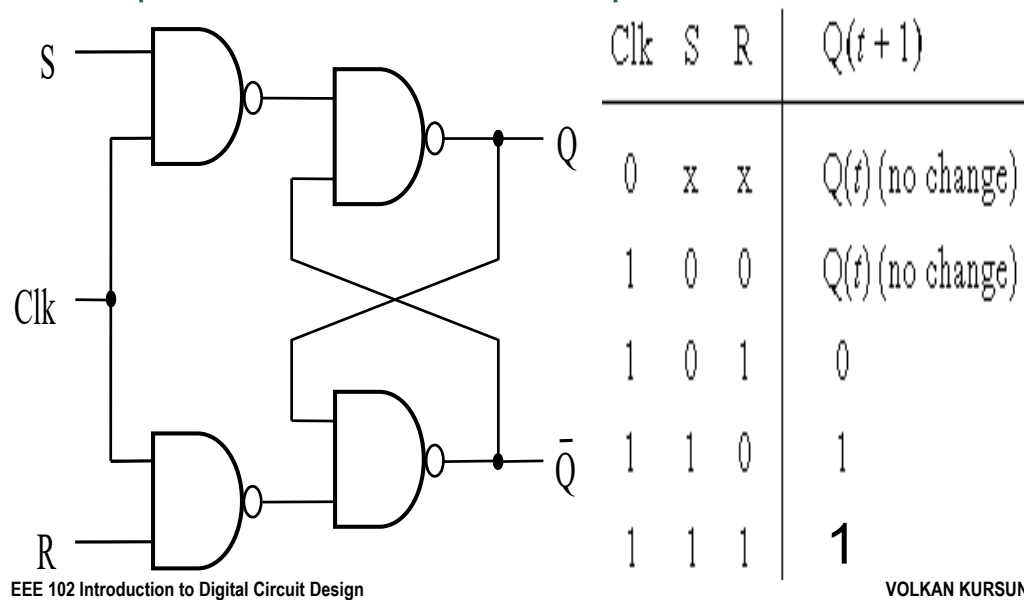
# Gated SR Latch with NAND

- S and R assignments have been reversed as compared to the AND-NOR implementation



# Gated SR Latch with NAND


- $\text{Clk} = 0$ : **maintains state**

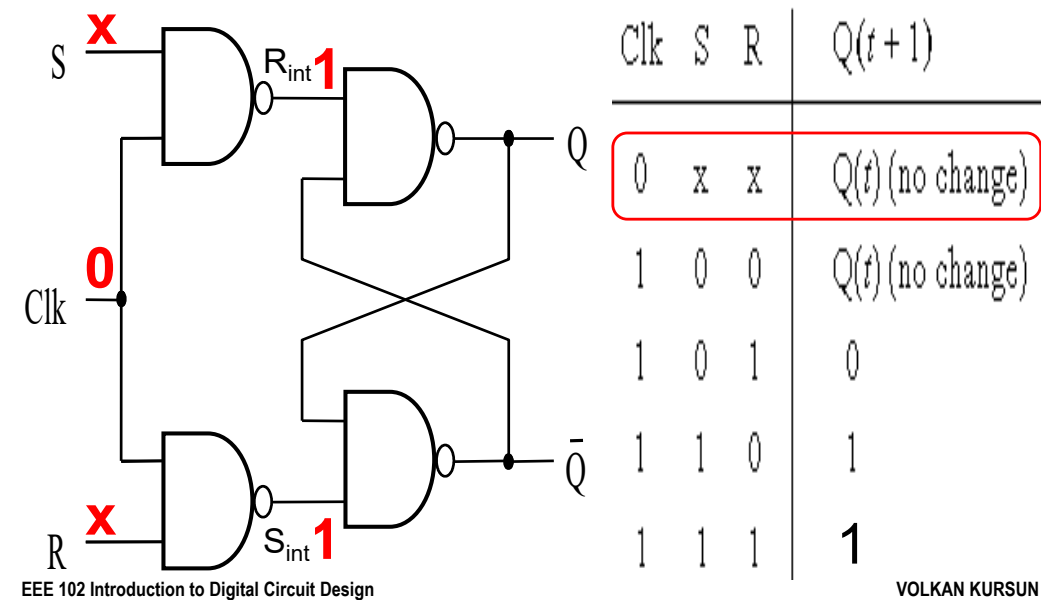



# Gated SR Latch with NAND


□ Clk = 1, S = 0, R = 0: maintains state

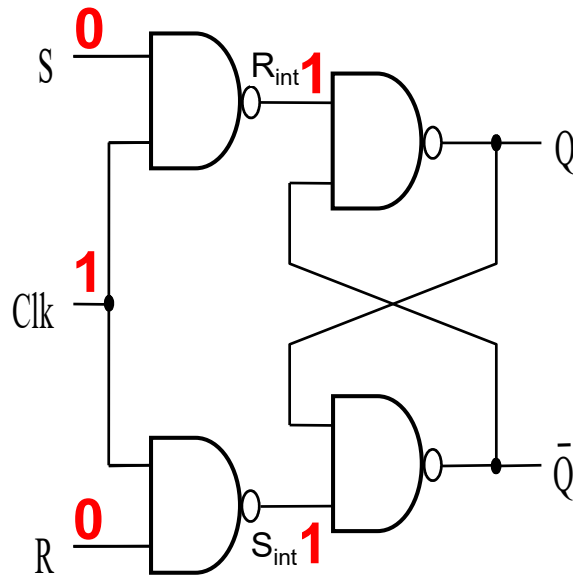

Clk	S	R	Q(t+1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	1

# Gated SR Latch with NAND


□ Clk = 1, S = 0, R = 1: reset the latch

 

Clk	S	R	Q(t+1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	1

# Gated SR Latch with NAND


□ Clk = 1, S = 1, R = 0: set the latch

 

Clk	S	R	Q(t+1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	1

# Gated SR Latch with NAND

□ Clk = 1, S = 1, R = 1: **Q = Q' = 1**

 

Clk	S	R	Q(t+1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	1

**Undefined**  
if both R  
and S or Clk  
transition to  
0 afterwards




VOLKAN KURSUN Bilkent University
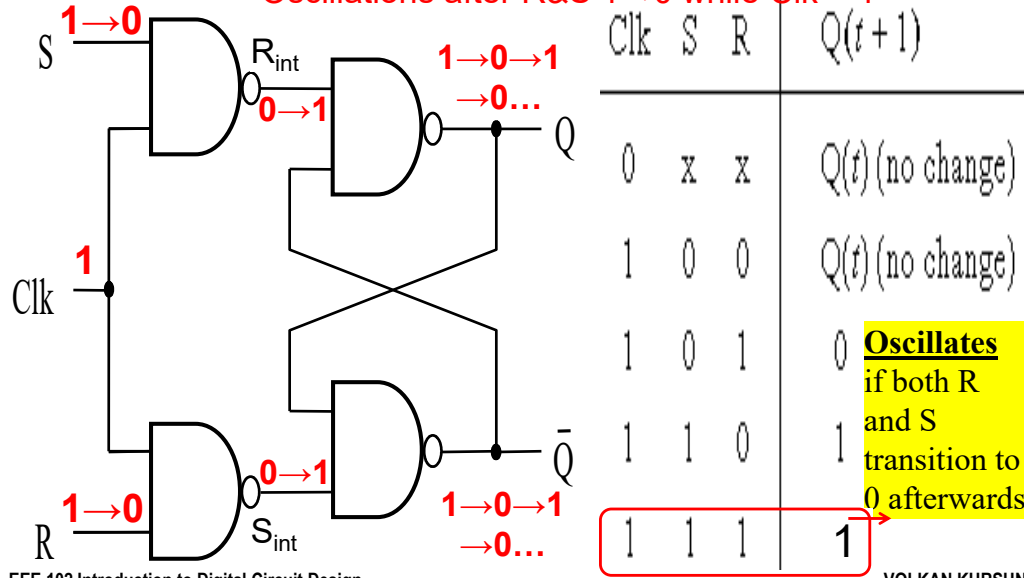
# NAND SR Latch Oscillations

- If S and R transition from 1 to 0 at the same time, Q and Q' oscillate between  $Q = Q' = 1$  and  $Q = Q' = 0$

Oscillations after R&S  $1 \rightarrow 0$  while Clk = 1



EEE 102 Introduction to Digital Circuit Design


VOLKAN KURSUN

VOLKAN KURSUN Bilkent University
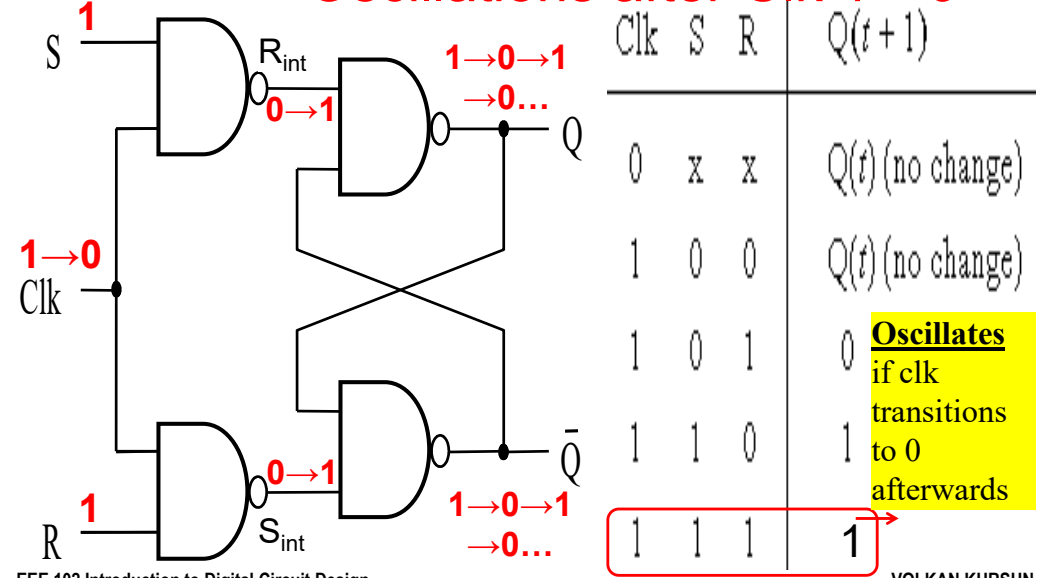
# NAND SR Latch Oscillations

- Similarly, if Clk transitions from 1 to 0 while  $S = R = 1$ , Q and Q' oscillate between  $Q = Q' = 1$  and  $Q = Q' = 0$

Oscillations after Clk  $1 \rightarrow 0$




EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN Bilkent University
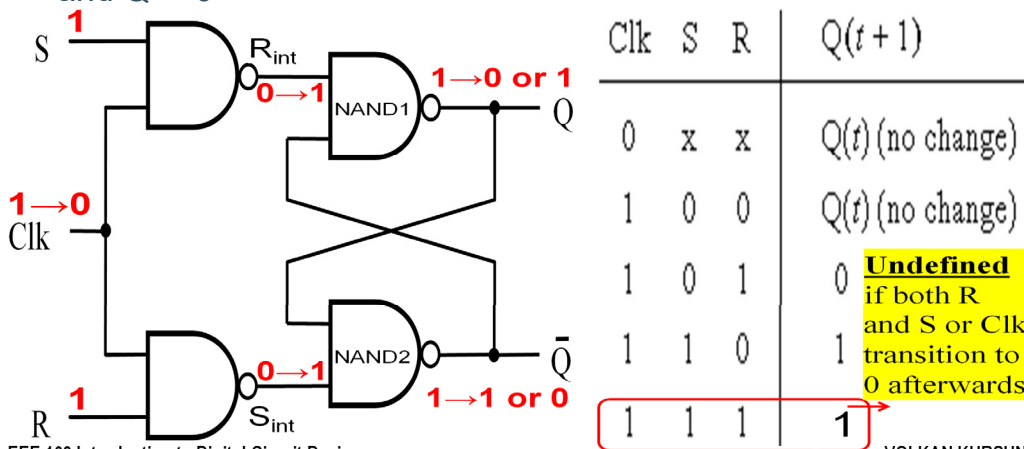
# NAND SR Latch Uncertainty

- In a real circuit, the delays of the two NAND gates will be different and the latch will eventually settle down to one of its two stable states (set or reset state): **however, the final state would be unknown (uncertain)**
- If  $\text{Delay}_{\text{NAND1}} < \text{Delay}_{\text{NAND2}}$ : will stabilize to  $Q = 0$  and  $Q' = 1$
- Alternatively, if  $\text{Delay}_{\text{NAND2}} < \text{Delay}_{\text{NAND1}}$ : will stabilize to  $Q = 1$  and  $Q' = 0$




EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN Bilkent University
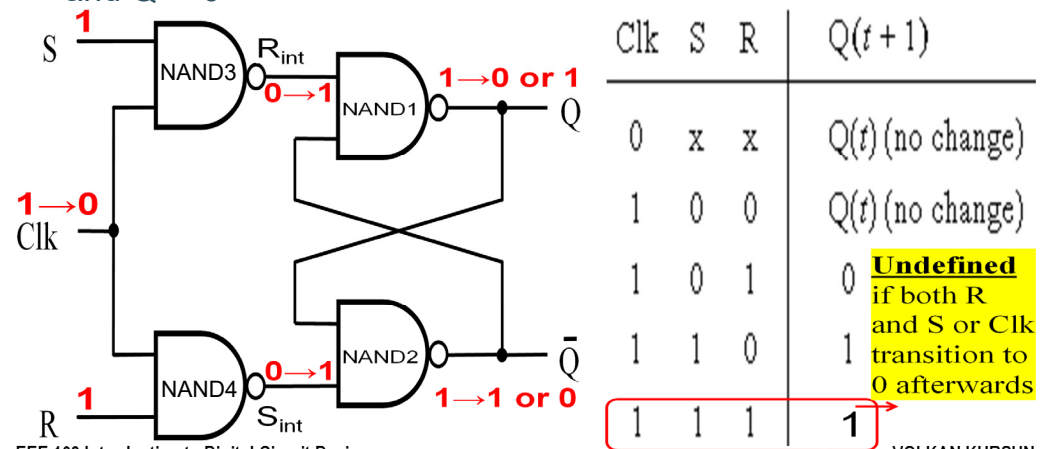
# NAND SR Latch Uncertainty

- Similarly, if the delays of NAND3 and NAND4 gates are different, the latch will settle down to one of its two stable states (set or reset state): **however, the final state would be unknown (uncertain)**
- If  $\text{Delay}_{\text{NAND3}} < \text{Delay}_{\text{NAND4}}$ : will stabilize to  $Q = 0$  and  $Q' = 1$
- Alternatively, if  $\text{Delay}_{\text{NAND4}} < \text{Delay}_{\text{NAND3}}$ : will stabilize to  $Q = 1$  and  $Q' = 0$



EEE 102 Introduction to Digital Circuit Design


VOLKAN KURSUN

## Outline

- Storage Elements
- Basic Latch
- Gated SR Latch
- Gated D Latch**

 
## Gated D Latch

- Stores the value of single data input (bit storage)
- Data is stored under the control of a clock signal: level-sensitive
- There is only one data input in a D latch and the internal Set and Reset signals are generated from the single data input:  $S = D$ ,  $R = D'$
- $\text{Clk} = 1$  and **D = 1**:  $S = 1$ ,  $R = 0$ , **set** the latch,  $Q = 1$
- $\text{Clk} = 1$  and **D = 0**:  $S = 0$ ,  $R = 1$ , **reset** the latch,  $Q = 0$



 
## Gated D Latch

- Since  $S = D$  and  $R = D'$ , the troublesome situation where  **$S = R = 1$  cannot occur in a D latch: no output uncertainty in a D latch**
- The output  $Q$  tracks the input  $D$  as long as  $\text{Clk} = 1$  (latch is transparent when  $\text{Clk} = 1$ ): level-sensitive behavior
- D latch stores the value of D shortly before the Clk transitions from 1 to 0**
- When  $\text{Clk} = 0$ , the latch is opaque and maintains state



 
## Gated D Latch Operation

- As long as  $\text{Clk} = 1$ , the  $Q$  output follows the  $D$  input
- When  $\text{Clk} = 0$ , the  $Q$  output cannot change and the latch maintains its state




Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

 

VOLKAN KURSUN Bilkent University
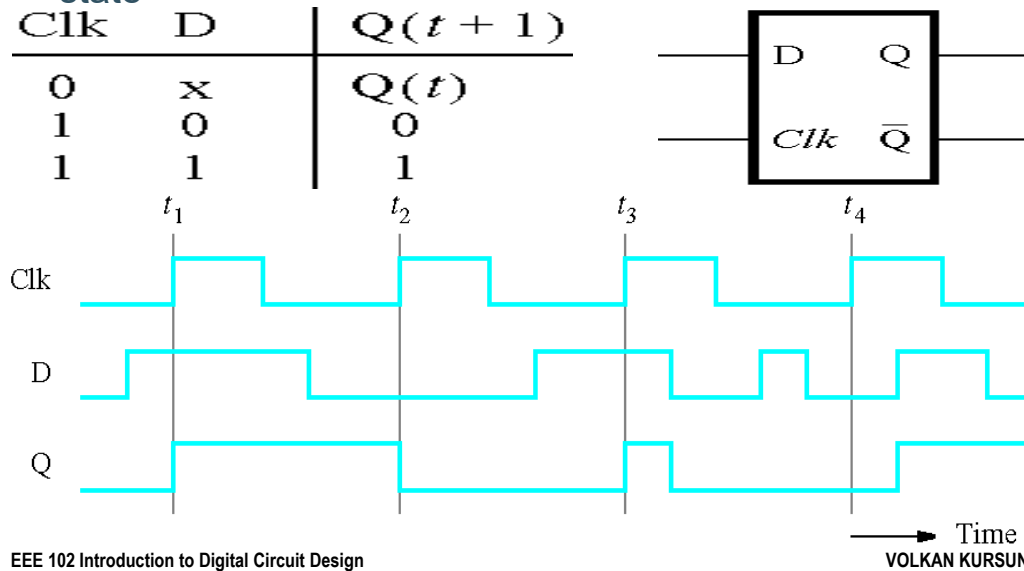
# Gated D Latch Timing Diagram


- As long as Clk = 1, the Q output follows the D input
- When Clk = 0, the Q output cannot change: maintains state



VOLKAN KURSUN Bilkent University
 
# Positive Latch Timing Definitions


- Transparent when clock is positive (clock = 1): Stores the value of D input that is present before the Clk 1 to 0 transition
- Opaque when the clock is negative (clock = 0)
- Set-up time
  - Valid data must arrive by set-up time before the negative edge of the clock (before the latch becomes opaque – end of the sampling period)
- Hold-time
  - Valid data must stay until hold time after the negative edge of the clock



VOLKAN KURSUN Bilkent University
 
# Negative Latch Timing Definitions

- Transparent when the clock is negative
  - Samples the input when clock = 0
- Opaque when the clock is positive (clock = 1)
- Set-up time
  - Valid data must arrive by set-up time before the positive edge of the clock (before the latch becomes opaque - end of the sampling period)
- Hold-time
  - Valid data must stay until hold time after the positive edge of the clock



VOLKAN KURSUN Bilkent University

# Gated D Latch VHDL

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY latch IS
    PORT (
        D, Clk : IN  STD_LOGIC ;
        Q      : OUT STD_LOGIC) ;
END latch ;
```

ARCHITECTURE Behavior OF latch IS

```
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

The code does not specify what Q should be assigned when the condition for the if statement is not satisfied: implies that the Q should maintain its value.

**IMPLIED MEMORY**