 



# Chapter 9 - ROM, RAM, Programmable Logic Devices

## Diode

Electronic component that conducts current primarily in one direction. E.g. p-n junction diode




Voltage-current characteristics (ideal)

 

$$\begin{array}{c} \circ \quad \circ \\ + \quad v \quad - \\ v < 0 \text{ then } i = 0 \end{array}$$

$$\begin{array}{c} \circ \quad \circ \\ + \quad v \quad - \\ i > 0 \text{ then } v = 0 \end{array}$$

Voltage-current characteristics (real)

 


William Shockley diode equation (co-inventor of transistor, 1956 Nobel prize):

$$\text{(current) } i = I_s * ( \exp( v / (n V_T) ) - 1 )$$


↑                      ↑                      ↗  
saturation current    ideality factor (between 1 and 2)    thermal voltage (temperature dependent)

## Logic functions using diodes and resistors.

Ex 1:  $Y = A + B + C$

 

Ex 2:  $Y = A \cdot B \cdot C$

 


## ROM (Read only memory)

- lookup table
- stores binary codes
- used to store firmware, TV remote control, BIOS, etc. Stores binary codes for sequence instructions

Many types:

 Masked ROM, Programmable ROM (PROM), UV Erasable PROM (EPROM), Electrically Erasable PROM (EEPROM)





non-volatile storage

# Diode ROM

8x4

8 nibble ROM

 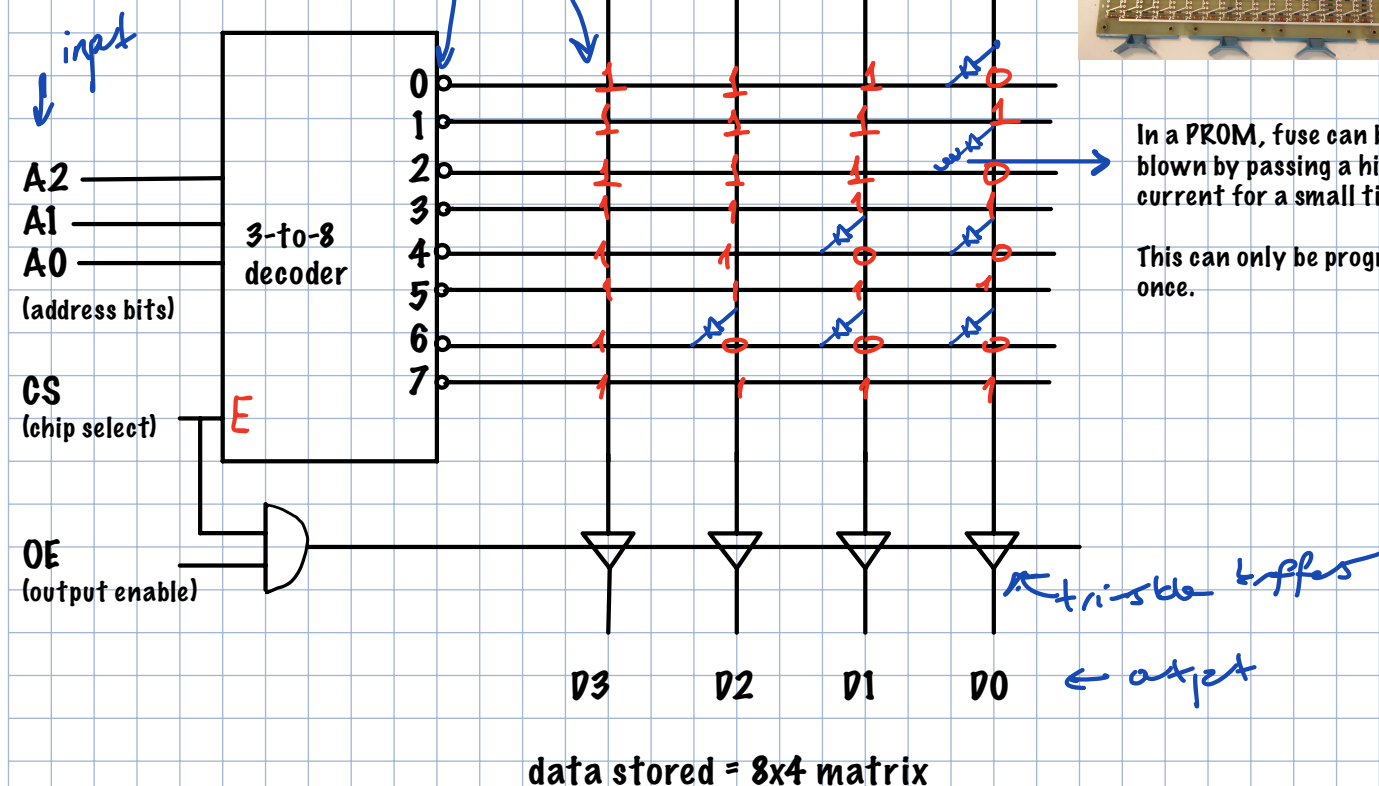

In a PROM, fuse can be blown by passing a high current for a small time.

This can only be programmed once.

- Default value for data is "1". Note: horizontal and vertical wires do not intersect!
- Put a diode whenever you want a "0" OR blow a fuse whenever you want a "1".
- Any truth table can be implemented.
- OE: Enables read operation
- CS: Used to select from multiple chips.

Data stored in the ROM above:

$x_2$	$x_1$	$x_0$	$D_3$	$D_2$	$D_1$	$D_0$
000	0	1	1	1	0	0
001			1	1	1	1
010			1	1	1	0
011	0	1	1	1	1	1
100			1	1	0	0
101	0	1	1	1	1	1
110	0	1	0	0	0	0
111			1	1	1	1


$$f(x_1, x_2, x_3) = x_1 \oplus x_2 \oplus x_3$$

$$D_3 = f(x_1, x_2, x_3)$$


⇒ can implement 4 3-input logic functions.

- $2^m \times n$  ROM can be built using  $m$  to  $2^m$  decoder for the address bits
- Any  $m$  input  $n$  output combinational circuit can be stored in a  $2^m \times n$  ROM.

## Are diodes necessary?

 

w1 = low then D1 low, D0 high

 

## Other Types of ROM

### EPROM

- Uses MOS transistors instead of diodes
- Programmed with EPROM programmer
- Erase stored data by exposing the chip to UV light for several minutes

### EEPROM

8 bits


- Allows individual Bytes to be erased or programmed
- Limited life for erasing and reprogramming (reaching a million operations in modern EEPROMs)
- Uses floating-gate MOSFET

### Flash Memory (Flash ROM)

- Variation of EEPROM
- EEPROM: erased and programmed at byte level
- Flash: erased and programmed in blocks (faster)
- Used in BIOS (basic input/output system), cell phones, LAN switches, USB flash drive.

## ROM Read Timing

How can we read content of address 100?

 

Exercise: design an FSM

to generate correct timing of signals to read

$S_0$ : idle from ROM



$S_1$  CLK 1: give address

$S_2$  CLK 2: select chip

$S_3$  CLK 3: enable output



$S_4$  CLK 4: read data into register

symbol for 8 nibble ROM

  

Making wider memory: 8 Byte ROM from 8 nibble ROM

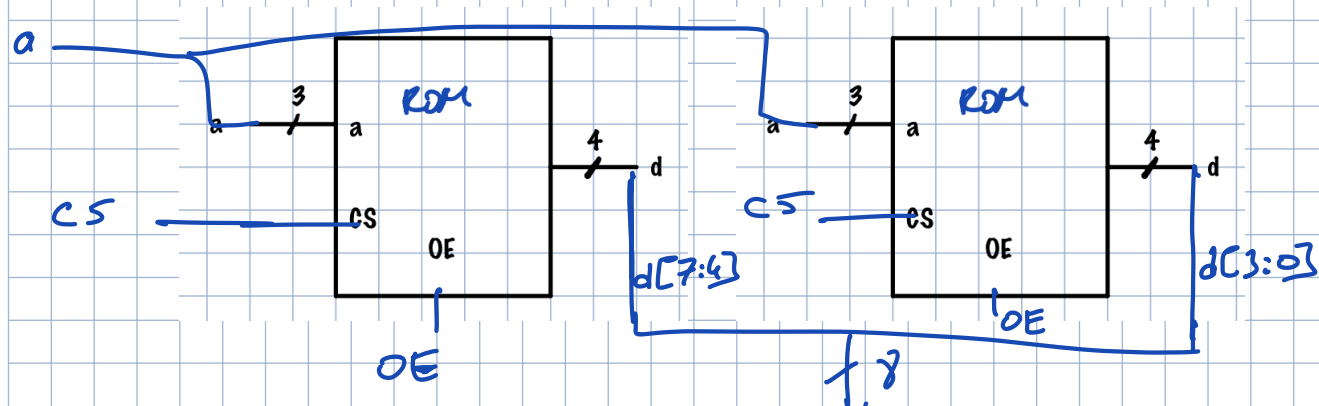 8 Byte ROM: 3 bit address input. CS input, OE input. 8 bit data output.




## Making larger memory. 16 nibble ROM from 8 nibble ROM

16x4

8x4

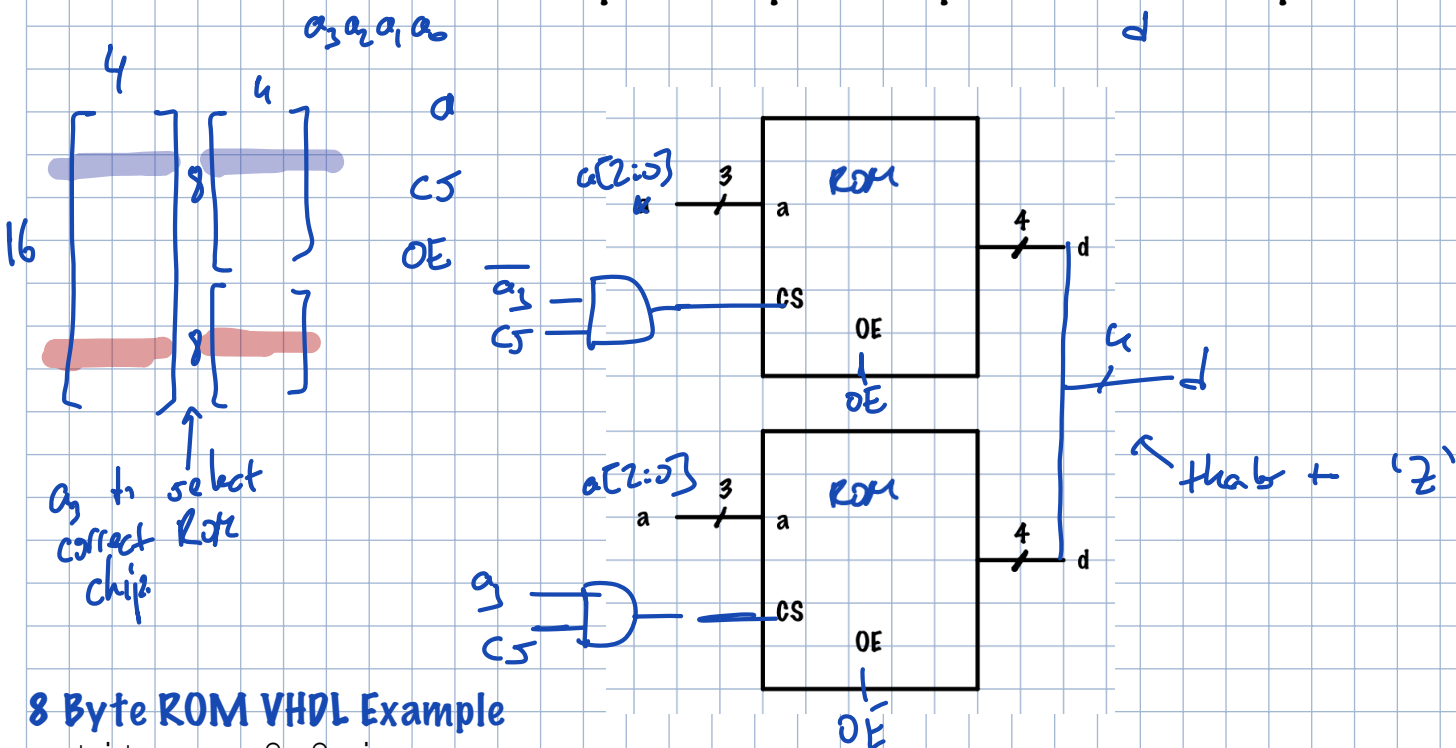16 nibble ROM: 4 bit address input. CS input. OE input. 4 bit data output.



## 8 Byte ROM VHDL Example

entity rom8x8 is

port(address: in integer range 0 to 7;

data: out std\_logic\_vector(7 downto 0);

CS, OE: in std\_logic);

end entity;

architecture rom\_arch of rom8x8 is

type rom\_array is array (0 to 7) of std\_logic\_vector(7 downto 0);

constant rom: rom\_array := ("11111011", "00010010",  
"10011011", "10010011", "01011011", "00111010", "11111011",  
"00010010");

begin

process(address, CS, OE) begin

data<=(others=>'Z'); --chip not selected

if CS='1' then

if OE='1' then --read

data<=rom(address);

end if;

end if;

end process;

end architecture;

The constant is a data object whose value cannot be changed. Unlike signal it does not represent a wire in the circuit.

## RAM (Random Access Memory)


**Random access:** access time independent of the location (address).

### Any storage device with location dependent access time?


RAM is volatile

Usualy operations: read & write  
/ active high

## 8 nibble RAM

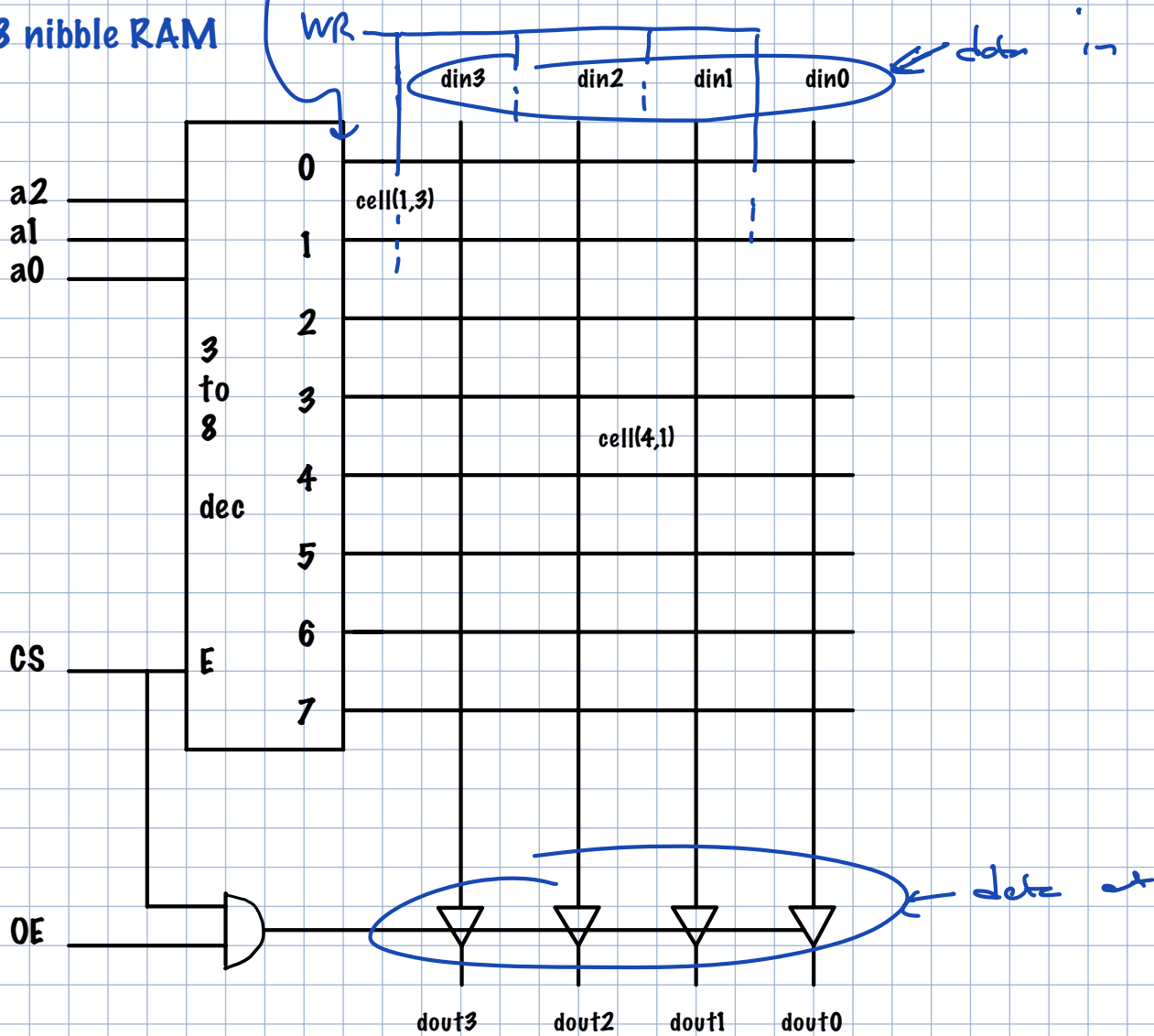
 
## Logic diagram of RAM cell (32 of them in 8x8)



## RAM Read and Write Timing


### Task:

1. Read address 110
2. Write 1010 to address 110
3. Read address 101
4. Read address 110

### Initial contents:

Address	Data
000	1110
001	1111
010	1110
011	1111
100	1100
101	1111
110	1000
111	1111



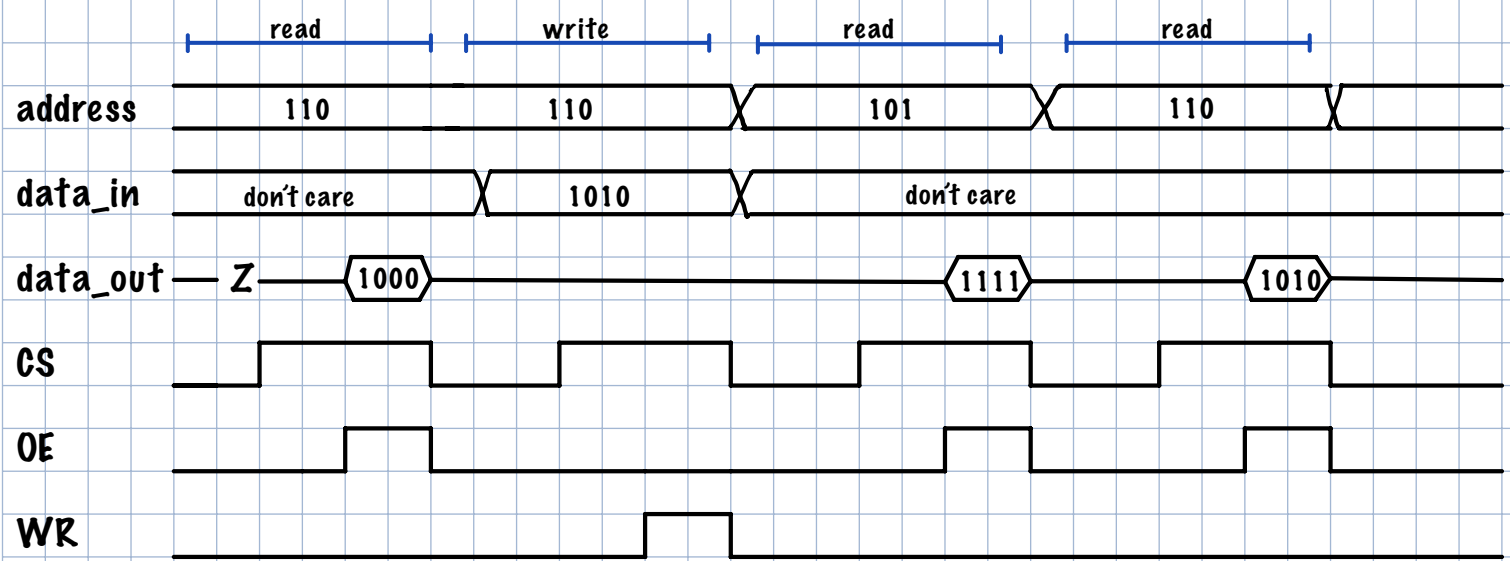

## VHDL code for 64 Byte RAM

```
use ieee.std_logic_arith.all
```

```
entity ram64x8 is
```

```
    port(address: in unsigned(5 downto 0);
```

```
          data: inout std_logic_vector(7 downto 0);
```

```
          WR, CS, OE: in std_logic);
```

```
end ram64x8;
```

```
architecture ram_arch of ram64x8 is
```

```
    type ram_type is array (0 to 63) of std_logic_vector(7 downto 0);
```

```
    signal raml: ram_type;
```

```
begin
```

```
    process(address,WR,CS,OE) begin
```

```
        data<=(others=>'Z'); --chip not selected
```

```
        if CS='1' then
```

```
            if WR='1' then --write
```

```
                raml(conv_integer(address))<=data;
```

```
            end if;
```

```
            if WR='0' and OE='1' then --read
```

```
                data<=raml(conv_integer(address));
```

```
            else
```

```
                data<=(others=>'Z');
```

```
            end if;
```

```
        end if;
```

```
    end process;
```


```
end ram_arch;
```

conv\_integer: converts its argument to an integer.


# Programmable Logic Device (PLD)

Contains logic gates with programmable switches (introduced in 1970s)

## Programmable Logic Array (PLA)

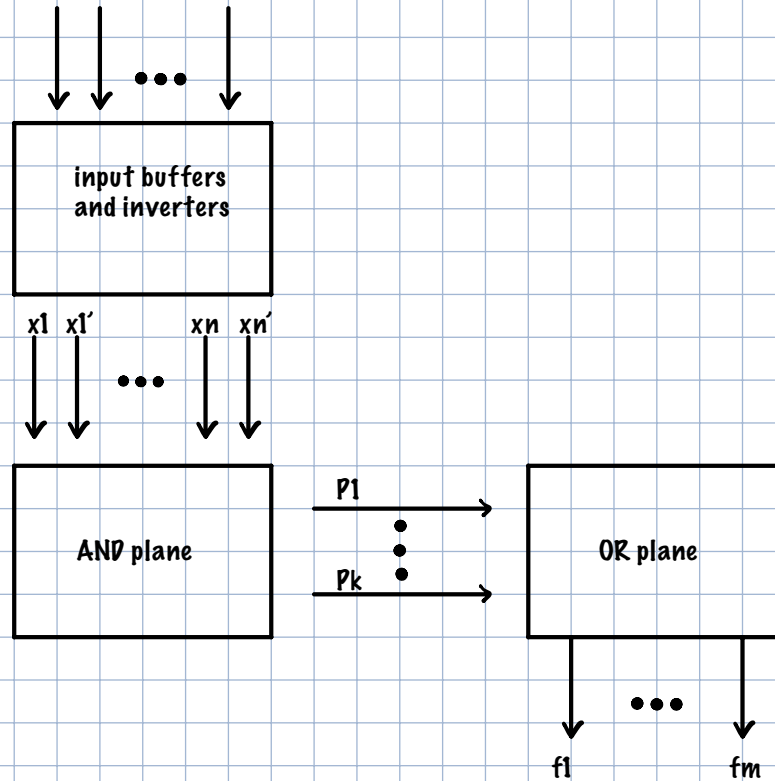

 - **AND-OR array**
- Implements logic functions in sum of products form
- Both AND and OR gates are programmable
- Programming can be made by melting metal fuses (one-time programmable)
- Size of the AND plane constrains the set of functions that can be implemented



Can we implement the following? ✓

$$f_1 = x_1x_2 + x_1'x_3$$

$$f_2 = x_1'x_3 + x_1'x_2' + x_1x_2x_3$$

What about

$$f_1 = x_1x_2 + x_1'x_2x_3$$

$$f_2 = x_1'x_2'x_3' + x_1x_2x_3 + x_1'x_2x_3' + x_1x_3$$

not directly  
maybe a simplified form  
fibo ✓


$$f_2 = x_1 x_3 + \bar{x}_1 \bar{x}_3$$

## Programmable Array Logic (PAL)


- AND plane programmable, OR plane fixed
- Less expensive than PLA
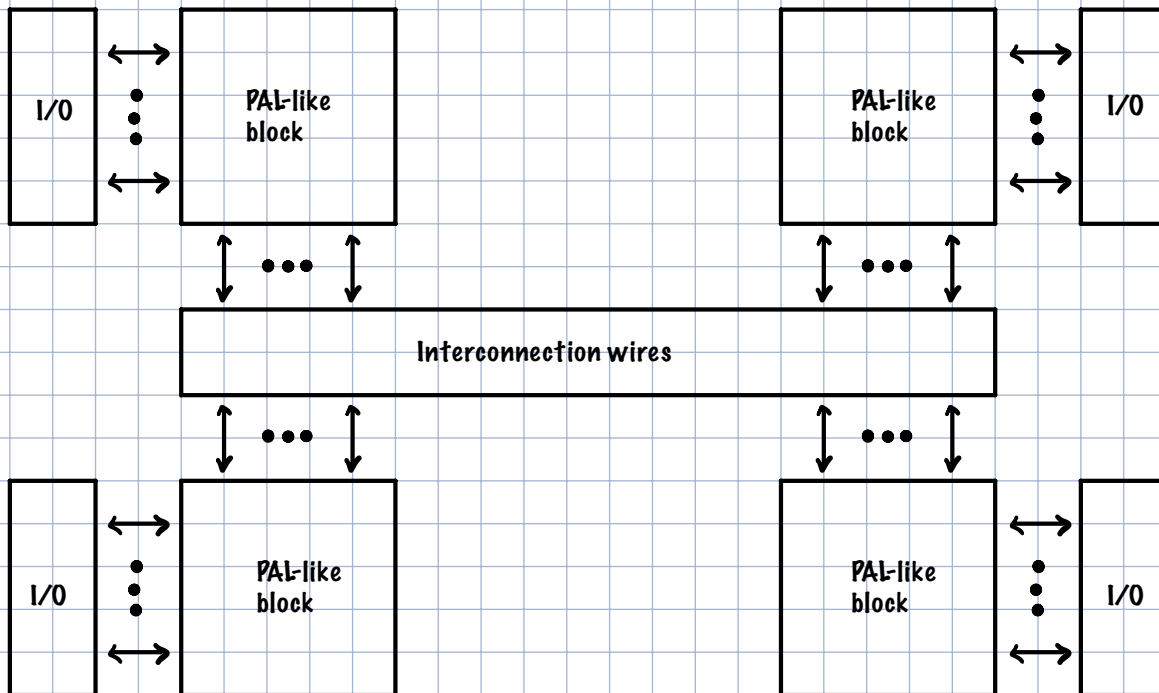
## Complex Programmable Logic Devices (CPLD)

PLA and PAL most of the time limited to 32 inputs+outputs



PAL-like block:

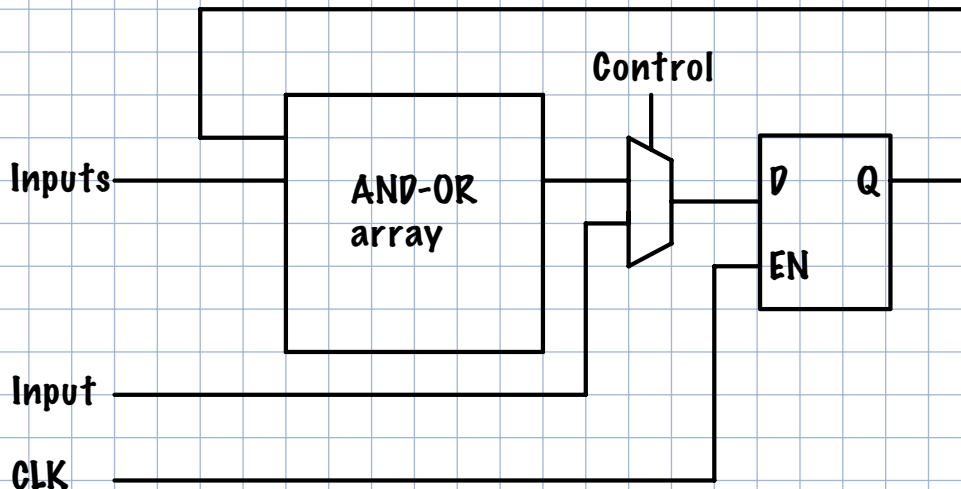

- Large CPLDs have more than 200 PAL-like blocks
- To be programmed in a programming unit, a socket is required to hold the chip
- Sockets are expensive
- Printed circuit board (PCB) that contains CPLD has a small connector to program the CPLD
- JTAG (Joint Test Action Group) port is used to transfer programming information from the computer into the CPLD. This is called in system programming.

## FPGA (Field Programmable Gate Array)


- No AND-OR plane
- Can implement millions of gates
- Consists of logic blocks that act like a look up table (LUT)
- Storage cells are made up of SRAM
- FPGA LUTs are volatile

Ex: Basys3, Artix-7 FPGA

-Consists of 5200 slices

-Each slice consists of four 6 input LUT and 8 FFs

Ex: 2 input LUT

 

$x_1$	$x_2$	$f$
0	0	1
0	1	0
1	0	0
1	1	1

$$f = x_1 \text{ XNOR } x_2$$