

BILKENT UNIVERSITY  
Department of Electrical and Electronics Engineering  
EEE102 Introduction to Digital Circuit Design  
MidTerm Exam II SOLUTION  
29-04-2006  
Duration 110 minutes

Surname: \_\_\_\_\_

Name: \_\_\_\_\_

ID-Number: \_\_\_\_\_


Signature: \_\_\_\_\_

There are 5 questions of equal weights. Total weight of the exam is 110 points (10 points bonus). Solve all. Do not detach pages.  
Show all your work.


Q1	
Q2	
Q3	
Q4	
Q5	
TOTAL	

**Q1. For the circuit below obtain and write excitation table, output table, next state table, and also the state definitions and diagram. Is this a Moore or Mealy FSM, why? X is the input and  $Y_1Y_0$  is the output of this circuit. Explain the function of the RESET input, and include it in your state diagram.**

SOLUTION:

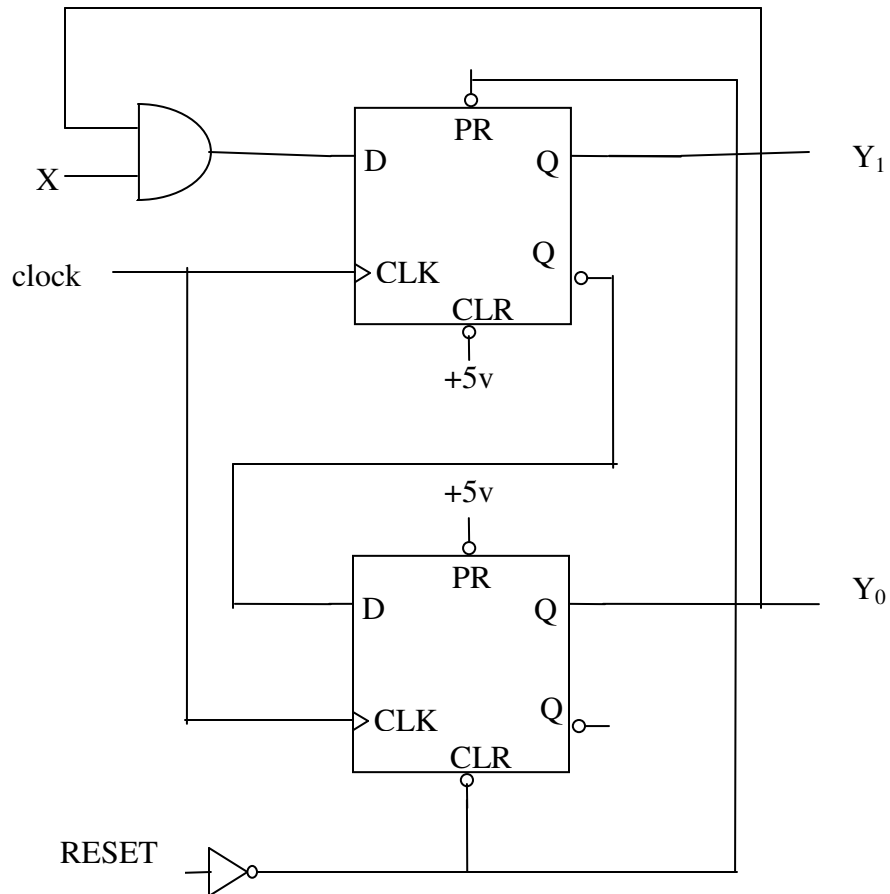

SOLUTION:

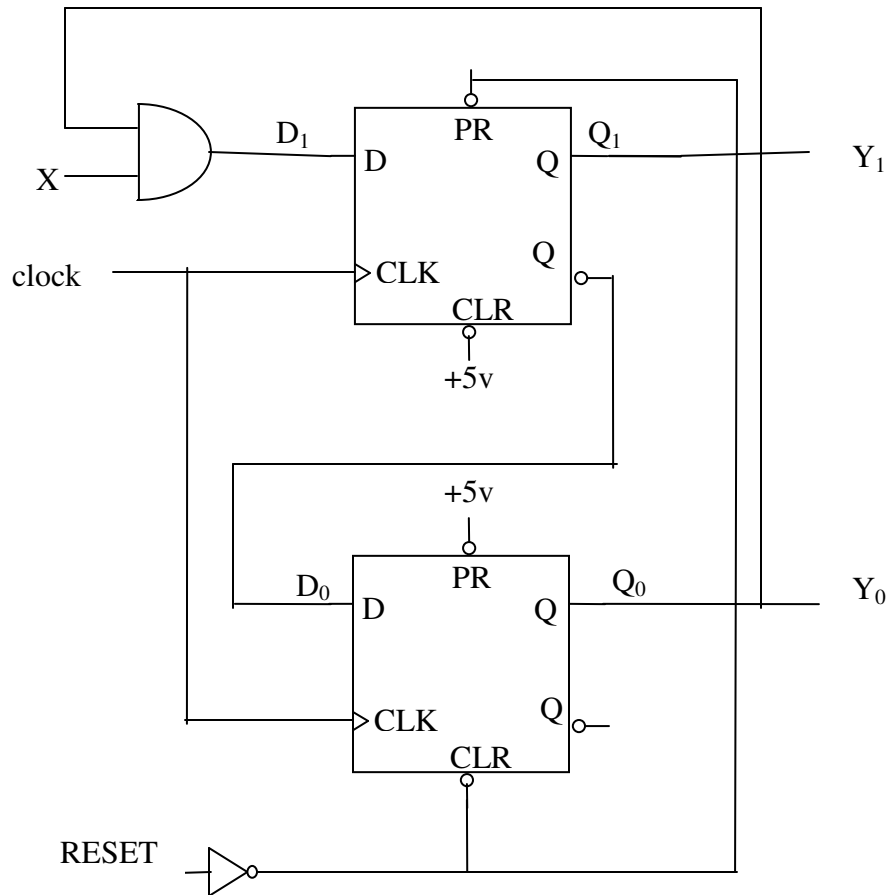

Excitation Equations:  $D_1 = XQ_0$  and  $D_0 = Q_1'$   
Excitation table is

$Q_1$	$Q_0$	X(at tick)	$D_1$	$D_0$
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	0

Next state table is the same as the excitation table with  $D_1$  replaced by  $Q_1^*$  and  $D_0$  replaced by  $Q_0^*$ .

Output equations:  $Y_1 = Q_1$  and  $Y_0 = Q_0$


Output table

$Q_1$	$Q_0$	$Y_1$	$Y_0$
0	0	0	0
0	1	0	1
1	0	1	0
1	1	1	1

State Encoding

name	$Q_1$	$Q_0$
$S_0$	0	0
$S_1$	0	1
$S_2$	1	0
$S_3$	1	1

State diagram

 

Note that I have indicated in the state circles also the outputs, and therefore the above diagram is in fact a state/output diagram.

RESET is an asynchronous input which makes the FSM go to state  $S_2$  independent of the clock.

This FSM is a Moore FSM if do not consider RESET as a proper input.

It is a Mealy FSM if we consider RESET as a proper input as well.

**Q2. Write VHDL code for a 3-to-8 generic decoder (with enable), which has all inputs and and outputs active-high, using structural type programming using two instances of the following module which is already available in the library.**

**SOLUTION:**

```
library IEEE;
```

```

use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

entity cat is

```

    Port ( E : in std_logic;
           S : in std_logic_vector(1 downto 0);
           Y : out std_logic_vector(0 to 3));
end cat;

```

architecture Behavioral of cat is

```

    signal temp:std_logic_vector(0 to 3);
begin
    with S select  temp <=
        "1000" when "00",
        "0100" when "01",
        "0010" when "10",
        "0001" when "11",
        "0000" when others;
    Y <= temp when E = '1' else "0000";
end Behavioral;

```

Solution:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

entity top is

```

    Port ( EN : in std_logic;
           SEL : in std_logic_vector(2 downto 0);
           DECOUT : out std_logic_vector(0 to 7));
end top;

```

architecture Behavioral of top is

component cat is

```

    Port ( E : in std_logic;
           S : in std_logic_vector(1 downto 0);
           Y : out std_logic_vector(0 to 3));
end component;

```

```

signal G0,G1:std_logic_vector(0 to 3);
signal Z0,Z1:std_logic;
signal SS:std_logic_vector(1 downto 0);
begin
SS<= SEL(1)&SEL(0);


```

```

Z0<= EN and not SEL(2);
Z1<=EN and SEL(2);
L1: cat port map (Z0,SS,G0);
L2: cat port map (Z1,SS,G1);
DECOU<=G0&G1;
end Behavioral;


```

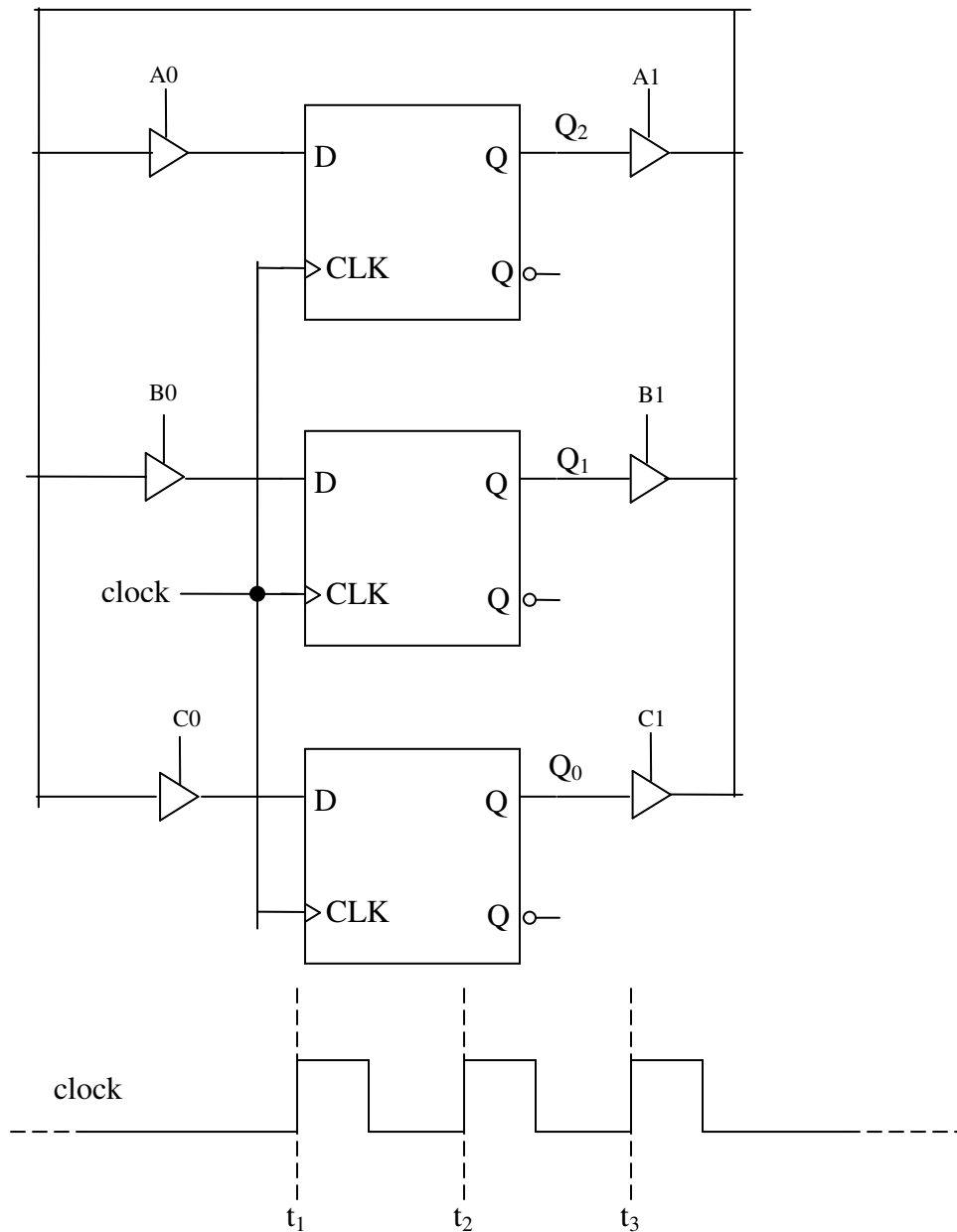**Q3. For the circuit and the clock signal shown below,  $Q_2 = X$ ,  $Q_1 = Y$ , and  $Q_0 = '0'$  before time  $t_1$ . Draw time waveforms for A0,A1,B0,B1,C0, and C1 so that  $Q_2 = Y$ , and  $Q_1 = X$  after time  $t_3$  (in other words the values of  $Q_2$  and  $Q_1$  are switched).**




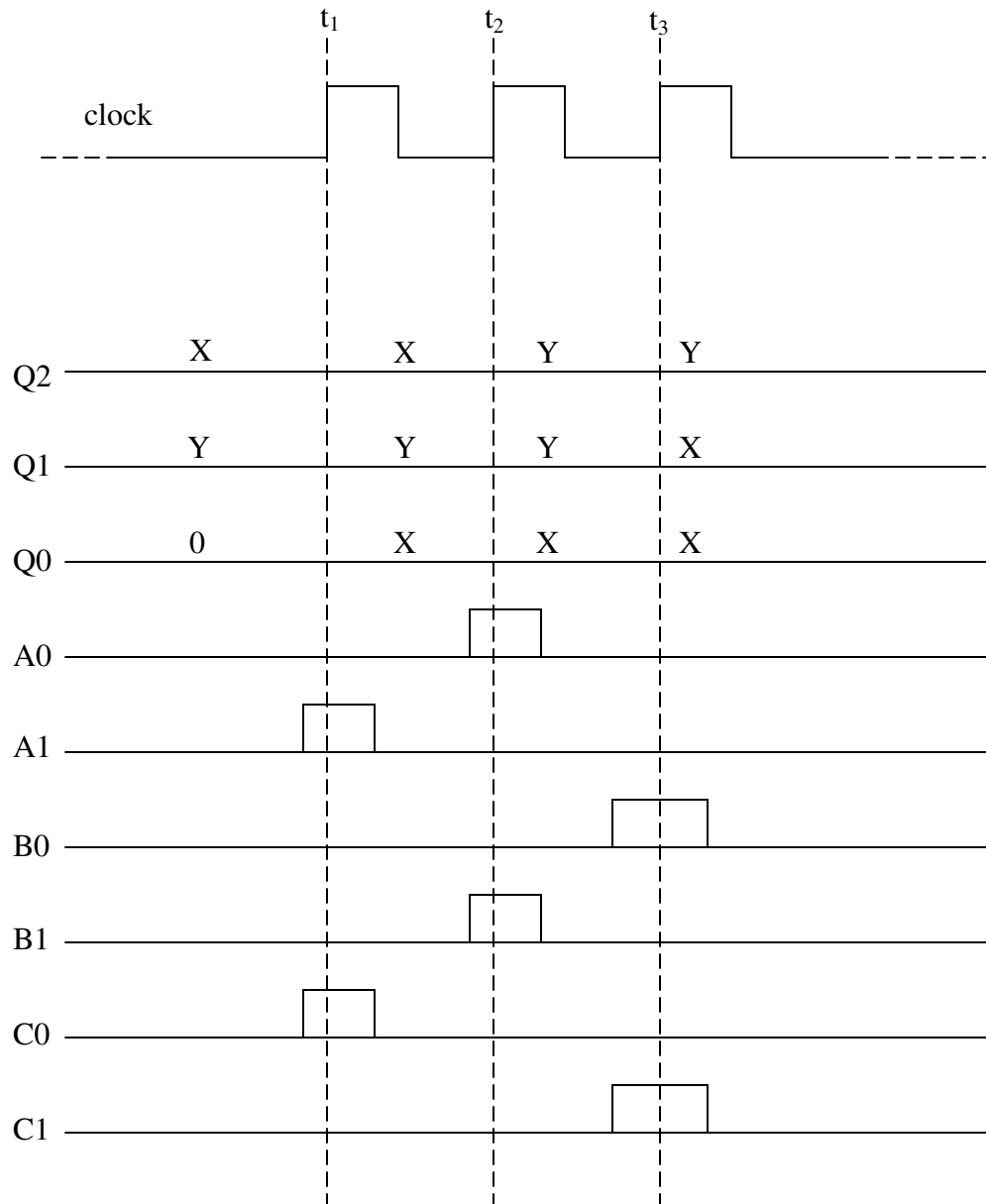**SOLUTION:**

As announced during the exam we assume if a ff's input is at high Z then its output is not changed at a clock tick. (Of course it is possible to include circuitry to guarantee this assumption but it makes the circuit look very complicated, therefore it was not drawn).




 For your information: One possible way of guaranteeing the above assumption is to gate the clock. For example (shown only for the first ff) the following circuit does it.




**Q4. The internal circuit of a PAL which has 2 input pins and 3 input-output pins is drawn below. In this PAL, AND gate inputs are '1' if they are not connected. Implement the function  $F = A'B' + BC' + ABC$  using this PAL. Do not simplify or modify the expression. Do not use any external wire or component.**

**SOLUTION:**

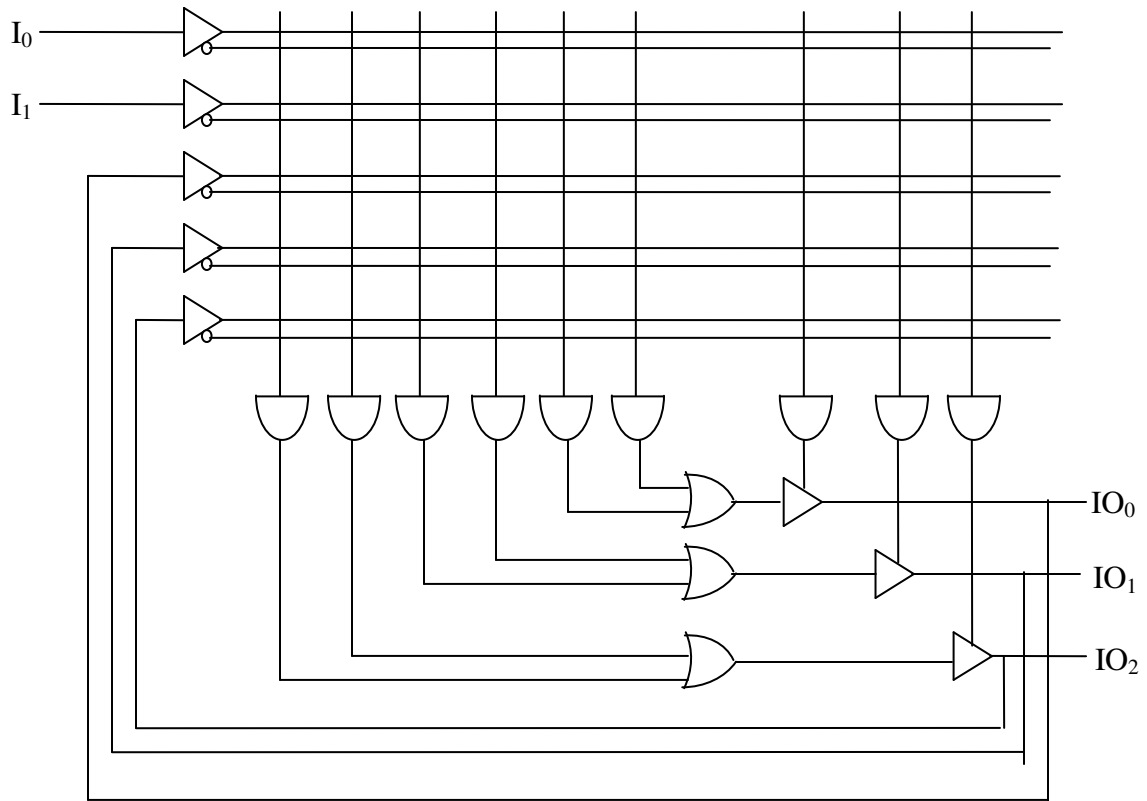


 To avoid any confusion, the pin diagram (excluding ground and supply connections) of the above PAL is given below:






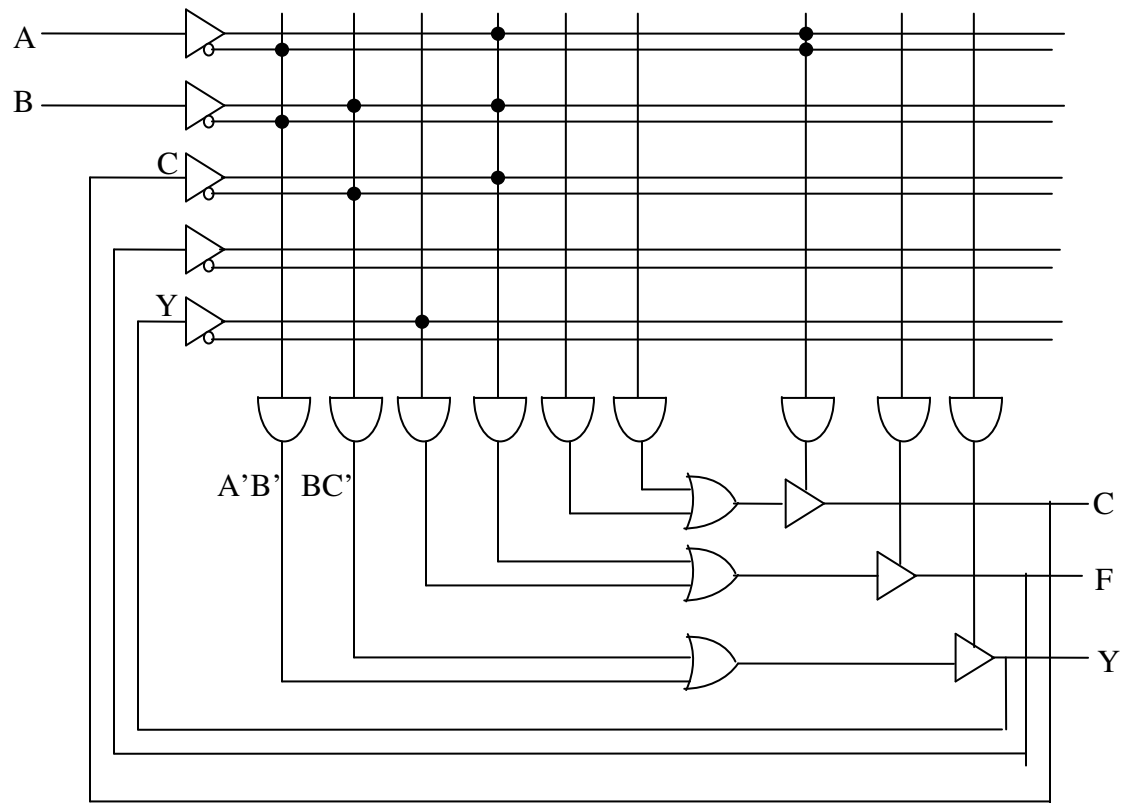Solution: Say  $Y = A'B' + BC'$ . Then  $F = Y + ABC$



 **Q5. We have 2-to-1 multiplexers in stock. These have active-high pins and the block diagram is as follows:**



**a) Design and draw a circuit which implements this 2-to-1 multiplexer, using NAND and NOT gates.**

**b) Use 3 of these 2-to-1 multiplexers, a 2-to-4 decoder, and additional minimum number of simple gates to realize a 6-to-1 multiplexer which has the following properties: It has three control inputs S2, S1, S0, six data inputs D0, D1, D2, D3, D4, D5 and two outputs OUT and ERROR. It has the following function table:**


Function	S2	S1	S0	OUT	ERROR
(choose)	0	0	0	D0	0
(choose)	0	0	1	D1	0
(choose)	0	1	0	D2	0
(choose)	0	1	1	D3	0
(choose)	1	0	0	D4	0
(choose)	1	0	1	D5	0
(disable)	1	1	0	0	0
(error)	1	1	1	0	1

SOLUTION:

a)

EN	S	Y
0	0	0
0	1	0
1	0	$I_0$
1	1	$I_1$

Thus  $Y = EN.S'.I_0 + EN.S.I_1$

 

b)

