

Counters


Revisited

VOLKAN KURSUN

Some material from McGraw Hill

Counter Design as an FSM

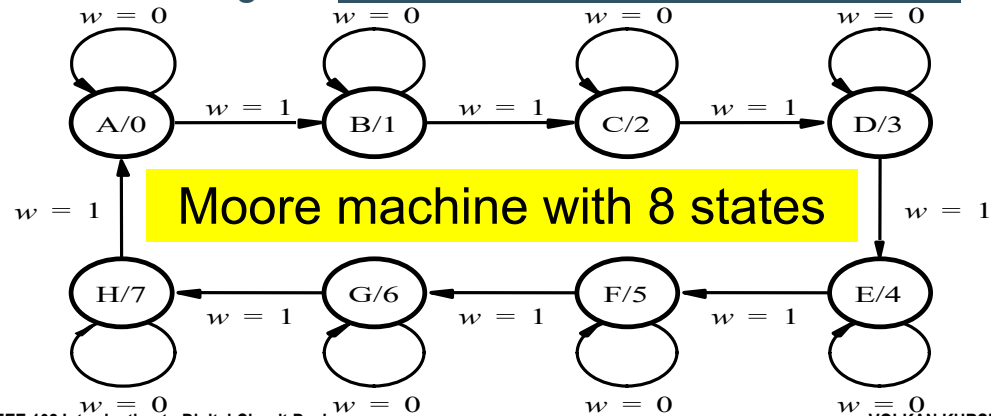- The counting sequence is 0, 1, 2, 3, 4, 5, 6, 7, 0, 1...
- An input signal w : if $w = 0$, maintain state (pause counting). If $w = 1$, increment the counter
- **Design** the counter as a synchronous sequential circuit using the formal fsm design methodology




Outline

- Counter Design as FSM
- A Different Counter
- Self Correcting Ring Counter
- Self Correcting Johnson Counter

Counter State Table

- The counting sequence is 0, 1, 2, 3, 4, 5, 6, 7, 0, 1...

Present state	Next state		Output
	$w = 0$	$w = 1$	
A	A	B	0
B	B	C	1
C	C	D	2
D	D	E	3
E	E	F	4
F	F	G	5
G	G	H	6
H	H	A	7

 

Counter State Assigned Table

□ The counting sequence is 0, 1, 2, 3, 4, 5, 6, 7, 0, 1...

	Present state $y_2 y_1 y_0$	Next state		Count $z_2 z_1 z_0$
		$w = 0$	$w = 1$	
		$Y_2 Y_1 Y_0$	$Y_2 Y_1 Y_0$	
A	000	000	001	000
B	001	001	010	001
C	010	010	011	010
D	011	011	100	011
E	100	100	101	100
F	101	101	110	101
G	110	110	111	110
H	111	111	000	111

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

Counter Implementation with D

□ The counting sequence is 0, 1, 2, 3, 4, 5, 6, 7, 0, 1...

	Present state $y_2 y_1 y_0$	Next state		Count $z_2 z_1 z_0$
		$w = 0$	$w = 1$	
		$Y_2 Y_1 Y_0$	$Y_2 Y_1 Y_0$	
A	000	000	001	000
B	001	001	010	001
C	010	010	011	010
D	011	011	100	011
E	100	100	101	100
F	101	101	110	101
G	110	110	111	110
H	111	111	000	111

$y_1 y_0$	$w y_2$	$y_1 y_0$			
		00	01	11	10
00	00	0	1	1	0
01	00	0	1	1	0
11	11	1	0	0	1
10	10	1	0	0	1

$$Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2$$


EEE 102 Introduction to Digital Circuit Design

$$Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1$$

VOLKAN KURSUN

Counter Implementation with D
 
$$Y_0 = \bar{w}y_0 + w\bar{y}_0 \quad Y_1 = \bar{w}y_1 + y_1\bar{y}_0 + wy_0\bar{y}_1 \quad Y_2 = \bar{w}y_2 + \bar{y}_0y_2 + \bar{y}_1y_2 + wy_0y_1\bar{y}_2$$



EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

Counter Implementation with JK

□ The counting sequence is 0, 1, 2, 3, 4, 5, 6, 7, 0, 1...

	Present state $y_2y_1y_0$	Flip-flop inputs								Count $z_2z_1z_0$
		$w = 0$				$w = 1$				
		$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	
A	000	000	0d	0d	0d	001	0d	0d	1d	000
B	001	001	0d	0d	d0	010	0d	1d	d1	001
C	010	010	0d	d0	0d	011	0d	d0	1d	010
D	011	011	0d	d0	d0	100	1d	d1	d1	011
E	100	100	d0	0d	0d	101	d0	0d	1d	100
F	101	101	d0	0d	d0	110	d0	1d	d1	101
G	110	110	d0	d0	0d	111	d0	d0	1d	110
H	111	111	d0	d0	d0	000	d1	d1	d1	111

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

JK Flip-Flop Excitation Table			
$q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

Counter Implementation with JK

	Present state $y_2y_1y_0$	Flip-flop inputs								Count $z_2z_1z_0$
		$w = 0$				$w = 1$				
		$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	
A	000	000	0d	0d	0d	001	0d	0d	1d	000
B	001	001	0d	0d	d0	010	0d	1d	d1	001
C	010	010	0d	d0	0d	011	0d	d0	1d	010
D	011	011	0d	d0	d0	100	1d	d1	d1	011
E	100	100	d0	0d	0d	101	d0	0d	1d	100
F	101	101	d0	0d	d0	110	d0	1d	d1	101
G	110	110	d0	d0	0d	111	d0	d0	1d	110
H	111	111	d0	d0	d0	000	d1	d1	d1	111

y_1y_0

wy_2

	00	01	11	10
00	0	0	0	0
01	d	d	d	d
11	d	d	d	d
10	0	0	1	0

$$J_2 = wy_0y_1$$

y_1y_0

wy_2

	00	01	11	10
00	d	d	d	d
01	0	0	0	0
11	0	0	1	0
10	d	d	d	d

$$K_2 = wy_0y_1$$

Counter Implementation with JK

	Present state $y_2y_1y_0$	Flip-flop inputs								Count $z_2z_1z_0$
		$w = 0$				$w = 1$				
		$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	
A	000	000	0d	0d	0d	001	0d	0d	1d	000
B	001	001	0d	0d	d0	010	0d	1d	d1	001
C	010	010	0d	d0	0d	011	0d	d0	1d	010
D	011	011	0d	d0	d0	100	1d	d1	d1	011
E	100	100	d0	0d	0d	101	d0	0d	1d	100
F	101	101	d0	0d	d0	110	d0	1d	d1	101
G	110	110	d0	d0	0d	111	d0	d0	1d	110
H	111	111	d0	d0	d0	000	d1	d1	d1	111

y_1y_0

wy_2

	00	01	11	10
00	0	0	d	d
01	0	0	d	d
11	0	1	d	d
10	0	1	d	d

$$J_1 = wy_0$$

y_1y_0

wy_2

	00	01	11	10
00	d	d	0	0
01	d	d	0	0
11	d	d	1	0
10	d	d	1	0

$$K_1 = wy_0$$

Counter Implementation with JK

	Present state $y_2y_1y_0$	Flip-flop inputs								Count $z_2z_1z_0$
		$w = 0$				$w = 1$				
		$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	$Y_2Y_1Y_0$	J_2K_2	J_1K_1	J_0K_0	
A	000	000	0d	0d	0d	001	0d	0d	1d	000
B	001	001	0d	0d	d0	010	0d	1d	d1	001
C	010	010	0d	d0	0d	011	0d	d0	1d	010
D	011	011	0d	d0	d0	100	1d	d1	d1	011
E	100	100	d0	0d	0d	101	d0	0d	1d	100
F	101	101	d0	0d	d0	110	d0	1d	d1	101
G	110	110	d0	d0	0d	111	d0	d0	1d	110
H	111	111	d0	d0	d0	000	d1	d1	d1	111

y_1y_0

wy_2

	00	01	11	10
00	0	d	d	0
01	0	d	d	0
11	1	d	d	1
10	1	d	d	1

$$J_0 = w$$

y_1y_0


wy_2

	00	01	11	10
00	d	0	0	d
01	d	0	0	d
11	d	1	1	d
10	d	1	1	d

$$K_0 = w$$

Counter Implementation with JK
 
$$J_2 = wy_0y_1 \quad K_2 = wy_0y_1 \quad J_1 = wy_0 \quad K_1 = wy_0 \quad J_0 = w \quad K_0 = w$$



Outline

- Counter Design as FSM
- A Different Counter**
- Self Correcting Ring Counter
- Self Correcting Johnson Counter

A Different Counter Sequence

- The counting sequence is 0, 4, 2, 6, 1, 5, 3, 7, 0, 4...
- Assume the counter is always enabled

State Table

Present state	Next state	Output $z_2 z_1 z_0$
A	B	000
B	C	100
C	D	010
D	E	110
E	F	001
F	G	101
G	H	011
H	A	111

State Assigned Table

Present state $y_2 y_1 y_0$	Next state $Y_2 Y_1 Y_0$	Output $z_2 z_1 z_0$
000	100	000
100	010	100
010	110	010
110	001	110
001	101	001
101	011	101
011	111	011
111	000	111

Counter Implementation

$y_1 y_0$	00	01	11	10
y_2				
0	1	1	1	1
1	0	0	0	0

$$Y_2 = y_2'$$

Present state $y_2 y_1 y_0$	Next state $Y_2 Y_1 Y_0$	Output $z_2 z_1 z_0$
000	100	000
100	010	100
010	110	010
110	001	110
001	101	001
101	011	101
011	111	011
111	000	111

$y_1 y_0$	00	01	11	10
y_2				
0	0	1	1	0
1	0	1	0	1

$$Y_1 = y_2' y_1 + y_2 y_1'$$


$$= y_2 \oplus y_1$$

$$Y_0 = y_2' y_0 + y_1' y_0 + y_2 y_1 y_0'$$

$$= y_0 (y_1' + y_2') + y_0' y_2 y_1 = y_0 \oplus (y_2 y_1)$$

Counter Implementation
 
$$Y_2 = y_2' \quad Y_1 = y_2 \oplus y_1 \quad Y_0 = y_0 \oplus (y_2 y_1)$$




Clock

Outline

- Counter Design as FSM
- A Different Counter
- Self Correcting Ring Counter
- Self Correcting Johnson Counter


Shift Left Ring Counter

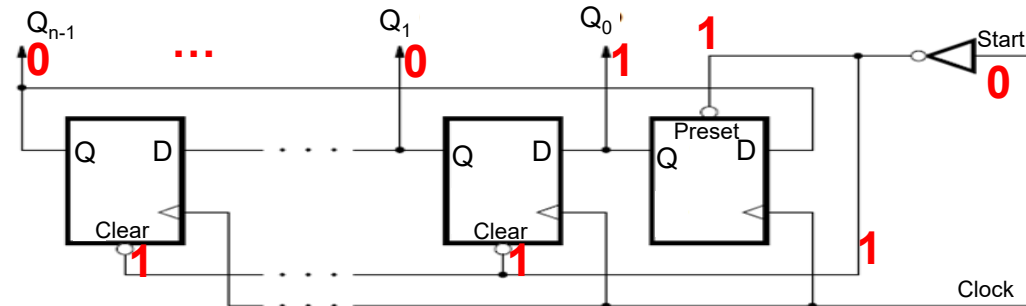- 0001 → 0010 → 0100 → 1000 → 0001...
 - **Start = 0**: count (shift left) with the positive edges of the clock
- $$Q(N-1) \leq Q(N-2), Q(N-2) \leq Q(N-3), \dots,$$
- $$Q(1) \leq Q(0), Q(0) \leq Q(N-1)$$




Shift Left Ring Counter

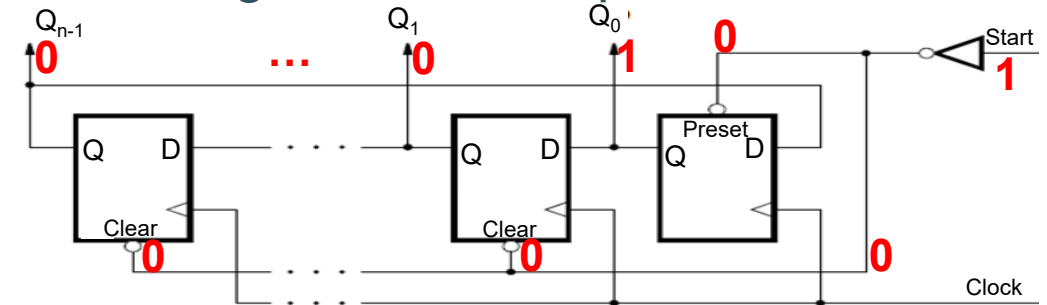
- ❑ $0001 \rightarrow 0010 \rightarrow 0100 \rightarrow 1000 \rightarrow 0001 \dots$
- ❑ Can be implemented with a shift-register with the following connections
- ❑ **Start = 1**: inject 1 into the LSB while clearing the other bit positions



4-Bit Shift Left Ring Counter

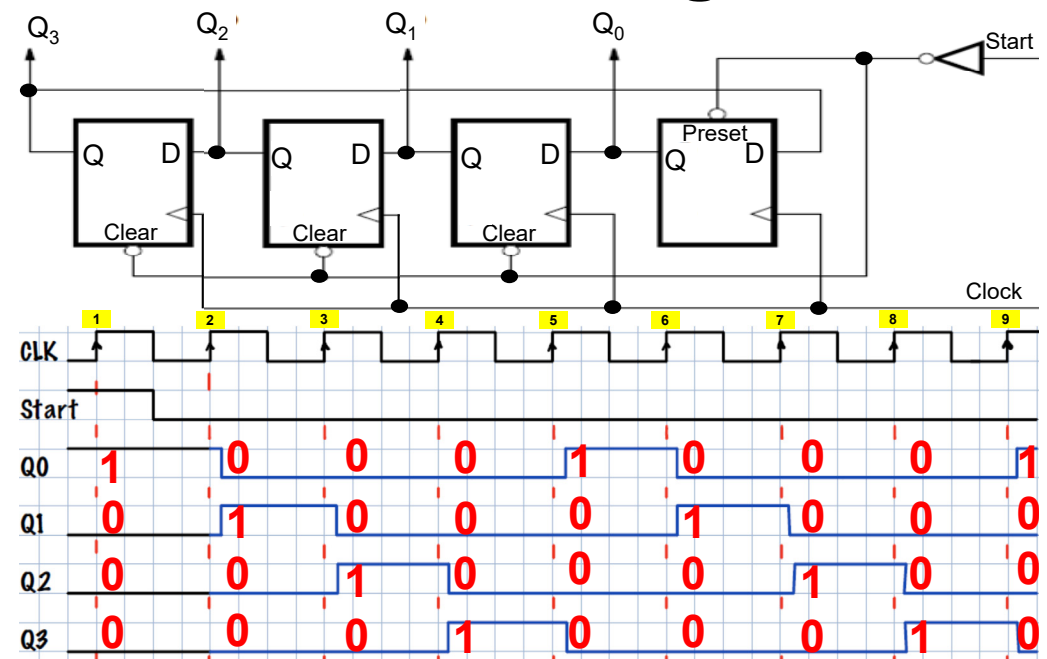

4-Bit Shift Left Ring Counter

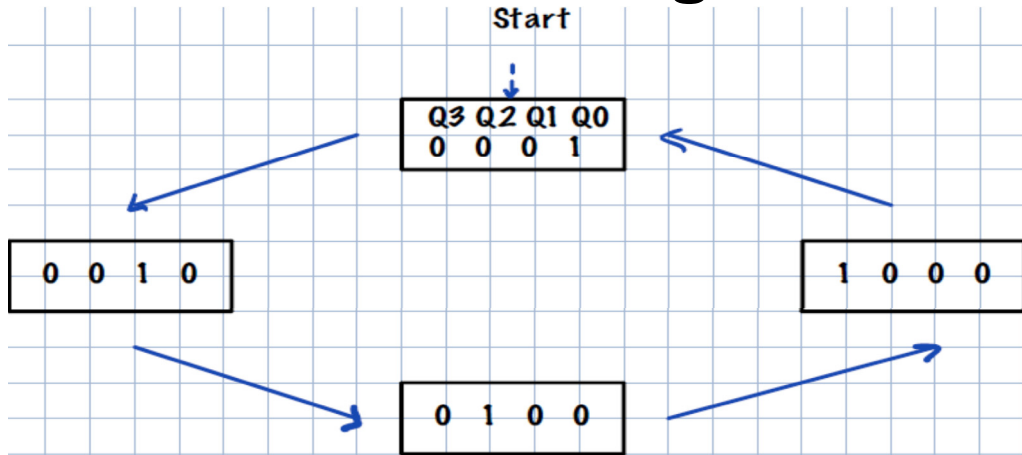

This is the normal mode of counting. In the normal mode, states are one-hot.

What is the total number of states? 16

What will happen if we enter a state which is not given above?

4-Bit Ring Counter State Table

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	d	d	d	d
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	d	d	d	d
0	1	0	0	1	0	0	0
0	1	0	1	d	d	d	d
0	1	1	0	d	d	d	d
0	1	1	1	d	d	d	d
1	0	0	0	0	0	0	1
1	0	0	1	d	d	d	d
1	0	1	0	d	d	d	d
1	0	1	1	d	d	d	d
1	1	0	0	d	d	d	d
1	1	0	1	d	d	d	d
1	1	1	0	d	d	d	d
1	1	1	1	d	d	d	d

□ Counter

without self correction:

assume the counter will always go through the valid states.

Invalid states are don't care

□ 0001 → 0010 → 0100 → 1000 → 0001...

4-Bit Shift Left Ring Counter Maps

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	d	0	d	0
	01	1	d	d	d
	11	d	d	d	d
	10	0	d	d	d

$$Y_3 = y_2$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	d	1	d	0
	01	0	d	d	d
	11	d	d	d	d
	10	0	d	d	d

$$Y_1 = y_0$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	d	0	d	1
	01	0	d	d	d
	11	d	d	d	d
	10	0	d	d	d

$$Y_2 = y_1$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	d	0	d	0
	01	0	d	d	d
	11	d	d	d	d
	10	1	d	d	d

$$Y_0 = y_3$$

4-Bit Ring Counter State Table


Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	0
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	1	1
1	0	1	0	0	1	0	1
1	0	1	1	0	1	1	1
1	1	0	0	1	0	0	1
1	1	0	1	1	0	1	1
1	1	1	0	1	1	0	1
1	1	1	1	1	1	1	1

□ The state table after the don't care outputs are assigned values for logic minimization for the ring counter without error correction

□ 0001 → 0010 → 0100 → 1000 → 0001...

Shift Left Ring Counter Invalid Modes

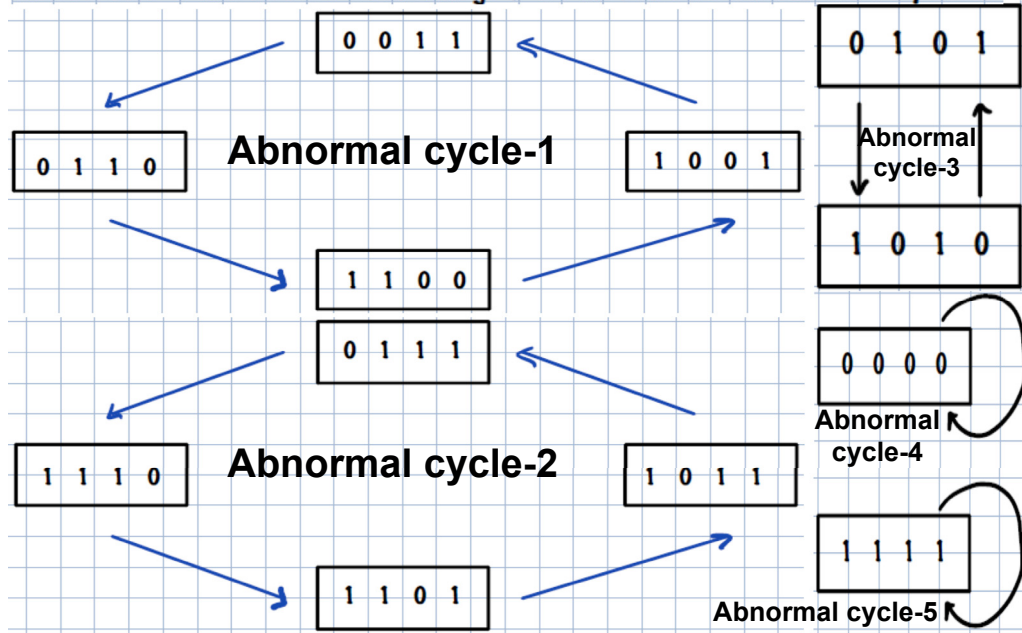There are 6 modes of counting. 5 of them are abnormal cycles.




EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

Self Correcting Ring Counter Cycles

Corrects abnormal state (moves to a valid state)

after at most 3 active clock edges

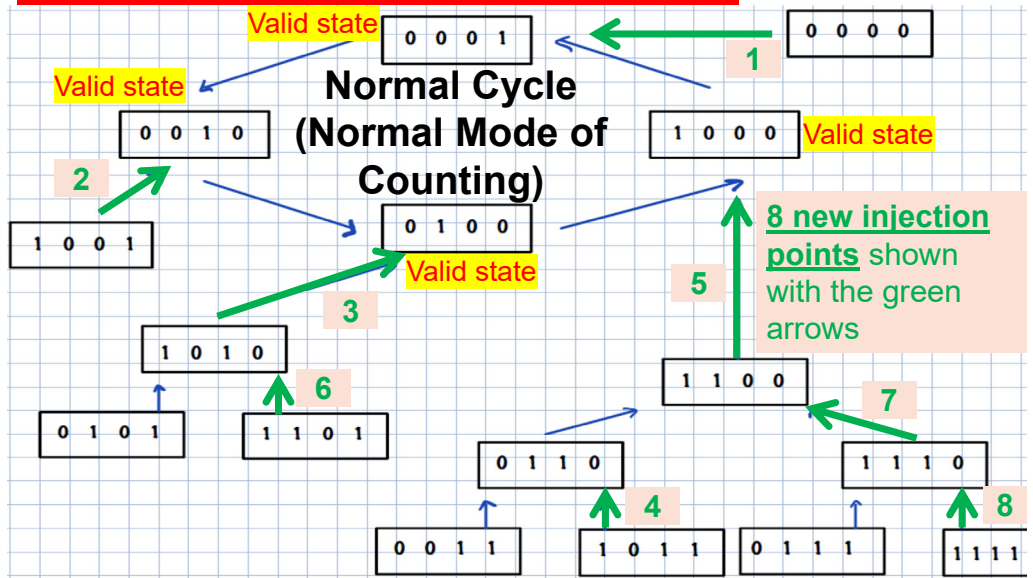

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

Ring Counter State Table Without Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	0
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	1	1
1	0	1	0	0	1	0	1
1	0	1	1	0	1	1	1
1	1	0	0	1	0	0	1
1	1	0	1	1	0	1	1
1	1	1	0	1	1	0	1
1	1	1	1	1	1	1	1

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

- Injection point-1: Invalid state 0000
 - Without error correction, the next state is 0000
- Injection point-2: Invalid state 1001
 - Without error correction, the next state is 0011
- Injection point-3: Invalid state 1010
 - Without error correction, the next state is 0101
- Injection point-4: Invalid state 1011
 - Without error correction, the next state is 0111

Ring Counter State Table Without Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	0
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	1	1
1	0	1	0	0	1	0	1
1	0	1	1	0	1	1	1
1	1	0	0	1	0	0	1
1	1	0	1	1	0	1	1
1	1	1	0	1	1	0	1
1	1	1	1	1	1	1	1

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

- Injection point-5: Invalid state 1100
 - Without error correction, the next state is 1001
- Injection point-6: Invalid state 1101
 - Without error correction, the next state is 1011
- Injection point-7: Invalid state 1110
 - Without error correction, the next state is 1101
- Injection point-8: Invalid state 1111
 - Without error correction, the next state is 1111

VOLKAN KURSUN Bilkent University

Self Correcting Ring Counter State Table

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
1	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	0
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1
2	1	0	0	1	0	0	1
3	1	0	1	0	1	0	0
4	1	0	1	1	1	1	0
1	1	0	0	1	0	0	1
1	1	0	1	1	0	1	1
1	1	1	0	1	1	0	1
1	1	1	1	1	1	1	1

EEE 102 Introduction to Digital Circuit Design

- Injection point-1:
Invalid state 0000
 - For error correction, the next state is 0001
- Injection point-2:
Invalid state 1001
 - For error correction, the next state is 0010
- Injection point-3:
Invalid state 1010
 - For error correction, the next state is 0100
- Injection point-4:
Invalid state 1011
 - For error correction, the next state is 0110

VOLKAN KURSUN

VOLKAN KURSUN Bilkent University

Self Correcting Ring Counter State Table

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	0
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0
5	1	1	0	0	1	0	0
6	1	1	0	1	0	1	0
7	1	1	1	0	1	1	0
8	1	1	1	1	1	1	0

EEE 102 Introduction to Digital Circuit Design

- Injection point-5:
Invalid state 1100
 - For error correction, the next state is 1000
- Injection point-6:
Invalid state 1101
 - For error correction, the next state is 1010
- Injection point-7:
Invalid state 1110
 - For error correction, the next state is 1100
- Injection point-8:
Invalid state 1111
 - For error correction, the next state is 1110

VOLKAN KURSUN

VOLKAN KURSUN Bilkent University

Error Correcting Ring Counter Maps

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$Y_3 = y_2$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	1	1	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	1	1	0

$$Y_1 = y_0$$

EEE 102 Introduction to Digital Circuit Design

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	1	1
	01	0	0	1	1
	11	0	0	1	1
	10	0	0	1	1

$$Y_2 = y_1$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	1	0	0	0
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	0	0

$$Y_0 = y_2'y_1'y_0' = (y_2 + y_1 + y_0)'$$

VOLKAN KURSUN

VOLKAN KURSUN Bilkent University

Self Correcting Ring Counter

1000 → 0001 → 0010 → 0100 → 1000 → 0001...

- $Q_{N-2} = Q_{N-3} = \dots = Q_1 = Q_0 = 0$ is the only legitimate state after which a 1 should be injected into Q_0
- From all other states, including the erroneous states, 0 should be injected into Q_0 to be able to return to the normal cycles
- To construct an n-bit self correcting ring counter: $D_0 = (Q_{n-2} + Q_{n-3} + \dots + Q_1 + Q_0)'$

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

Self Correcting Ring Counter

1000 → 0001 → 0010 → 0100 → 1000 → 0001 ...

□ Assume an abnormal state with n bits:

X111...1111 ¹→ 1111...1110 ²→ 1111...1100

³→ 1111...1000 ⁴→ ... ⁿ⁻²→ 1100...0000

ⁿ⁻¹→ 1000...0000 ⁿ→ 0000...0001

→ 0000...0010 → ...

□ To construct an n-bit self correcting ring counter:


$$D_0 = (Q_{n-2} + Q_{n-3} + \dots + Q_1 + Q_0)'$$

NOR function of all the bits (all state variables) except the MSB

$D_0 = 1$, iff $Q_0 = Q_1 = \dots = Q_{n-2} = 0$

$D_0 = 0$, for all other states → **corrects an abnormal state in at most n-1 clock cycles**

Self Correcting 4-Bit Ring Counter

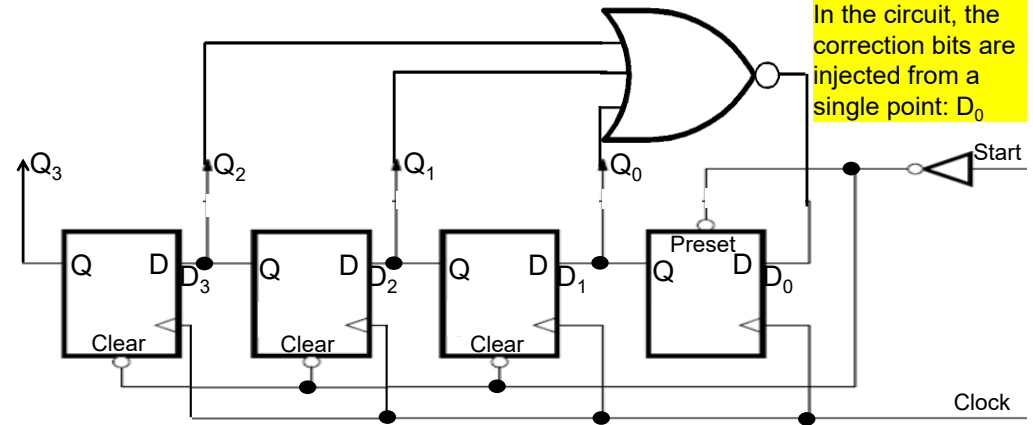

□ To construct an n-bit self correcting ring counter:

$$D_0 = (Q_2 + Q_1 + Q_0)'$$

NOR function of all the bits (all state variables) except the MSB

$D_0 = 1$ iff $Q_2 = Q_1 = Q_0 = 0$ (corrects an abnormal state in at most 3 clock cycles)

Ring Counter State Table for Single Cycle Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	0	1	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	0
0	1	1	1	1	0	0	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	0	1
1	0	1	0	0	0	1	0
1	0	1	1	0	0	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

□ **For fastest recovery**, design a circuit that can **recover from any invalid state in only one clock cycle**

□ **All the invalid states must transition to a valid state in the next clock cycle** for one cycle recovery

□ **More complex circuit needed**: logic expressions for Y_2 , Y_1 , and Y_0 change


□ No change in Y_3 :
 $Y_3 = y_2$

Outline

- Counter Design as FSM
- A Different Counter
- Self Correcting Ring Counter
- Self Correcting Johnson Counter


Shift Left Johnson Counter

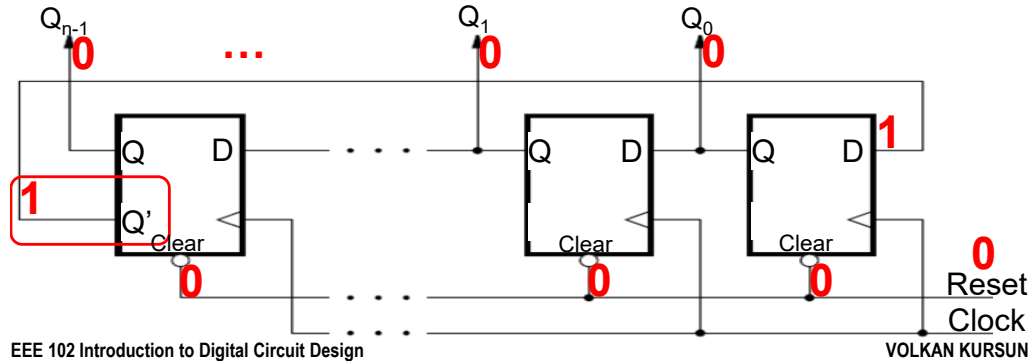- Instead of the Q output of the final stage as in a ring counter, connect the Q' output of the final stage to the D input of the first stage flip-flop in a Johnson counter (AKA twisted ring, switched tail)
- First initialize with Reset = 0 (clear all bit positions to 0): $Q_{n-1}Q_{n-2}\dots Q_1Q_0 = 0b00\dots00$




Shift Left Johnson Counter

- When Reset = 1, counter starts counting with the positive edges of the clock signal
- n-bit Johnson counter (shift left with Q_{n-1}' (MSB complement) injected to LSB from right):
 $00\dots00 \xrightarrow{1} 00\dots01 \xrightarrow{2} 00\dots11 \rightarrow \dots \rightarrow 01\dots11 \xrightarrow{n} 11\dots11 \rightarrow 11\dots10 \rightarrow 11\dots00 \rightarrow \dots \rightarrow 10\dots00 \xrightarrow{2n} 00\dots00 \rightarrow 00\dots01 \rightarrow \dots$

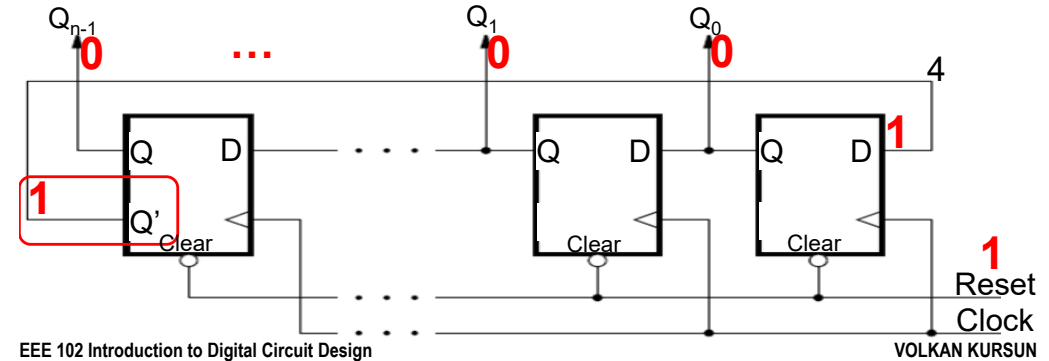


4-Bit Shift Left Johnson Counter

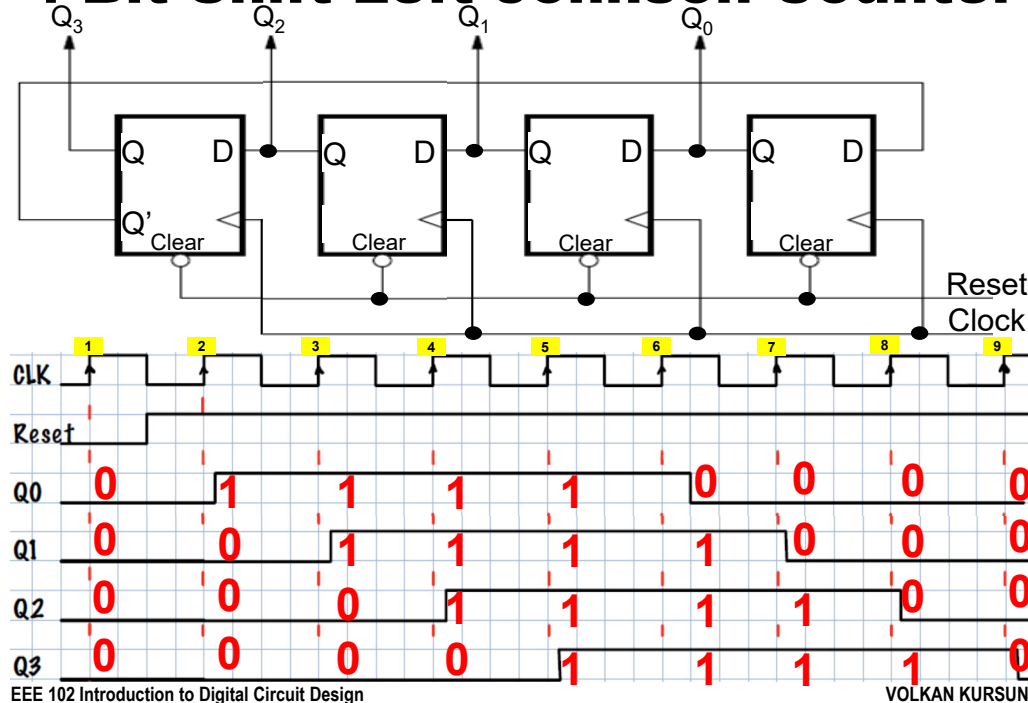

Johnson Counter States

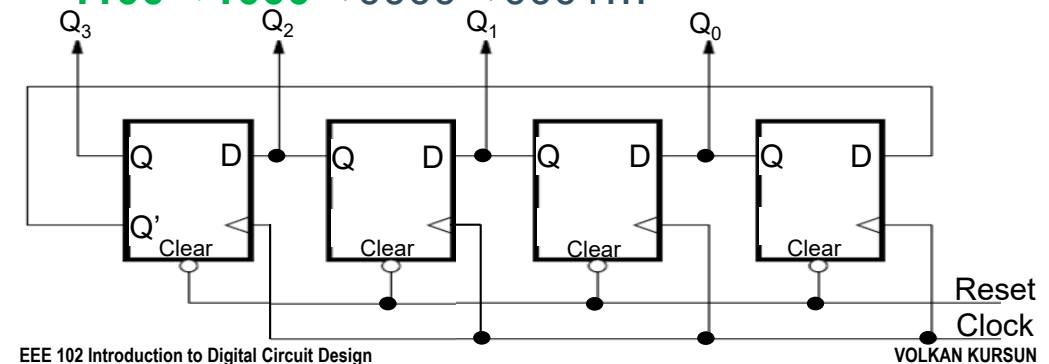- An n-bit Johnson counter goes through $2n$ valid states
- There are $2^n - 2n$ invalid states
- Example: 4-bit Johnson counter goes through 8 valid states. There are also 8 invalid states.
- $0000 \rightarrow 0001 \rightarrow 0011 \rightarrow 0111 \rightarrow 1111 \rightarrow 1110 \rightarrow 1100 \rightarrow 1000 \rightarrow 0000 \rightarrow 0001 \dots$



4-Bit Johnson Counter State Table

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	d	d	d	d
0	0	1	1	0	1	1	1
0	1	0	0	d	d	d	d
0	1	0	1	d	d	d	d
0	1	1	0	d	d	d	d
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	d	d	d	d
1	0	1	0	d	d	d	d
1	0	1	1	d	d	d	d
1	1	0	0	1	0	0	0
1	1	0	1	d	d	d	d
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

□ Counter without
self correction:

assume the
counter will
always go
through the
valid states.

Invalid states
are don't care

□ 0000 → 0001 → 0
011 → 0111 → 11
11 → 1110 →
1100 → 1000 → 0
000 → 0001...

4-Bit Johnson Counter Maps

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	0	d
	01	d	d	1	d
	11	1	d	1	1
	10	0	d	d	d

$$Y_3 = y_2$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	1	1	d
	01	d	d	1	d
	11	0	d	1	0
	10	0	d	d	d

$$Y_1 = y_0$$

EEE 102 Introduction to Digital Circuit Design

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	1	d
	01	d	d	1	d
	11	0	d	1	1
	10	0	d	d	d

$$Y_2 = y_1$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	1	1	1	d
	01	d	d	1	d
	11	0	d	0	0
	10	0	d	d	d

$$Y_0 = y_3'$$

VOLKAN KURSUN

4-Bit Johnson Counter State Table

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

EEE 102 Introduction to Digital Circuit Design


VOLKAN KURSUN

□ After the
assignments
of the don't
cares for the
next state
logic
minimization,
the state table
looks like this

□ 0000 → 0001 → 0
011 → 0111 → 11
11 → 1110 →
1100 → 1000 → 0
000 → 0001...

Johnson Counter Cycles

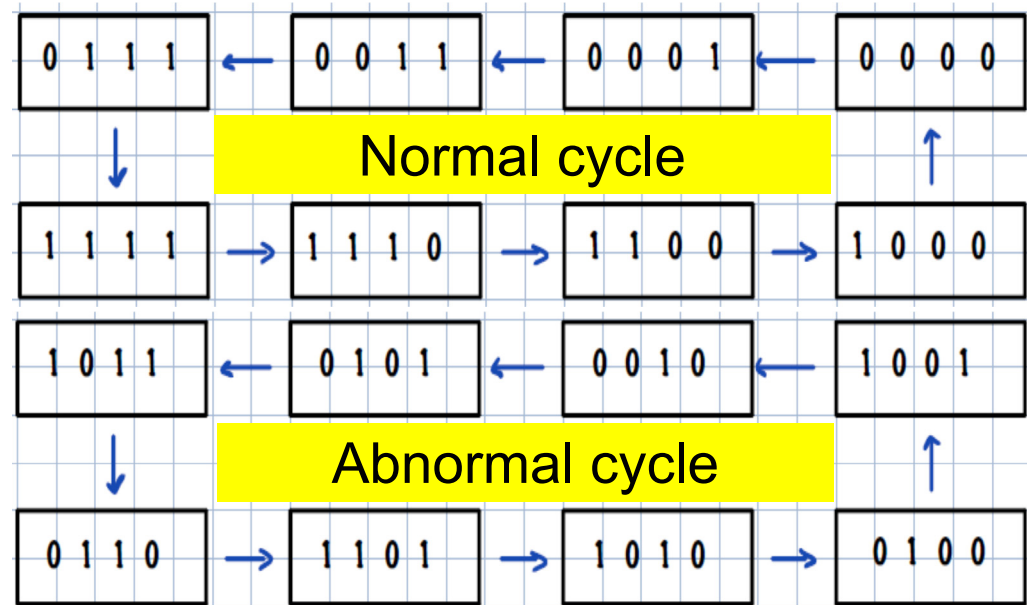□ Original design without error correction capability




EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN


Error Correcting Johnson Counter Design

 - To design a self-correcting Johnson counter, examine the existing Karnaugh maps of the original design and identify don't care conditions that can be changed to recover from erroneous states with the minimum hardware overhead




Error Correcting Johnson Counter

 - With single injection point: worst case latency for error correction is 8 cycles



Error Correcting Johnson Counter Design-1

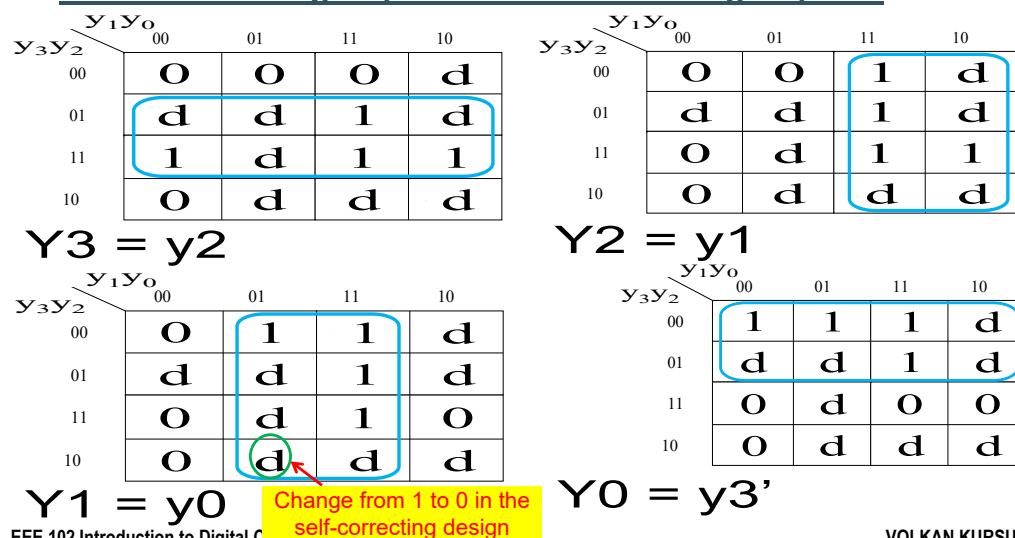- In design-1, we will explore having only one injection point
- Replace the highlighted don't care condition for Y1 from 1 to 0 to recover from erroneous state with minimum hardware overhead
- Form three new groups of 4 instead of one group of 8



Original State Table Without Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

- Single injection point: Invalid state 1001**

- Without error correction, the next state is **0010**

Modified State Table-1 for Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

Single injection point: Invalid state 1001

With error correction, the next state is 0000

Error Correcting Johnson Counter-1 Maps

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$Y_3 = y_2$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	1	1	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	0	1	0

$$Y_1 = y_3'y_0 + y_2y_0 + y_1y_0$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	1	1
	01	0	0	1	1
	11	0	0	1	1
	10	0	0	1	1


$$Y_2 = y_1$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	1	1	1	1
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$$Y_0 = y_3'$$

Self Correcting Johnson Counter Design-2

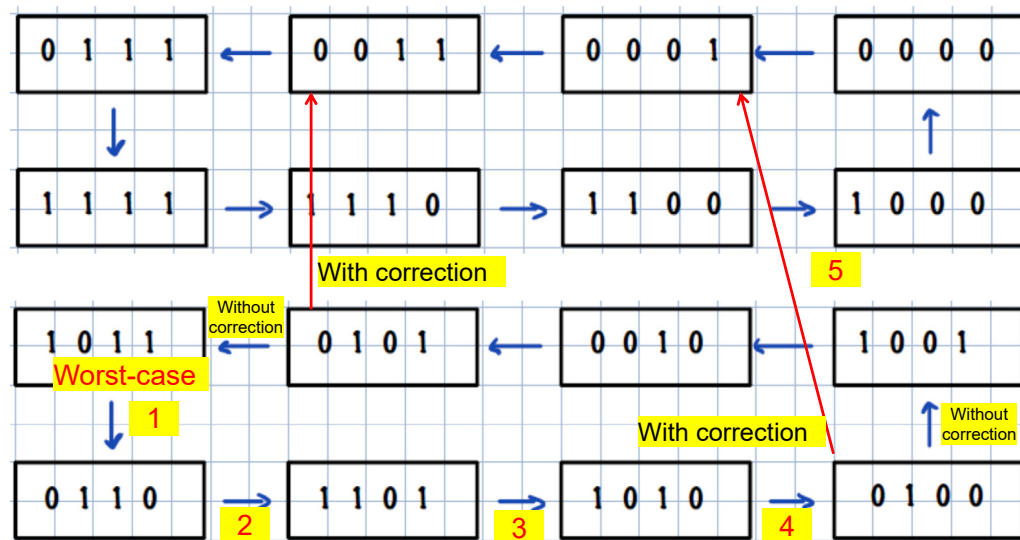- Multiple injection points reduce the latency for correction
- Two injection points for error correction: worst case latency for correction is reduced to 5 cycles



Error Correcting Johnson Counter Design-2

- In design option-2, we will replace the highlighted don't care conditions for Y3 from 1 to 0 to recover from erroneous states with minimum hardware overhead
- Form two new groups of 4 instead of one group of 8

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	0	d
	01	d	d	1	d
	11	1	d	1	1
	10	0	d	d	d

$$Y_3 = y_2$$

Change from 1 to 0 in the self-correcting design

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	1	1	d
	01	d	d	1	d
	11	0	d	1	0
	10	0	d	d	d

$$Y_1 = y_0$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	1	d
	01	d	d	1	d
	11	0	d	1	1
	10	0	d	d	d

$$Y_2 = y_1$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	1	1	1	d
	01	d	d	1	d
	11	0	d	0	0
	10	0	d	d	d

$$Y_0 = y_3'$$

State Table Without Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

□ **Injection point-1: Invalid state 0100**

▪ Without error correction, the next state is **1001**

□ **Injection point-2: Invalid state 0101**

▪ Without error correction, the next state is **1011**

Design-2 for Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
1	0	0	0	0	0	0	1
2	0	1	0	0	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

□ **Injection point-1: Invalid state 0100**

▪ **With error correction**, the next state is **0001**

□ **Injection point-2: Invalid state 0101**

▪ **With error correction**, the next state is **0011**

□ Y_3 logic function changes

□ Y_2 , Y_1 , and Y_0 do NOT change

Error Correcting Design-2 Maps

		y_1y_0			
		00	01	11	10
y_3y_2	00	0	0	0	0
	01	0	0	1	1
	11	1	1	1	1
	10	0	0	0	0

$$Y_3 = y_3y_2 + y_2y_1 = y_2(y_3 + y_1)$$

		y_1y_0			
		00	01	11	10
y_3y_2	00	0	1	1	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	1	1	0

$$Y_1 = y_0$$

EEE 102 Introduction to Digital Circuit Design

		y_1y_0			
		00	01	11	10
y_3y_2	00	0	0	1	1
	01	0	0	1	1
	11	0	0	1	1
	10	0	0	1	1

$$Y_2 = y_1$$

		y_1y_0			
		00	01	11	10
y_3y_2	00	1	1	1	1
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$$Y_0 = y_3'$$

VOLKAN KURSUN

Error Correcting Johnson Counter Design-3

□ In design option-3, we will replace the highlighted don't care conditions for Y_2 from 1 to 0 to recover from erroneous states with minimum hardware overhead

□ **Form two new groups of 4 instead of one group of 8**

		y_1y_0			
		00	01	11	10
y_3y_2	00	0	0	0	d
	01	d	d	1	d
	11	1	d	1	1
	10	0	d	d	d

$$Y_3 = y_2$$

		y_1y_0			
		00	01	11	10
y_3y_2	00	0	1	1	d
	01	d	d	1	d
	11	0	d	1	0
	10	0	d	d	d

$$Y_1 = y_0$$

EEE 102 Introduction to Digital Circuit Design

		y_1y_0			
		00	01	11	10
y_3y_2	00	0	0	1	d
	01	d	d	1	d
	11	0	d	1	1
	10	0	d	d	d

$$Y_2 = y_1$$

		y_1y_0			
		00	01	11	10
y_3y_2	00	1	1	1	d
	01	d	d	1	d
	11	0	d	0	0
	10	0	d	d	d


$$Y_0 = y_3'$$

Change from 1 to 0 in the self-correcting design


VOLKAN KURSUN

4-Bit Johnson Counter State Diagram

 - Two injection points for error correction lower the latency for correction: maximum 5 cycles to a valid state



 Note: Only a single bit changes its value during successive clock ticks. 8 states used in normal operation. 8 states unused.



4-Bit Johnson Counter State Table

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

- Injection point-1: Invalid state 0010

- Without error correction, the next state is 0101

- Injection point-2: Invalid state 1010

- Without error correction, the next state is 0100

Modified State Table for Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
1	0	0	0	0	0	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
2	1	0	1	0	0	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

- Injection point-1: Invalid state 0010

- With error correction, the next state is 0001

- Injection point-2: Invalid state 1010

- With error correction, the next state is 0000

- Y₂ logic function changes

- Y₃, Y₁, and Y₀ do NOT change

Error Correcting Johnson Counter-3 Maps

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$Y_3 = y_2$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	1	1	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	1	1	0

$$Y_1 = y_0$$

		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	0	0	1	0
	01	0	0	1	1
	11	0	0	1	1
	10	0	0	1	0

$$Y_2 = y_2y_1 + y_1y_0 = y_1(y_2 + y_0)$$


		y ₁ y ₀			
		00	01	11	10
y ₃ y ₂	00	1	1	1	1
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$$Y_0 = y_3'$$

Self Correcting Johnson Counter-3

$$Y_3 = y_2 \quad Y_2 = y_2 y_1 + y_1 y_0 = y_1 (y_2 + y_0)$$

$$Y_1 = y_0 \quad Y_0 = y_3'$$

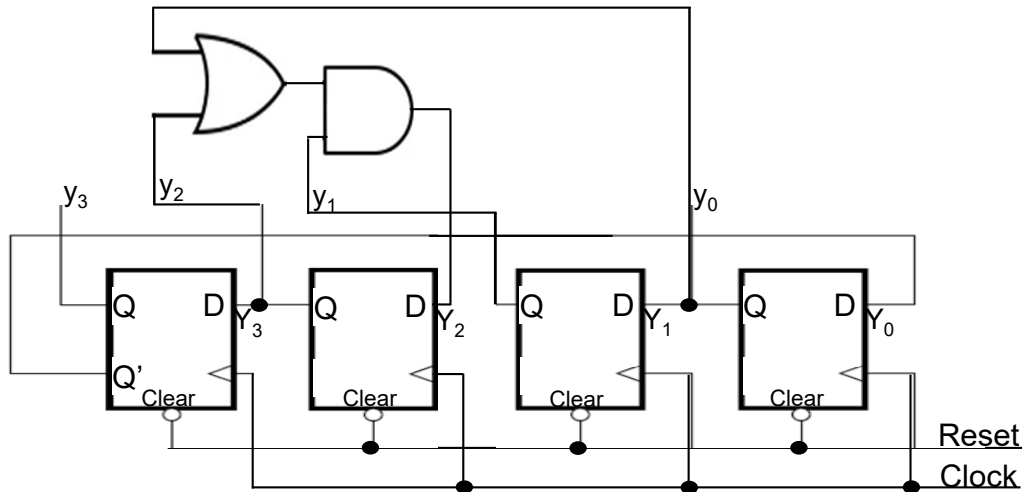

Error Correcting Johnson Counter Design-4

- In design option-4, we will replace the highlighted don't care conditions for Y1 from 1 to 0 to recover from erroneous states with minimum hardware overhead
- Form two new groups of 4 instead of one group of 8

$y_1 y_0$	00	01	11	10
$y_3 y_2$ 00	0	0	0	d
01	d	d	1	d
11	1	d	1	1
10	0	d	d	d

$$Y_3 = y_2$$

$y_1 y_0$	00	01	11	10
$y_3 y_2$ 00	0	1	1	d
01	d	d	1	d
11	0	d	1	0
10	0	d	d	d

$$Y_1 = y_0$$

Change from 1 to 0 in the self-correcting design

$y_1 y_0$	00	01	11	10
$y_3 y_2$ 00	0	0	1	d
01	d	d	1	d
11	0	d	1	1
10	0	d	d	d


$$Y_2 = y_1$$

$y_1 y_0$	00	01	11	10
$y_3 y_2$ 00	1	1	1	d
01	d	d	1	d
11	0	d	0	0
10	0	d	d	d


$$Y_0 = y_3'$$

Self Correcting Johnson Counter Alternative Design-4

 - Two injection points for error correction lower the latency for correction: maximum 5 cycles to a valid state



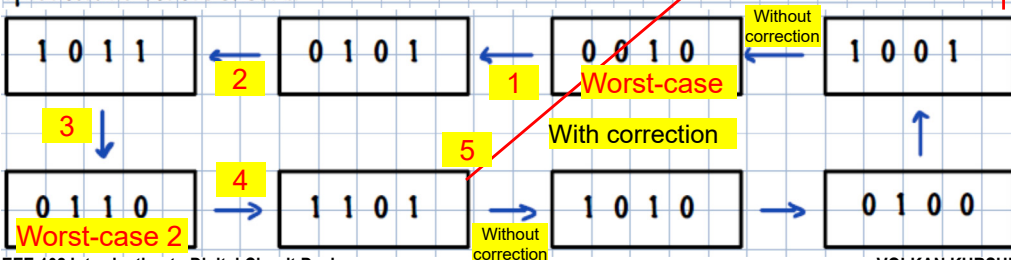Note: Only a single bit changes its value during successive clock ticks. 8 states used in normal operation. 8 states unused.



State Table Without Correction

Present State				Next State			
y_3	y_2	y_1	y_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

- Injection point-1: Invalid state 1001

Without error correction, the next state is 0010

- Injection point-2: Invalid state 1101

Without error correction, the next state is 1010

Design-4 for Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	1
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	1	0	0	1	0	0	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

❑ **Injection point-1:**
Invalid state 1001

▪ **With error correction,** the next state is **0000**

❑ **Injection point-2:**
Invalid state 1101

▪ **With error correction,** the next state is **1000**

❑ Y_1 logic function changes

❑ $Y_3, Y_2,$ and Y_0 do NOT change

Error Correcting Design-4 Maps

		$y_1 y_0$			
		00	01	11	10
$y_3 y_2$	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$Y_3 = y_2$$

		$y_1 y_0$			
		00	01	11	10
$y_3 y_2$	00	0	1	1	0
	01	0	1	1	0
	11	0	0	1	0
	10	0	0	1	0

$$Y_1 = y_3' y_0 + y_1 y_0 = y_0 (y_3' + y_1)$$

EEE 102 Introduction to Digital Circuit Design

		$y_1 y_0$			
		00	01	11	10
$y_3 y_2$	00	0	0	1	1
	01	0	0	1	1
	11	0	0	1	1
	10	0	0	1	1

$$Y_2 = y_1$$

		$y_1 y_0$			
		00	01	11	10
$y_3 y_2$	00	1	1	1	1
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$$Y_0 = y_3'$$

VOLKAN KURSUN

Johnson Counter State Table for Single Cycle Error Correction

Present State				Next State			
y3	y2	y1	y0	Y3	Y2	Y1	Y0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	0	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	0
0	1	1	0	1	1	0	0
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	0

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

❑ Modified design that can **recover from any invalid state in one clock cycle**

❑ **All the invalid states must transition to a valid state in the next clock cycle**

❑ **More complex circuit needed for 1 cycle recovery**

❑ Y_2 and Y_0 logic expressions change

❑ No change in Y_3 :

$$Y_3 = y_2$$

❑ No change in Y_1 :

$$Y_1 = y_0$$