

EEE102
Sample Problems for Fall 2009
15-10-2009
KARNAUGH MAP MINIMIZATION


Q1.

Given the function $F(A,B,C,D) = \Sigma_{A,B,C,D} (1,4,5,8,10,13,14,15) + d(7,9)$.

- Find all minimal sums for F.
- Find all minimal products for F
- Which of the above minimal sums are equivalent to which of the above minimal products? Equivalent means having the same Truth Table.

Solution:

a)

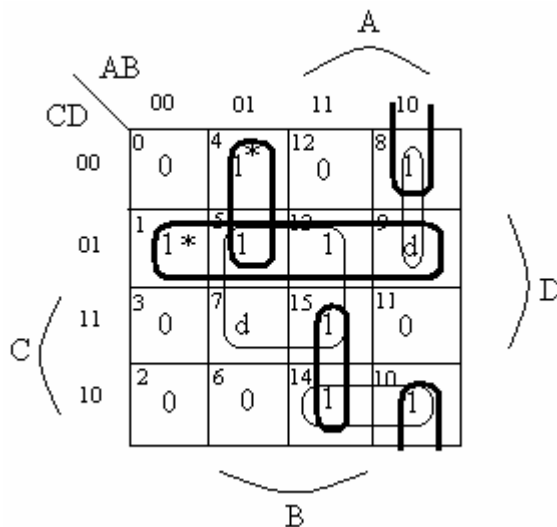


SOP1:

$$F = C'D + A'BC' + ABC + AB'D'$$

7 is zero

9 is one

b)

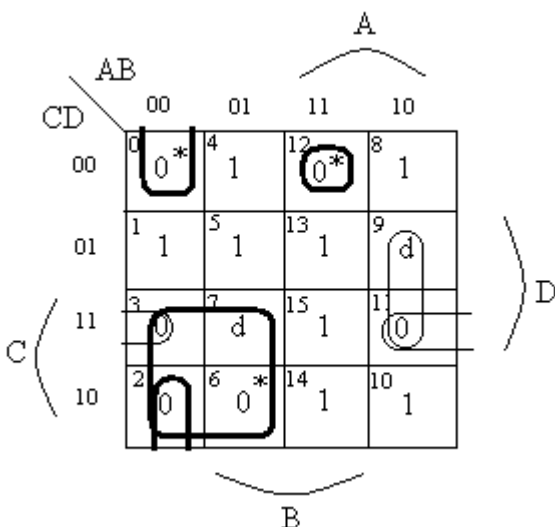

POS1:

F =

$$(A+B+D)(A+C')(A'+B'+C+D)(B+C'+D')$$

7 is zero

9 is one

POS2:

$$F = (A+B+D)(A+C')(A'+B'+C+D)(A'+B+D')$$

7 is zero

9 is zero

c) SOP1 is equivalent to POS1 because in each case 7 is zero, 9 is one.


Q2.

Find a minimal SOP expression for

$$F = \sum_{A,B,C,D} (0,1,2,3,4,5,7,14,15)$$

using a Karnaugh map. In so doing, clearly show the distinguished 1-cells and also draw the reduced map.

Solution:

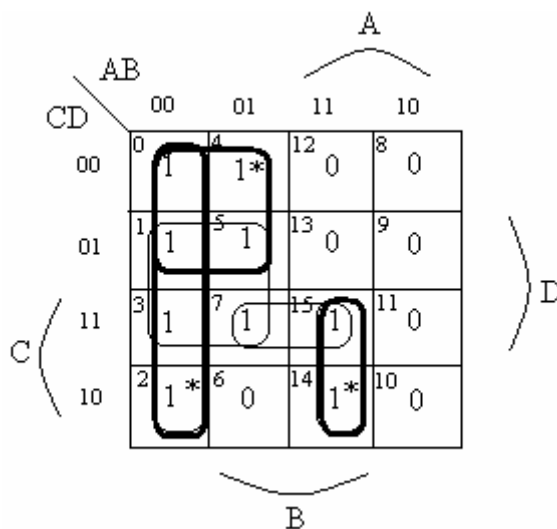

F:


Expression including essential prime implicants

$$A'C' + A'B' + ABC$$

Reduced Map:

minimal SOP:

$$F = A'C' + A'B' + ABC + A'D$$

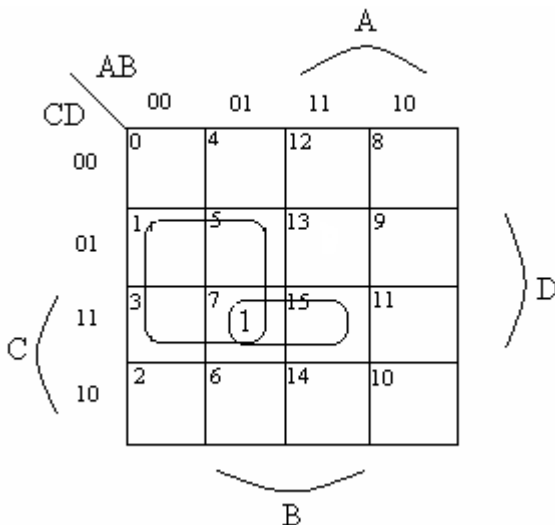


Q3.

Find all minimal SOPs for each of the following logic functions:

- a) $F = \Sigma_{W,X,Y,Z} (0,1,3,5,14) + d (8,15)$
- b) $F = \Sigma_{W,X,Y,Z} (2,5,13,15,10) + d (8,0,12)$
- c) $F = \Pi_{W,X,Y,Z} (4,5,6,7,10,12,13,14) + d (3,9,15)$
- d) $F = \Sigma_{W,X,Y,Z} (0,1,3,5,14) + d (8,12,15)$
- e) $F = \Sigma_{W,X,Y,Z} (0,2,4,6,8,10,12,14) + d (9,13)$
- f) $F = \Sigma_{W,X,Y,Z} (0,2,8,10) + d (5,13)$

Solution:

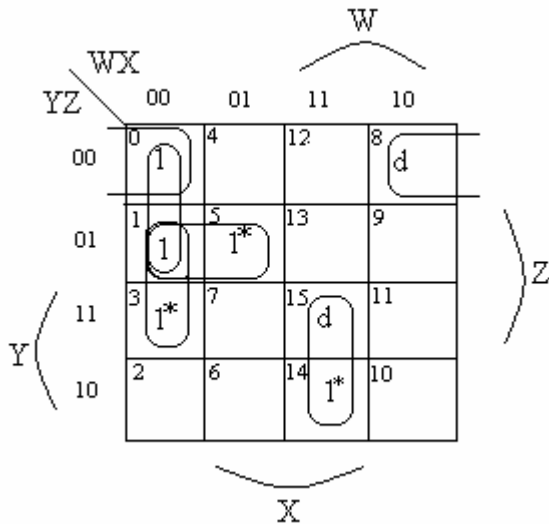a) $F = \Sigma_{W,X,Y,Z} (0,1,3,5,14) + d (8,15)$




$$F = W'Y'Z + W'X'Z + WXY + X'Y'Z'$$

or

$$F = W'Y'Z + W'X'Z + WXY + W'X'Y'$$

There are two minimal SOPs

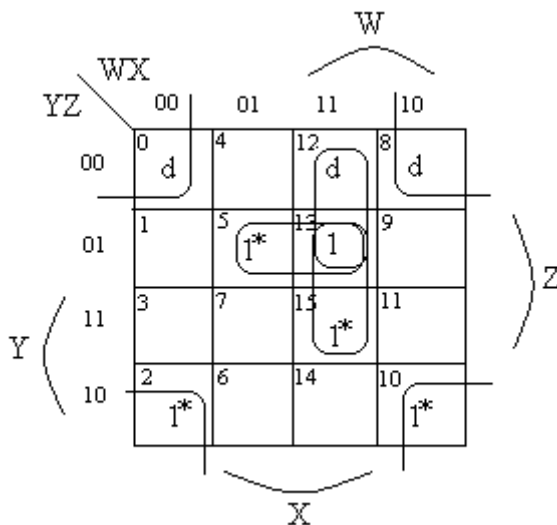
b) $F = \Sigma_{W,X,Y,Z} (2,5,13,15,10) + d (8,0,12)$



$$F = X'Z' + ZWX + XY'Z$$

There is only one minimal SOP

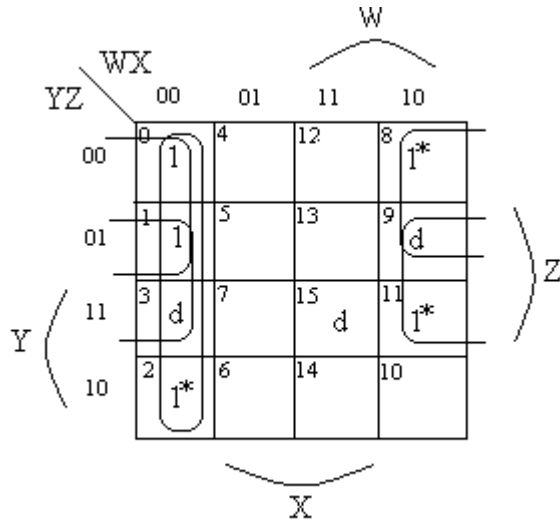
c) $F = \Pi_{W,X,Y,Z} (4,5,6,7,10,12,13,14) + d (3,9,15)$



$$F = W'X' + X'Y' + ZX'$$

There is only one minimal SOP

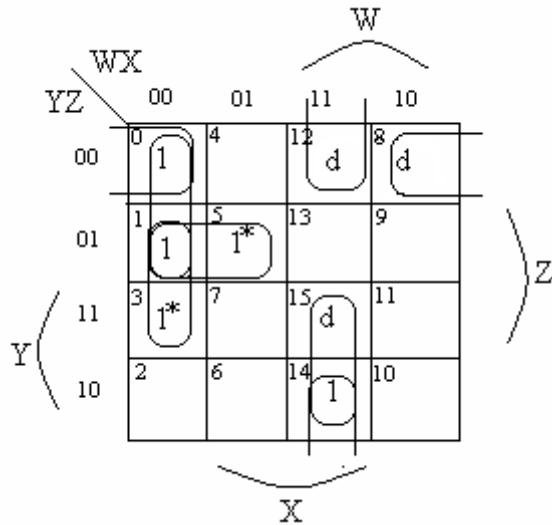d) $F = \Sigma_{W,X,Y,Z} (0,1,3,5,14) + d (8,12,15)$



$$F_1 = W'Y'Z + W'X'Z + W'X'Y' + YWX$$


$$F_2 = W'Y'Z + W'X'Z + W'X'Y' + WXZ'$$

$$F_3 = W'Y'Z + W'X'Z + X'Y'Z' + YWX$$

$$F_4 = W'Y'Z + W'X'Z + X'Y'Z' + WXZ'$$


There are 4 minimal SOPs

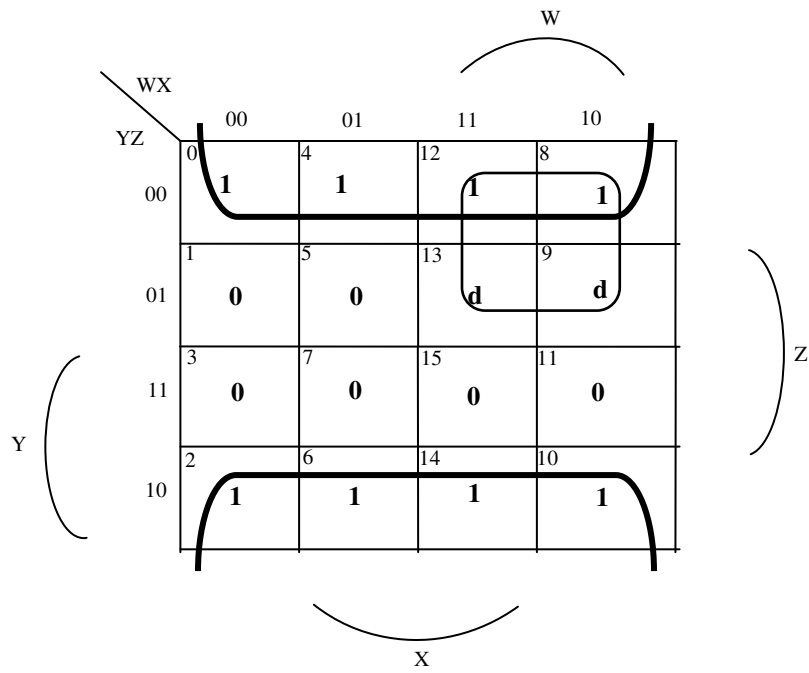e) $F = \Sigma_{W,X,Y,Z} (0,2,4,6,8,10,12,14) + d (9,13)$



$F = Z'$ There is only one minimal SOP

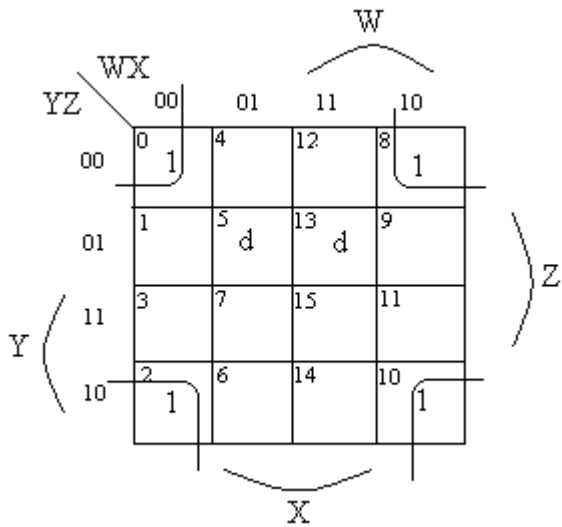f) $F = \Sigma_{W,X,Y,Z} (0,2,8,10) + d (5,13)$



$F = X'Z'$

There is only one minimal SOP

Q4.


Find the lowest cost two-level realization for

$$F = \sum_{A,B,C,D} (0,4,6,8,9) + d(10,11,12,13,14,15).$$

Solution:


First let us find a minimal SOP expression

$$F_{SOP} = A + C'D' + BD'$$

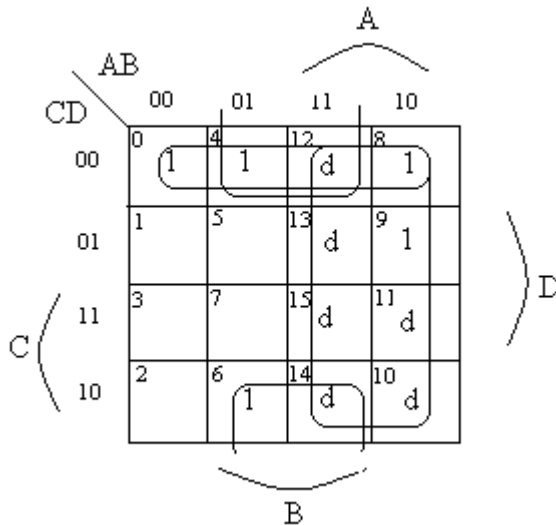

Second let us find a minimal POS expression

$$F_{POS} = (A + D')(B + C')$$

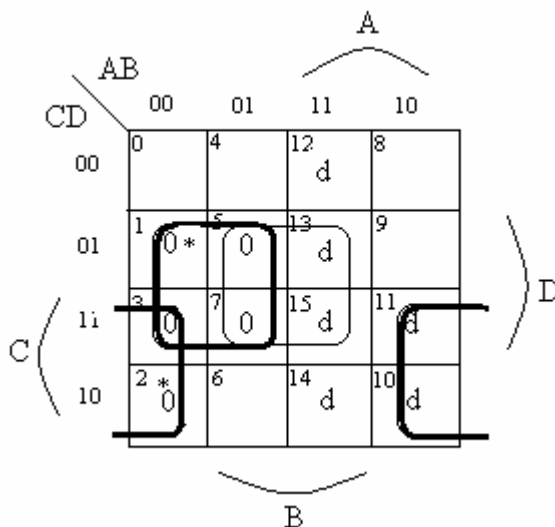

F_{SOP} has 3 terms

F_{POS} has 2 terms


Therefore F_{POS} is of lowest cost.

Q5.

Solve exercise 4.58 from Wakerly 4th Edition


Solution:

a) $F = X'Z + XY + XY'Z$

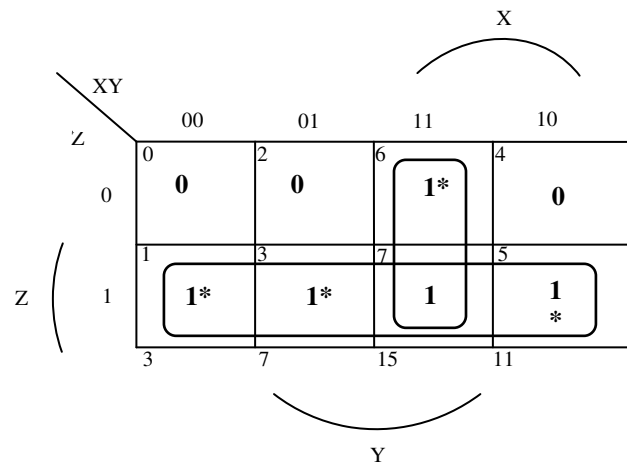


$F = Z + XY$

b) $F = A'C'D + B'CD + AC'D + BCD$

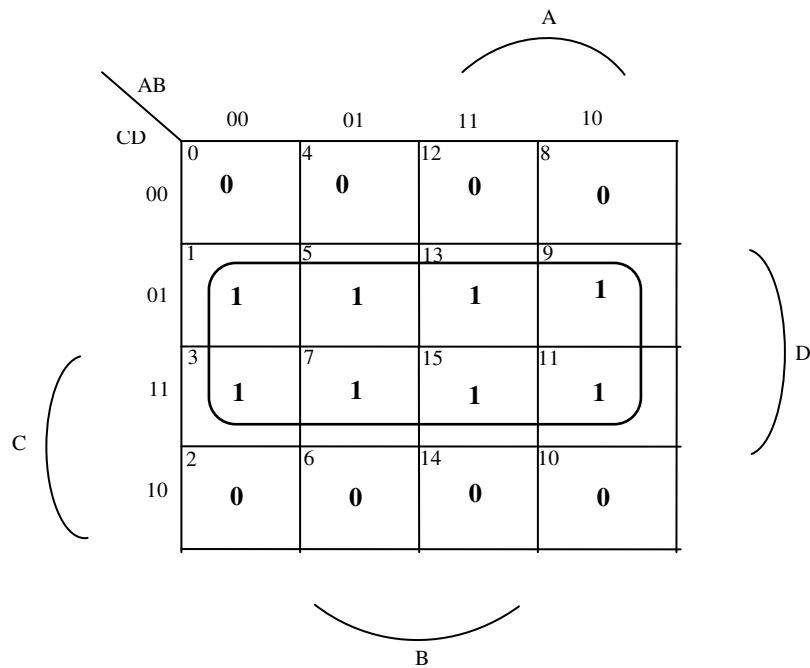


$F = D$


c) $F = W'XZ' + WXYZ + W'Z$

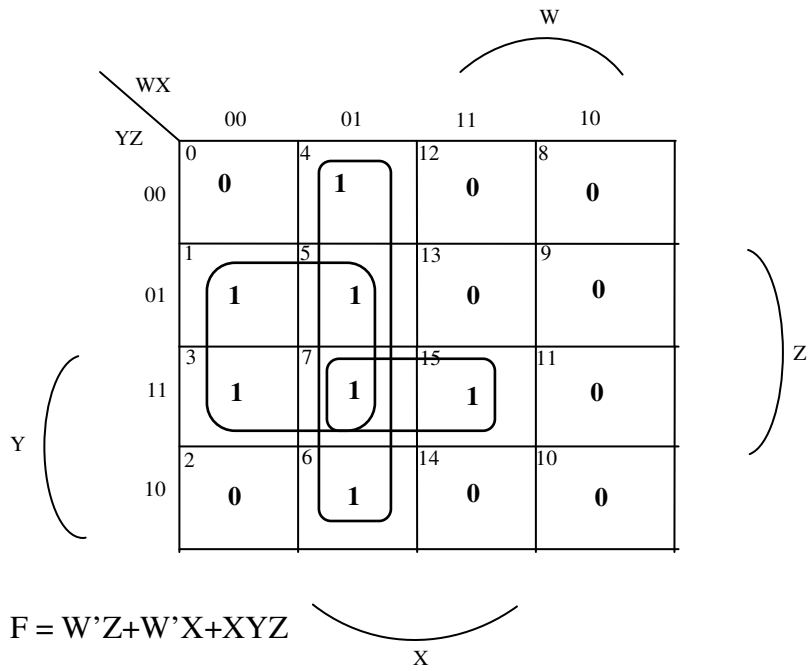

d) $F = (W+Z')(W'+Y'+Z')(X+Y'+Z)$

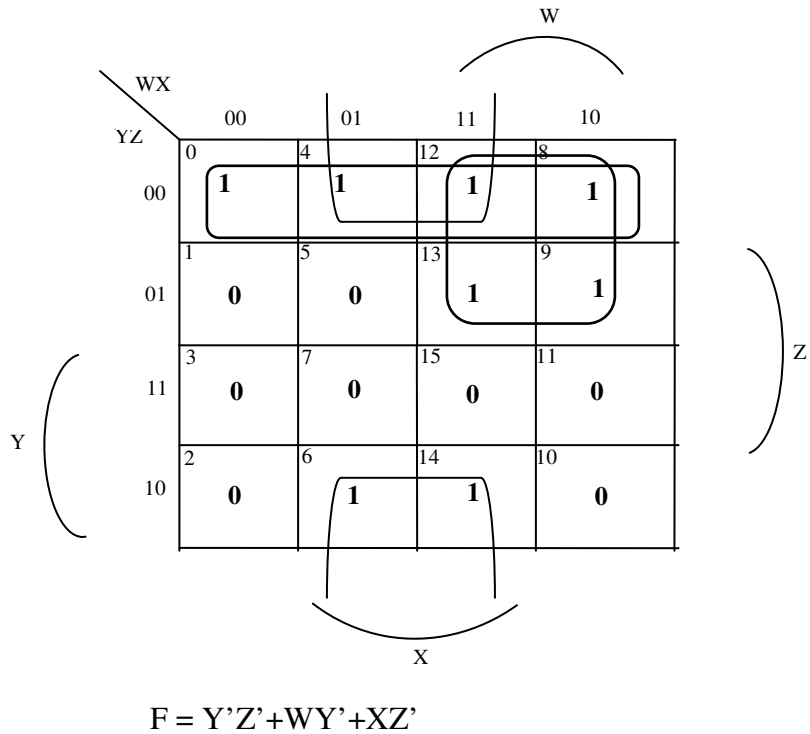

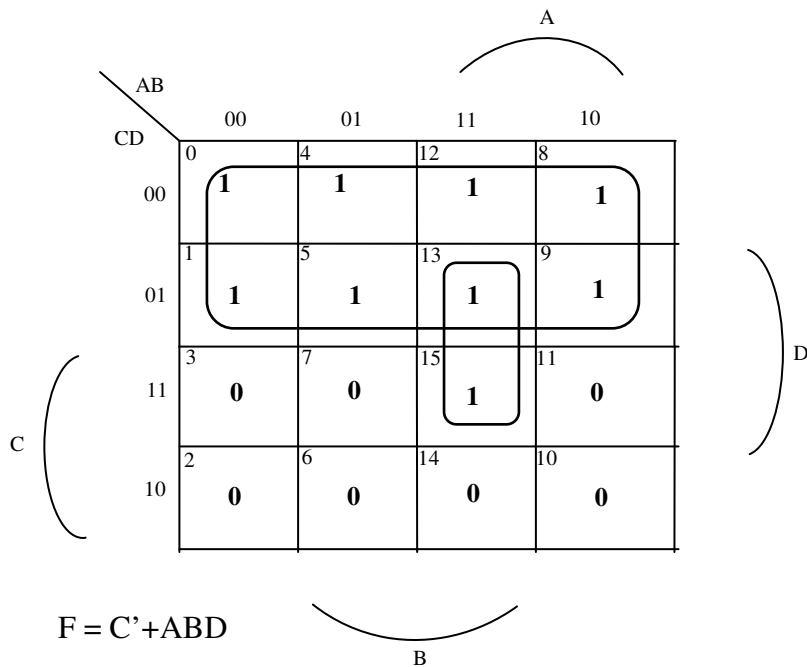e) $F = A'B'C'D' + A'C'D + BC'D' + ABD + AB'C'$



Q6.

Use the Karnaugh Map method to answer the following questions for the function

$$F = A'B'C'D' + A'BC'D' + ABC'D' + AB'C'D' + A'B'C'D + A'BC'D + AB'CD + ABCD' + AB'CD'$$

- Draw the Karnaugh map for F
- Find a minimal SOP expressions for F.
- Find a minimal POS expressions for F.
- Which of the above found expressions would you use for implementation. Why?

Solution:

a)

		A			
		00	01	11	10
CD	AB				
	00	0 1	4 1	12 1	8 1
	01	1 1	5 1	13 0	9 0
	11	3 0	7 0	15 0	11 1
	10	2 0	6 0	14 1	10 1

B

C

D

b)

		A			
		00	01	11	10
CD	AB				
	00	0 1	4 1	12 1	8 1
	01	1 1	5 1	13 0	9 0
	11	3 0	7 0	15 0	11 1
	10	2 0	6 0	14 1	10 1

B


C

D

In this case, essential prime implicants cover all ones.

$$F = A' C' + A D' + A B' C$$

c)

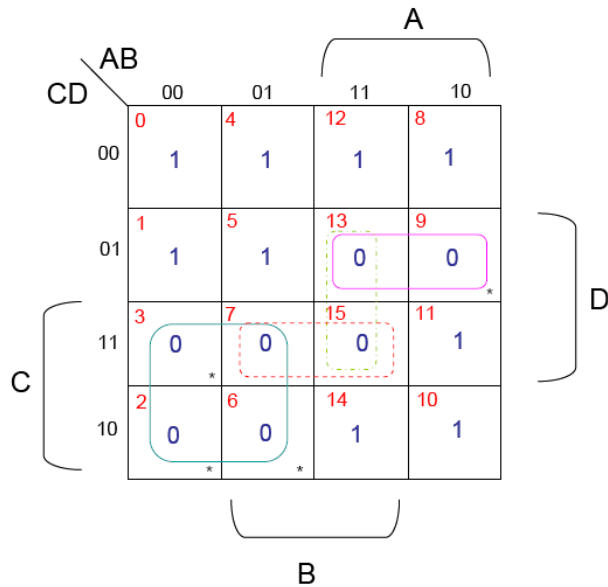

In this case, after essential prime implicants are chosen, only one 0-cell is left uncovered (cell 15). This cell can be covered by the maxterm $(A' + B' + D')$ which is depicted with dash-dot in the graph, or by the maxterm $(B' + C' + D')$ which is depicted with dash in the graph. Both choices are equally good.

$$F = (A + C') (A' + C + D') (A' + B' + D')$$

or

$$F = (A + C') (A' + C + D') (B' + C' + D')$$

d)


SOP form has 3 terms and 7 literals. POS form has 3 terms and 8 literals. We would use SOP form, since it has no more terms and fewer literals, thus would result in fewer or smaller gates.

Q7.

Use the Karnaugh Map method to find a minimal SOP form for the function

$$F = \Sigma_{A,B,C,D}(0,1,2,3,4,5,7,14,15)$$

Solution:

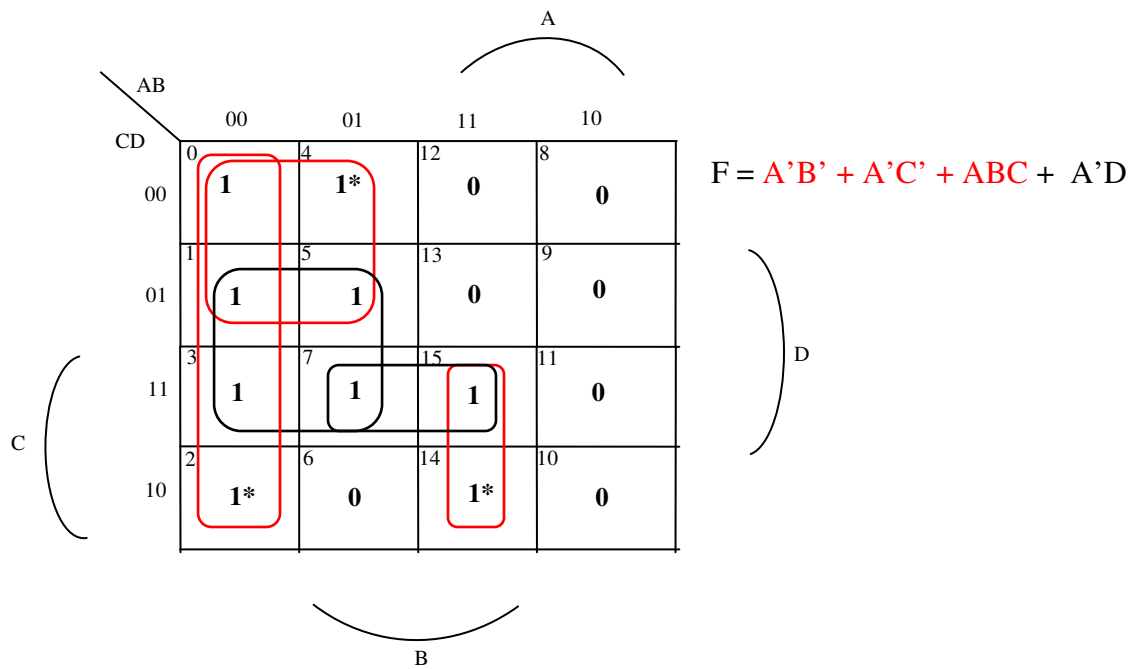


Q8.

Write down the consensus theorem and show using a Karnaugh map what it means in terms minimization.

Solution:

$$XY + X'Z = XY + X'Z + YZ$$

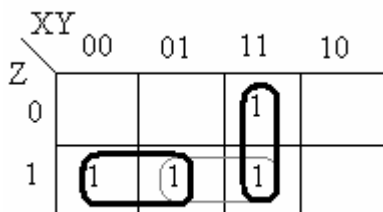

The light (not-dark) gray prime implicant is not necessary for a minimum function as YZ is not necessary in the expression