

Bilkent University, EEE 102 Final Exam, Part I, Fall 2020 [75 minutes]

All of your work/derivation must be shown on the paper to get credit.


Question 1 [25 pts] Design 4-to-1 multiplexer by using **one** 2-to-4 decoder, and **minimum number** of 2-input AND and 2-input OR gates (if necessary). For this question, complements of the variables are **NOT** available.

Question 2 [25 pts] Design synchronous counter that counts through the sequence

$$1 \rightarrow 3 \rightarrow 5 \rightarrow 7 \rightarrow 1 \rightarrow \dots$$

using **minimum number** of T flip flops and **minimum number** of AND and OR gates (if necessary).

 Question 3 [15 pts] Consider the following state diagram where x is the input, y is the output. Identify equivalent states and draw the minimal state diagram.



Bilkent University, EEE 102 Final Exam, Part II, Fall 2020



All of your work/derivation must be shown on the paper to get credit.

Question 4 [15 pts] Design a 3-bit shift register that shifts to left at each positive edge of the clock using J-K flip flops and minimum number of other gates (if needed), i.e.,

$$Q_2(t+1)Q_1(t+1)Q_0(t+1) = Q_1(t)Q_0(t)S_{in}$$

where $Q_i(t)$ represents the state of flip flip i and S_{in} represents 1-bit shift input.

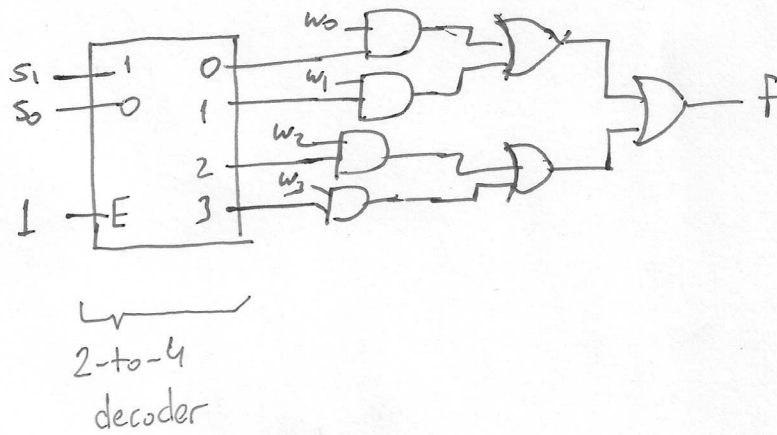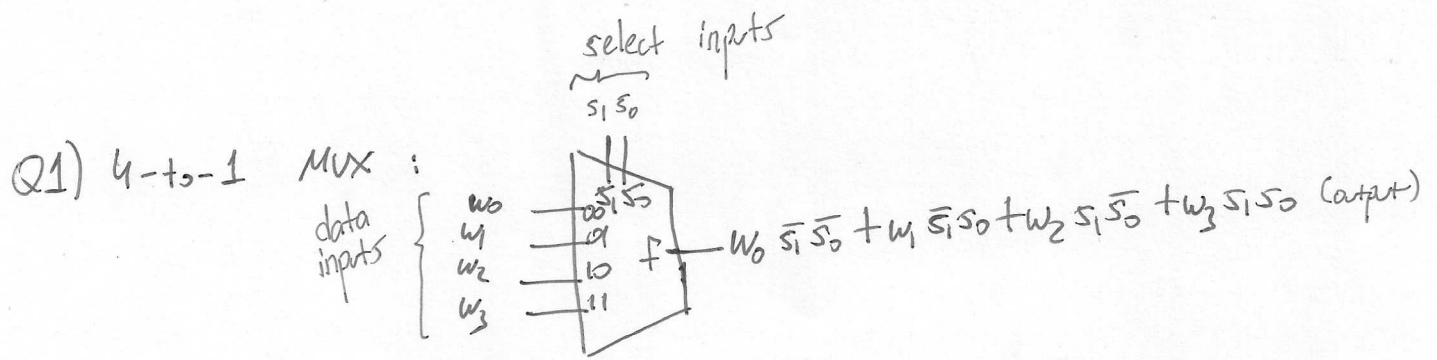Question 5 [20 pts] Design 8 Byte RAM by combining 4 nibble RAMs.




Q2) 4-states \Rightarrow 2 TFFs (minimum)

State mapping:

	$Q_1 Q_0$
1	00
3	01
5	10
7	11

2-bit synchronous up counter

 

State	$Q_1 Q_0$	$Y_2 Y_1 Y_0$	
	00	001	(1)
	01	011	(3)
	10	101	(5)
	11	111	(7)

$Y_2 = Q_1$
 $Y_1 = Q_0$
 $Y_0 = 1$

} output logic

Q3)


P.S.	N.S.		at	
	x=0	x=1	x=0	x=1
A	B	C	0	1
B	C	B	1	0
C	D	A	1	0
D	B	C	0	1

States A and D are equivalent,

reduced state table:


P.S.	N.S.		at	
	x=0	x=1	x=0	x=1
A	B	C	0	1
B	C	B	1	0
C	A	A	1	0

minimal state diagram:

 


Q4) JK | $Q(t+1)$


J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

 


Shift register with D-FF:

 

Shift register with JK-FF:

 

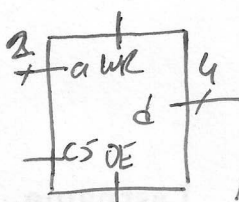Q5) 4-nibble RAM:  8 Byte RAM

address: $a_2 a_1 a_0$ } inputs
 write: \overline{WR}
 output enable: \overline{OE}
 chip select: \overline{CS}
 data: $d_7 d_6 d_5 d_4 d_3 d_2 d_1 d_0$ } input/output

