

**BILKENT UNIVERSITY**  
**Department of Electrical and Electronics Engineering**  
**EEE102 Introduction to Digital Circuit Design**  
**Final Exam**

**24-05-2007**

**Duration 150 minutes**

**Surname:** \_\_\_\_\_

**Name:** \_\_\_\_\_

**ID-Number:** \_\_\_\_\_

**Signature:** \_\_\_\_\_

**There are 9 questions. Solve all.**  
**Do not detach pages. Show all your work.**

<b>Q1</b>	
<b>Q2</b>	
<b>Q3</b>	
<b>Q4</b>	
<b>Q5</b>	
<b>Q6</b>	
<b>Q7</b>	
<b>Q8</b>	
<b>Q9</b>	
<b>Total</b>	

**Q1) (15 points)**

**a) What is a bistable element? Briefly explain. Draw an example circuit.**

**b) What is the formal definition of a counter?**

**c) Explain the fundamental difference between sequential logic circuits and combinational logic circuits.**

**d) What is the difference between DRAM and SRAM.**

**e) What kind of logic components are there in a configurable logic block (CLB) of a XILINX FPGA? ( Just name the logic components. )**

**Q2) (10 points) State the fundamental difference between a D-latch and a D-flip flop. Write VHDL modules one for a D-latch and another for a D-flip flop.**


**Q3) (10 points)**

**Implement the following function by using two 16x1 RAMs and one 8x1 RAM. No other components are allowed.**

A4	A3	A2	A1	A0	F
0	0	0	0	0	0
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	1
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	0
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	0	1	0
1	0	0	1	0	1
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	0	1	0
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	1
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	0
1	1	1	1	1	0

**Q4) (10 points)**

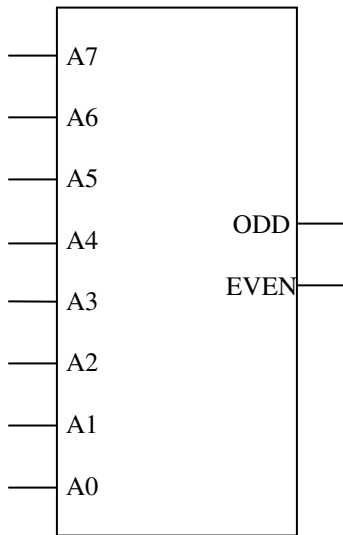
**Design an 8-bit parity circuit by using two-input logic gates only.**




**Q5) (10 points)**

What is the counting sequence of the below ring counter assuming that the following RESET signal is applied to S0. Is this counter self correcting? If yes, show that it is self correcting. Otherwise, modify the circuit so that it becomes self correcting.

S1	S0	Function
0	0	LAST Q
0	1	Shift Right
1	0	Shift Left
1	1	LOAD

 

 **T is sufficiently long to accomodate at least one clock tick**



**Q6) (15 points)**

**Design and draw a two input (X, Y), and one output (F) FSM that works as the following:**

**If  $X > Y$ , then FSM goes to state 1**

**If  $X < Y$ , then FSM goes to state 2**

**If  $X = Y$ , then FSM goes to state 3**

**$F = 1$  if  $X = Y$  at the last clock tick and also at present.**

**Power-on state is state 0.**

**Show all your design steps.**

**Q7) (10 points) For the following code draw the simulation waveform of Z for the below given waveforms of A and B.**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity circuit is

```
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          Z : out STD_LOGIC);
```

end circuit;

architecture Behavioral of circuit is

```
    signal C: std_logic;
```

```
begin
```

```
    process(A,B)
```


```
    begin
```

```
        C <= A and B;
```

```
        Z <= not C;
```


```
    end process;
```

```
end Behavioral;
```

 



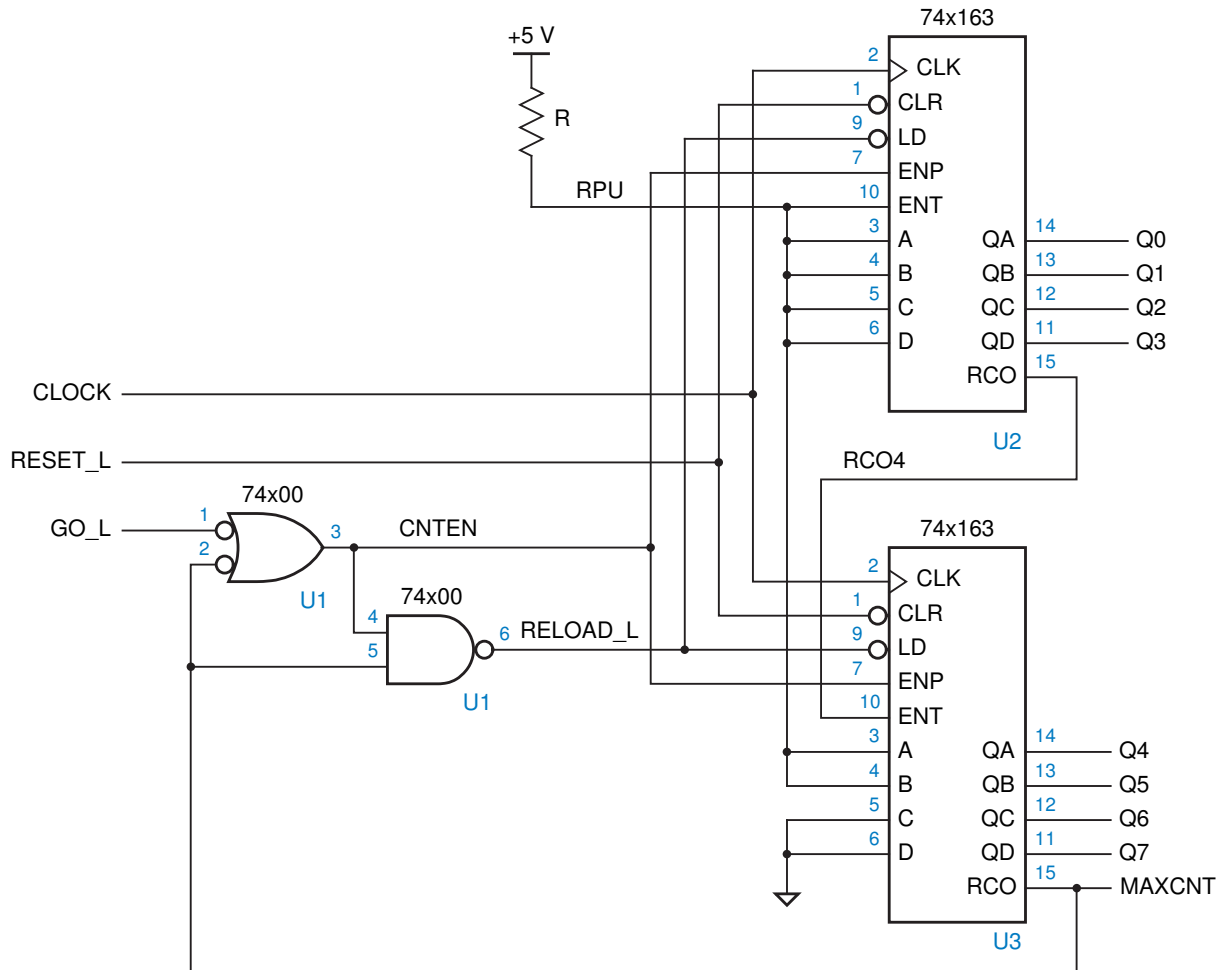**Q8) (10 points) For the circuit below the following VHDL code is written.**



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity modulo_193_counter is
    Port ( CLOCK : in  STD_LOGIC;
          RESET_L : in  STD_LOGIC;
          GO_L : in  STD_LOGIC;
          Q : out unsigned (7 downto 0));
end modulo_193_counter;
```

```
architecture Behavioral of modulo_193_counter is
    component counter_163 is
        Port ( CLK : in  STD_LOGIC;
              CLR_L : in  STD_LOGIC;
              LD_L : in  STD_LOGIC;
              ENP : in  STD_LOGIC;
```

```

    ENT : in STD_LOGIC;
    D : in unsigned (3 downto 0);
    Q : out unsigned (3 downto 0);
    RCO : out STD_LOGIC);
end component;
signal MAXCNT,CNTEN,RELOAD_L: std_logic;
begin
L1:counter_163 port map (CLOCK, RESET_L, RELOAD_L, CNTEN, RCO, "1100", Q,
MAXCNT);
L2:counter_163 port map (CLOCK, RESET_L, RELOAD_L, CNTEN, '1', "1111", Q,
RCO);
CNTEN<=not GO_L or not MAXCNT;
RELOAD_L<= not (CNTEN and MAXCNT);
end Behavioral;

```



**Find and correct the mistakes in this code. Explain your corrections.**

**Q9) (10 points)**

We have an 8-bit bus and three 8-bit positive edge triggered registers, R1, R2, and R3 connected to it as shown in the figure below. The register outputs are three-state and they have active-high output enable (OE) controls. The registers also have active-high input enable (IE) controls which gate their clock inputs. The contents of the registers R1, R2, and R3 are “00001111”, “10101010”, and “11100011” respectively at time 0.

The waveforms of the signals C1, C2, and C3 are shown below.

  At time 1100 ns what are the contents of the registers? Explain your reasoning. Only writing the contents will not be graded.



# Some VHDL Templates:

## ENTITY DECLARATION

```
entity entity_name is
    generic ( constant_names : constant type;
              constant_names : constant type;
              ...
              constant_names : constant type);
    port ( signal_names : mode signal_type;
           signal_names : mode signal_type;
           ...
           signal_names : mode signal_type);
end entity_name;
```

## ARCHITECTURE DEFINITIONS

```
architecture architecture-name of entity-name is
    type declarations
    signal declarations
    constant declarations
    function definitions
    procedure definitions
    component declarations
begin
    concurrent statement
    ...
    concurrent statement
end architecture-name;
```

## COMPONENT DECLARATION

```
component component_name
    port ( signal_names : mode signal type;
           signal_names : mode signal type;
           ...
           signal_names : mode signal type);
end component;
```

## COMPONENT INSTANTIATION

```
label: component_name port map (signal1, signal2, ..., signaln);
or,
label: component_name port map (port1 => signal1, port2 => signal2, ..., portn => signaln);
```

## DATAFLOW TYPE STATEMENTS:

### Simple concurrent assignment statement

```
signal_name <= expression;
```

### Conditional concurrent assignment statement

```
signal_name <=
    expression when boolean-expression else
    expression when boolean-expression else
    ...
    expression when boolean-expression else
    expression;
```

### with-select statement

```
with expression select
    signal_name <= signal_value when choices,
                  signal_value when choices,
    ...
    signal_value when choices;
```

Note that conditional concurrent assignment statement and with-select statement cannot be used in a process statement. Instead, in a process, one can use the sequential conditional assignment statements if and case.

#### BEHAVIORAL TYPE STATEMENTS:

process statement

process(*signal\_name*, *signal\_name*, ..., *signal\_name*)

*type\_declarations*

*variable declarations*

*constant declarations*

begin

*sequential-statement*

    ...

*sequential-statement*

end process;

Simple sequential assignment statement

*signal\_name* <= *expression*;

if statement in its general form

if *boolean\_expression* then *sequential\_statements*

elsif *boolean\_expression* then *sequential\_statements*

...

elsif *boolean\_expression* then *sequential\_statements*

else *sequential\_statements*

end if;

Note that you may not use the else and/or the elsif.

case-when statement

case *expression* is

    when *choices* => *sequential\_statements*

    ...

    when *choices* => *sequential\_statements*

end case;

loop statement

loop

*sequential\_statement*

    ...

*sequential\_statement*

end loop;

for-loop statement

for *identifier* in *range* loop

*sequential\_statement*

    ...

*sequential\_statement*

end loop;

while statement

while *boolean\_expression* loop

*sequential\_statement*

    ...

*sequential\_statement*

end loop;

Note that the if, case, loop, for, and while statements are called sequential statements and they can only be used in a process statement. Also note that each process is one concurrent statement.

Concatenation operator & is used as follows: If A and B are 2 bit numbers then A&B is a four bit number with A being more significant.