

Chapter 4

Karnaugh Map


Task: Combinational circuit minimization

$$f(x_1, x_2, x_3) = \sum m(0, 1) = \bar{x}_1 \bar{x}_2 \bar{x}_3 + \bar{x}_1 \bar{x}_2 x_3 = \bar{x}_1 \bar{x}_2 (\bar{x}_3 + x_3) = \bar{x}_1 \bar{x}_2 = \overline{x_1 + x_2}$$

combinig theorem

Assume that complements of inputs are available

Circuit 1:

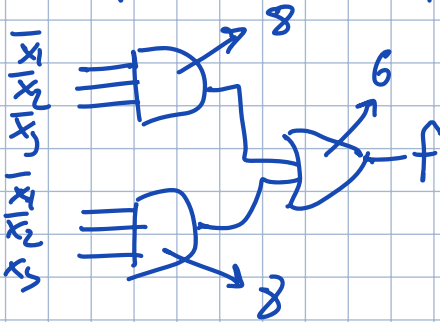

22 transistors in CMOS


3 gates, 8 gate inputs



16 transistors

= 2x # gate inputs.

Circuit 2:

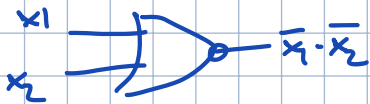

4 transistors, 2 gate inputs

3 variable K-MAP

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

$x_3 \backslash x_1 x_2$	00	01	11	10
0	m_0	m_2	m_6	m_4
1	m_1	m_3	m_7	m_5

neighbors

f:

$x_3 \backslash x_1 x_2$	00	01	11	10
0	1	0	0	0
1	1	0	0	0

$\bar{x}_1 \bar{x}_2$ x_2

$$f = x_1 \cdot x_2$$

- Each neighbor differs only in value of a single variable (Gray encoded)
- Neighbors combine
- Zero values = blank squares

$f:$

		$x_1 x_2$			
	x_3	00	01	11	10
0	1				
1	1				

	00	01	11	10
0	1	1		
1	1	1		

\bar{x}_1

\cdot

	00	01	11	10
0	1			1
1	1			1

\bar{x}_2

$=$

	00	01	11	10
0	1			
1	1			

$\bar{x}_1 \cdot \bar{x}_2$

Systematic Method for Simplification

literal: a variable or its complement



ex: $\bar{x}_1 x_2 x_3$ ← literal
 \uparrow
 literal

product term:


ex: $x_1 \bar{x}_2$, $x_1 x_2 x_3$, x_3 , \bar{x}_1

implicant: product term that covers a subset of 1s on KMAP but not any 0s

→ depends on the logic fn.

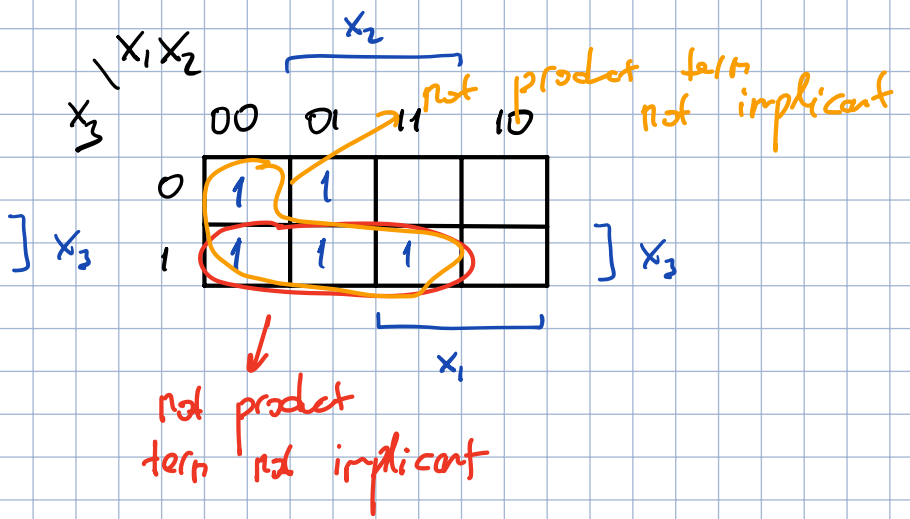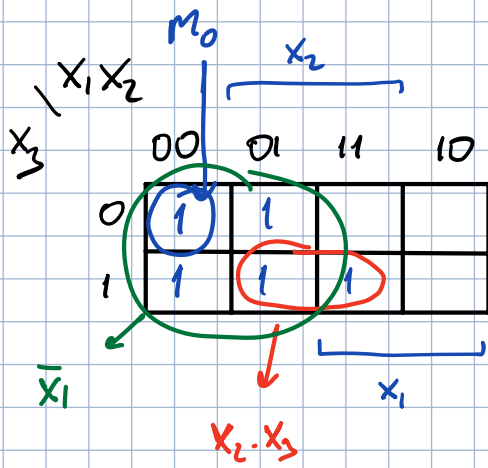

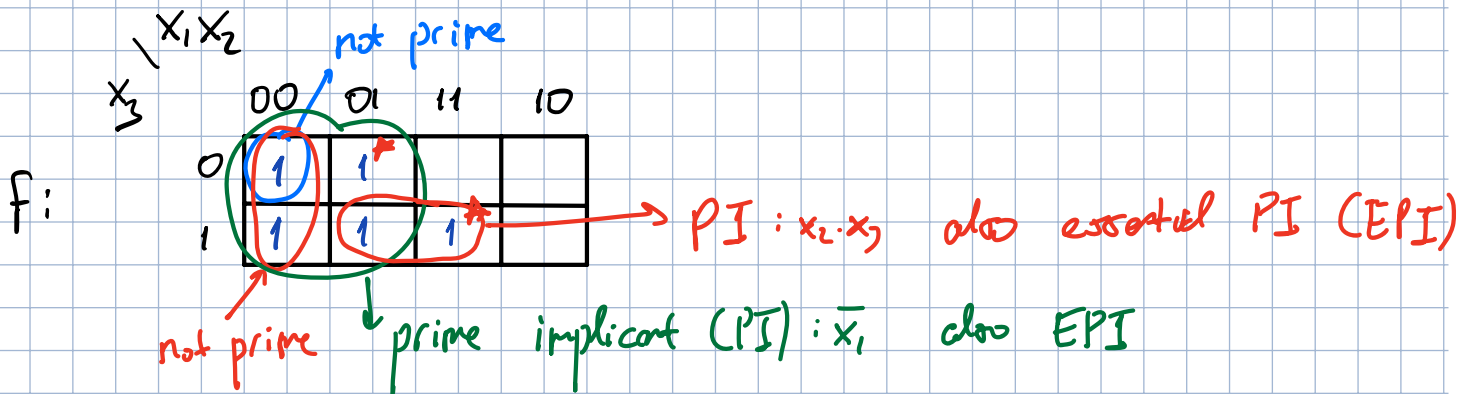Prime implicant: Implicant that cannot be combined into an implicant with fewer literals



Cover: a collection of implicants that cover all 1s on KMAP


ex: $\{m_0, m_1, m_2, m_3, m_7\}$, $\{\bar{x}_1, x_2x_3\}$

Essential prime implicant: A prime implicant that covers a 1 on KMAP that is not covered by any other prime implicant

Algorithm for SOP Minimization

- Find all prime implicants (PI) $\bar{x}_1, x_2 \cdot x_3$
- Find all essential prime implicants (EPI) $\bar{x}_1, x_2 \cdot x_3$
- Form a cover such that
 - It includes all EPIs $\{\bar{x}_1, x_2 \cdot x_3\}$ stopped.
 - If some 1s remain uncovered, include PIs that cover them.

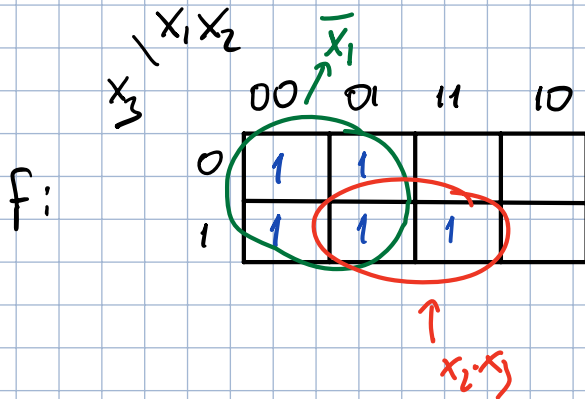
$$f = \bar{x}_1 + x_2 \cdot x_3 \quad \text{minimal SOP form of } f.$$



4 variable K-MAP

	x_1	x_2	x_3	x_4	g
m_0	0	0	0	0	1
m_1	0	0	0	1	0
m_2	0	0	1	0	1
m_3	0	0	1	1	1
m_4	0	1	0	0	1
m_5	0	1	0	1	0
m_6	0	1	1	0	1
m_7	0	1	1	1	1
m_8	1	0	0	0	0
m_9	1	0	0	1	0
m_{10}	1	0	1	0	0
m_{11}	1	0	1	1	0
m_{12}	1	1	0	0	1
m_{13}	1	1	0	1	1
m_{14}	1	1	1	0	0
m_{15}	1	1	1	1	1

		x_1			
		00	01	11	10
x_3	00	m_0	m_4	m_{12}	m_8
	01	m_1	m_5	m_{13}	m_9
	11	m_3	m_7	m_{15}	m_{11}
	10	m_2	m_6	m_{14}	m_{10}

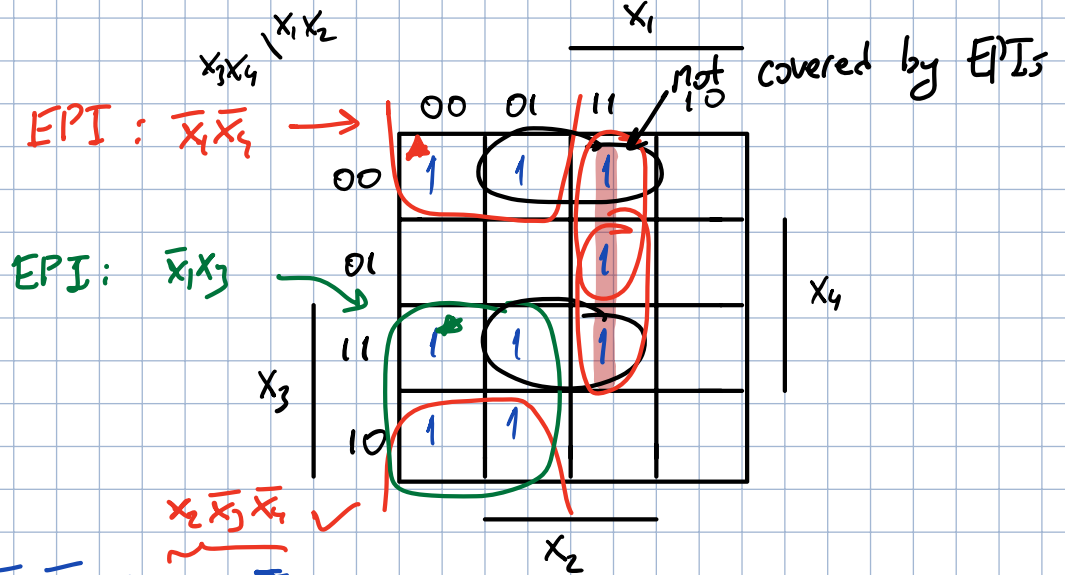

$$g = \bar{x}_1 x_3 + x_1 x_4 + x_1 x_2 \bar{x}_3 + \underbrace{x_1 x_2 x_4}_{x_2 x_3 x_4} \checkmark$$

$$g = \bar{x}_1 \bar{x}_4 + \bar{x}_1 x_3$$

3 minimal SOP forms

Other exercises:

$f:$

$x_3 x_4 \mid x_1 x_2$		x_1			
		00	01	11	10
x_3	00	1	1	1	
	01	1	1	1	
	11			1	1
	10			1	1
		x_2			

x_4

$f:$

$x_3 x_4 \mid x_1 x_2$		x_1			
		00	01	11	10
x_3	00	1			1
	01	1	1	1	1
	11				
	10	1			1
		x_2			

x_4

Annotations: Red lines group (00,00), (00,10), (01,00), (01,10), (11,00), (11,10), and (10,00), (10,10). A blue oval groups the entire row for $x_3=01$. Blue arrows point to the blue oval with label $\bar{x}_3 x_1$ and to the red line for (01,10) with label $\bar{x}_2 \bar{x}_4$.

$$f = \bar{x}_2 \bar{x}_4 + \bar{x}_3 x_1$$

POS Minimization

Truth table for function g :

$x_3x_4 \backslash x_1x_2$		g			
		00	01	11	10
x_3	00	1	1	1	
	01			1	
	11	1	1	1	
	10	1	1		

Grouped by x_2 and x_4 .

Truth table for function \bar{g} :

$x_3x_4 \backslash x_1x_2$		\bar{g}			
		00	01	11	10
x_3	00				1
	01	1	1		1
	11				1
	10			1	1

Grouped by x_2 and x_4 . Red circles indicate groups for $\bar{x}_1 \cdot \bar{x}_3 \cdot \bar{x}_4$ and $x_1 \cdot \bar{x}_2$. Blue oval indicates group for $x_1 \cdot x_3 \cdot \bar{x}_4$.

$$g = \overline{\bar{g}}$$

★ Find minimal SOP of \bar{g} . Use DeMorgan's theorem to get minimal POS of g .

$$\bar{g} = x_1 \bar{x}_2 + \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_1 x_3 \bar{x}_4$$

$$g = \overline{\bar{g}} = \overline{x_1 \bar{x}_2 + \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_1 x_3 \bar{x}_4} = (\bar{x}_1 + x_2) \cdot (x_1 + x_3 + \bar{x}_4) \cdot (\bar{x}_1 + \bar{x}_3 + x_4)$$

Alternative :

Truth table for function g with zeros circled for POS minimization:


$x_3x_4 \backslash x_1x_2$		g			
		00	01	11	10
x_3	00	1	1	1	0
	01	0	0	1	0
	11	1	1	1	0
	10	1	1	0	0

Grouped by x_2 and x_4 . Green circles indicate groups for $\bar{x}_1 + x_2$ and $\bar{x}_1 + \bar{x}_3 + x_4$. Blue arrow indicates group for $x_1 + x_3 + x_4$.

Incompletely Specified Functions

Design Example

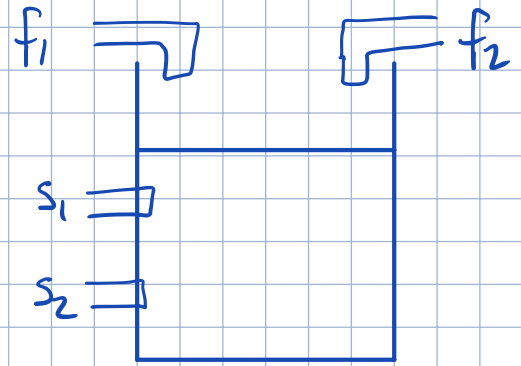- when time = 1
 - both faucets are turned on if pool is empty
 - only faucet 1 is turned on when pool is half empty
 - both faucets are off when pool is full
- when time = 0
 - faucets are always off



sensor = 1 if contacts with water, 0 otherwise.

inputs			outputs			
t	s ₁	s ₂	f ₁	f ₂	f ₁	f ₂
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	d	d	0	0
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	1	0	1	0
1	1	0	d	d	0	0
1	1	1	0	0	0	0

time (t) ↑

(safest option)

impossible →

don't care

without don't care $f_2 = t\bar{s}_2\bar{s}_1$

		s ₁			
		00	01	11	10
f ₁ :	0		d	d	1
	1				1

t

s₂

$$f_1 = t\bar{s}_1$$

		s ₁			
		00	01	11	10
f ₂ :	0		d	d	1
	1				

t

s₂

$$f_2 = t\bar{s}_2$$

```
entity pool is ع10،1،3  
    port(s1, s2, t: in std_logic;  
          f1, f2: out std_logic);  
end pool;
```

```
architecture pool_arch of pool is  
begin  
    f1 <= t and (not s1);  
    f2 <= t and (not s2);  
end pool_arch;
```