

# Synchronous Sequential Circuits - Part I

VOLKAN KURSUN


*Some material from McGraw Hill*

## Outline

- Finite State Machines
- Moore State Model
- State Assignment
- Mealy State Model

 
## Sequential Circuits

- ❑ **Sequential circuit**: the outputs depend on the past behavior of the circuit and the present values of the inputs
- ❑ **Synchronous** sequential circuit: flip-flops are used to implement the state and a clock signal is used to control the operation of the sequential circuit



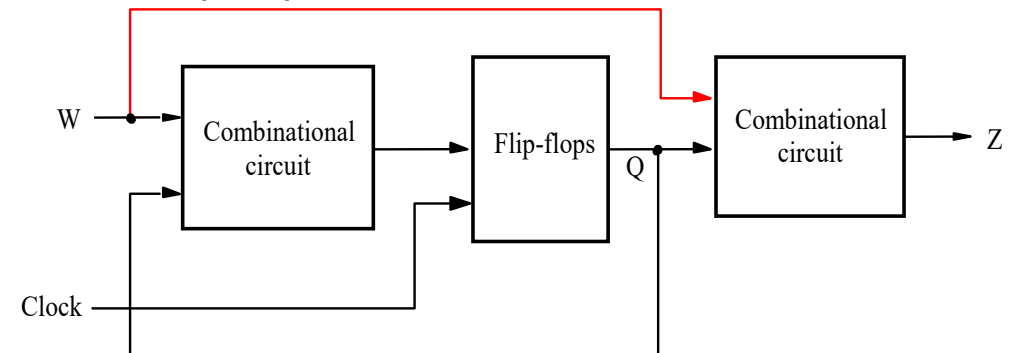
## Synchronous Sequential Circuits

- ❑ **Sequential circuit state**: the stored bits (Q) in the flip-flops are referred to as the state
- ❑ **Synchronized with an edge of a clock signal**, the flip-flops change their state as determined by the combinational circuit that feeds the inputs to these flip-flops



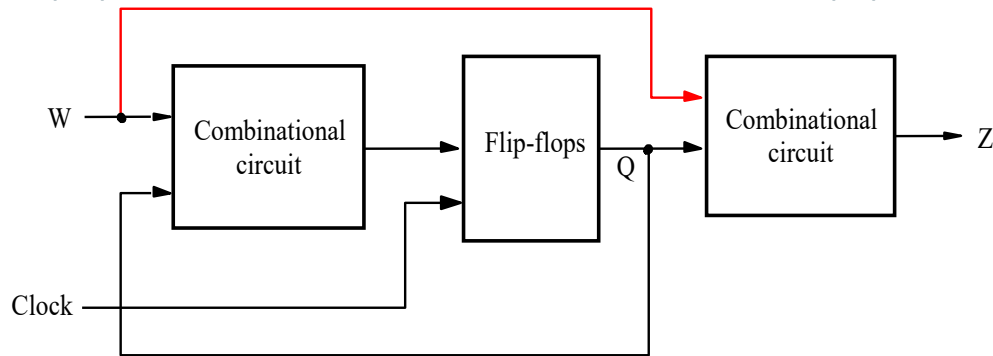
# Synchronous Sequential Circuits

- ❑ Only one transition from one state to another can occur during a clock cycle since the flip-flops are edge triggered
- ❑ The combinational circuit that provides the inputs to the flip-flops has two sources: the primary inputs (W) and the present state of the flip-flops (Q)



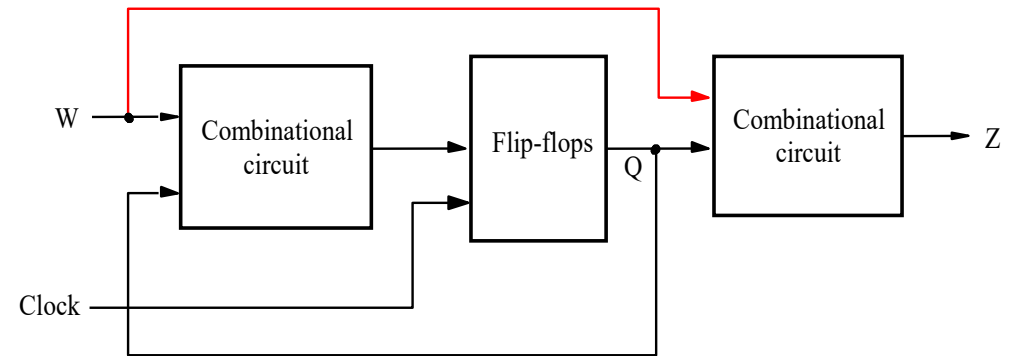
# Synchronous Sequential Circuits

- ❑ The changes in state depend on both the present state (Q) and the primary inputs (W)
- ❑ Sequential circuits are also called finite state machines: behavior of a sequential circuit is represented with a finite number of states


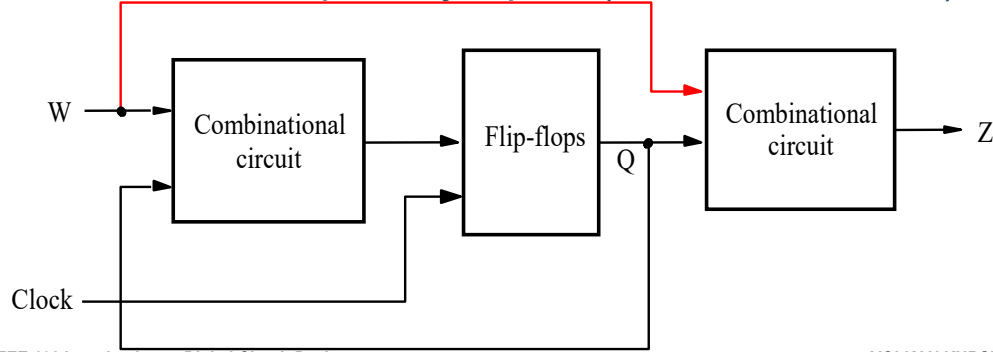
## Two Types of State Machines

- ❑ The outputs of the sequential circuit are produced by another combinational circuit
- 1) Moore Machine: the outputs depend only on the state of the circuit (**the red line does NOT exist**)
  - 2) Mealy Machine: the outputs depend on both the state and the primary inputs (**the red line exists**)



## Outline


- Finite State Machines
- Moore State Model
- State Assignment
- Mealy State Model

# Moore Machine Example

- A vehicle decelerator: a binary signal  $w$  indicates if the speed is within limit. If  $w = 1$  during two consecutive measurements, a control signal  $z$  is asserted to decelerate the car
- Assumptions:
  - 1) The circuit has one input  $w$  and one output  $z$
  - 2) All changes occur with the positive edges of the clock signal
  - 3) If during two immediately preceding clock cycles the input  $w$  was 1, the output  $z = 1$ . Otherwise,  $z = 0$
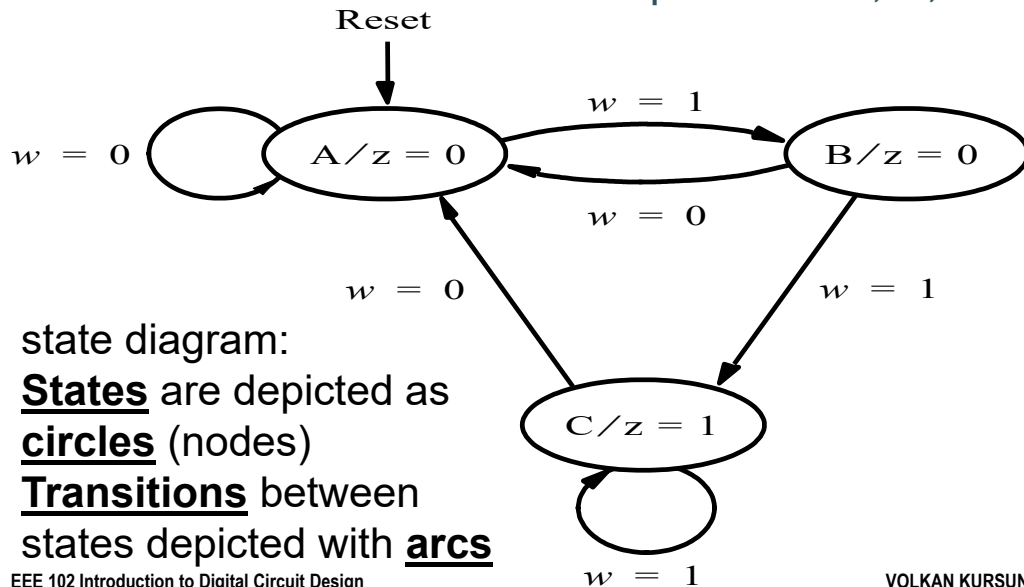
## Moore Machine State Diagram

- 3 states are sufficient to describe the behavior of this machine: states are depicted as A, B, C



## Moore Machine Input-Output Sequences

- Sequences of input and output signals:

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	0	1	0	0	1	1	0

- **Step-1**: determine the number of states and the transitions between states
- A state diagram helps to visualize the operation of the state machine
- Begin with an initial state: this is the state that the circuit should enter when power is first turned on or when reset

## Moore Machine State Table

- **State table**: all transitions from each present state to the next state for different values of the inputs are listed
- **Reset** is not listed in the table: the first state in the table is implied to be the initial state


Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

# Moore Machine State Assignment

- State assignment: the states are listed with letters A, B, and C in the state table
- For logic circuit implementation, each state is represented with a binary number which is composed of state variables
- Each state variable is implemented with a flip-flop
- To represent 3 states, 2 state variables are sufficient:  $y_1$  and  $y_2$
- The state variables are represented with flip-flops
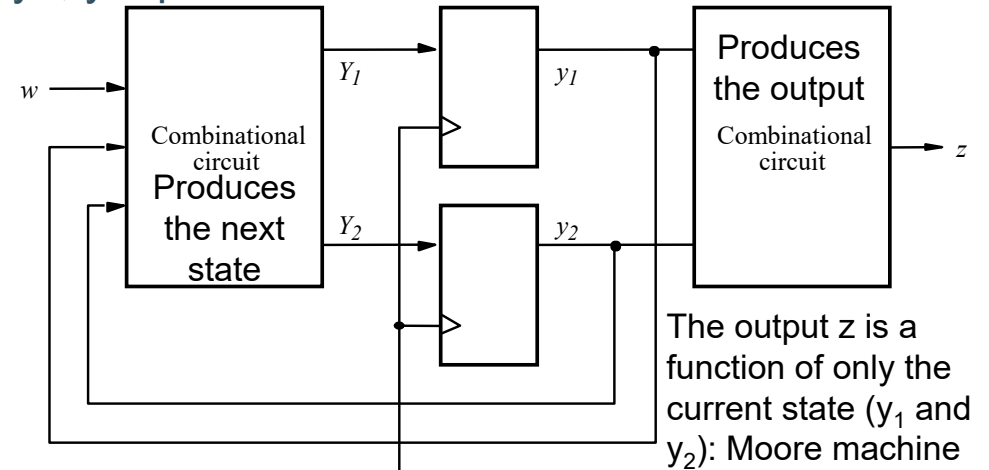
# Moore Machine Structure

- The circuit structure of the finite state machine:
- $Y_1, Y_2$ : next state variables
- $y_1, y_2$ : present state variables



# Moore Machine State Assigned Table

- State-assigned table (truth table for the state machine): assign specific binary numbers to each state
- One assignment (there are other assignment possibilities too):

State A is assigned 0b00, state B is assigned 0b01, and state C is assigned 0b10


	Present state $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$

# Moore Machine Combinational Circuits

- Use 2 D flip-flops to hold the present state variables  $y_1$  and  $y_2$
- Derive the logic expressions for the next state and output functions (design the combinational circuits that produce the next state and outputs)


	Present state $y_2 y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	$dd$	$dd$	$d$

# Moore Machine Next State Logic

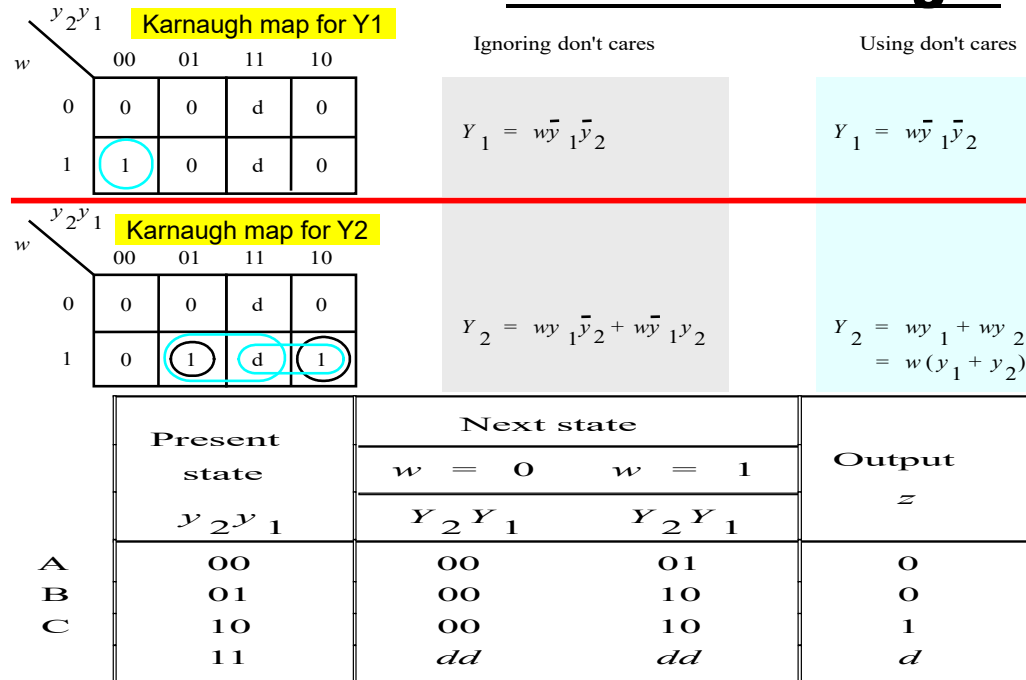
 
# Moore Machine Output Logic


In a **Moore machine**, the **output** is a **function of only the present state variables  $y_1$  and  $y_2$** :


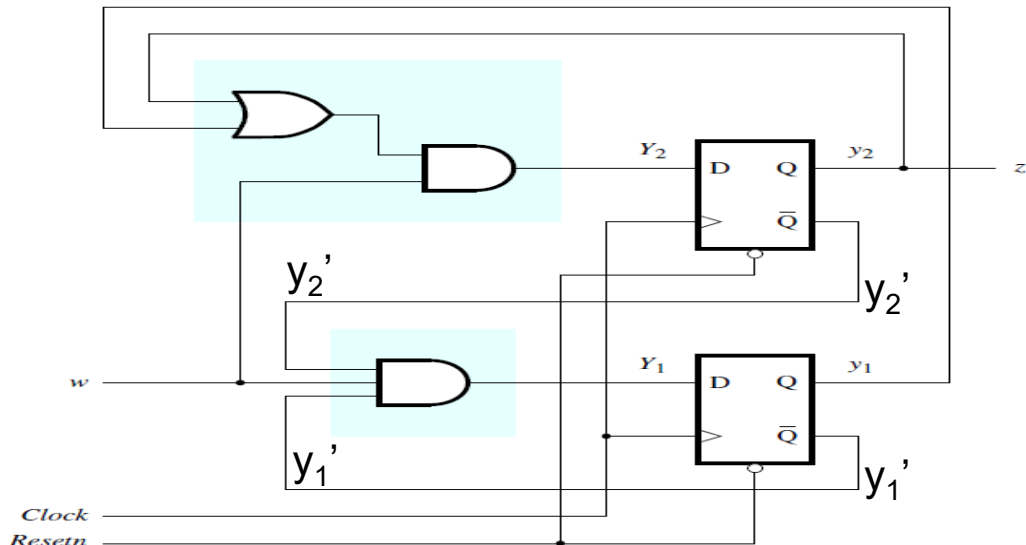
# Moore Machine Circuit

The circuit implementation is:

$$Y_1 = wy_1'y_2', Y_2 = w(y_1 + y_2), z = y_2$$



# Moore Machine VHDL

```

1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;
3  ENTITY simple IS
4      PORT ( Clock, Resetn, w : IN STD_LOGIC ;
              z : OUT STD_LOGIC );
5  END simple ;
6  ARCHITECTURE Behavior OF simple IS
7      TYPE State_type IS (A, B, C) ;
8      SIGNAL y : State_type ;
9      BEGIN
10         PROCESS ( Clock, Resetn, w )
11         BEGIN
12             IF Resetn = '0' THEN
13                 y <= A ;
14             ELSIF (Clock'EVENT AND Clock = '1') THEN
15                 CASE y IS
16                     WHEN A =>
17                         IF w = '0' THEN
18                             y <= A ;
19                         ELSE
20                             y <= B ;
21                         END IF ;
22                     WHEN B =>
23                         IF w = '0' THEN
24                             y <= A ;
25                         ELSE
26                             y <= C ;
27                         END IF ;
28                     WHEN C =>
29                         IF w = '0' THEN
30                             y <= A ;
31                         ELSE
32                             y <= C ;
33                         END IF ;
34                     END CASE ;
35                 END IF ;
36             END PROCESS ;
37             z <= '1' WHEN y = C ELSE '0' ;
38         END Behavior ;
39 END Behavior ;

```

User defined signal TYPE with 3 possible values: A, B, or C

y signal represents the flip-flops that hold the state

The number of flip-flops that hold the state is not specified in the code: **the synthesis tool assigns the states and chooses an appropriate number of flip-flops**


**Sensitivity list:** the signals that can cause the process to change y. **Resetn and Clock are the only two signals that can cause y to change**

The input w is NOT included in the sensitivity list since a change in w can NOT affect y until a change occurs in the Clock signal that may trigger a state change

If the machine is in state C, the output z must be asserted.

Otherwise, the output z must be 0. **MOORE machine**

# Moore Machine Synthesized

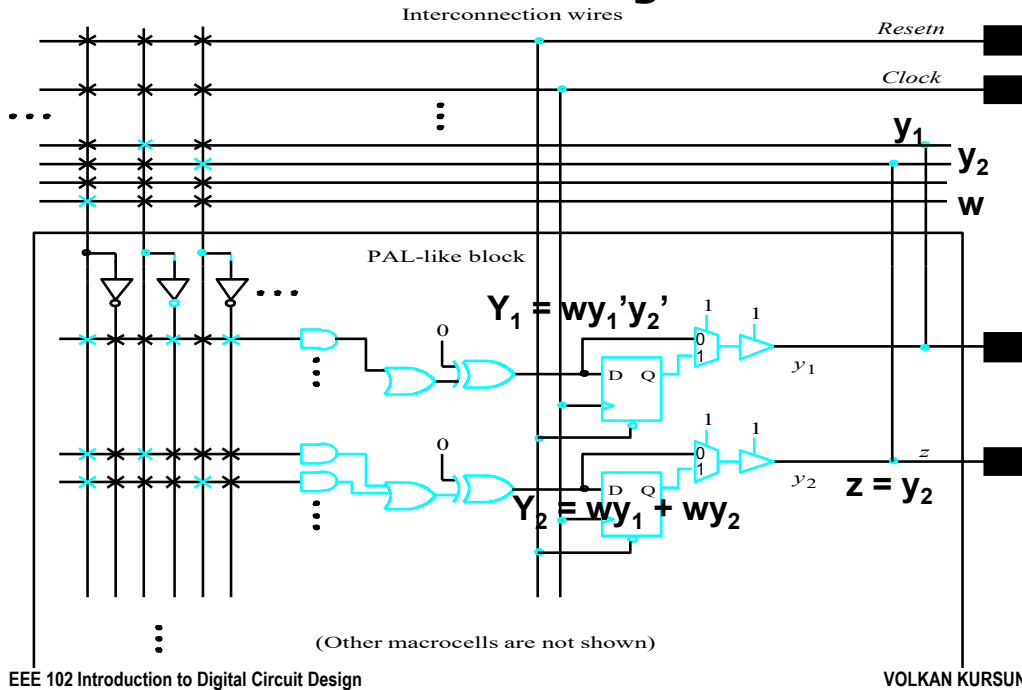

# Moore Machine VHDL-2

ARCHITECTURE Behavior OF simple IS

TYPE State\_type IS (A, B, C);

SIGNAL y\_present, y\_next : State\_type;

BEGIN

PROCESS (w, y\_present)

BEGIN

CASE y\_present IS

WHEN A =>

IF w = '0' THEN

y\_next <= A;

ELSE

y\_next <= B;

END IF;

WHEN B =>

IF w = '0' THEN

y\_next <= A;

ELSE

y\_next <= C;

END IF;

WHEN C =>

IF w = '0' THEN

y\_next <= A;

ELSE

y\_next <= C;

END IF;

END CASE;

END PROCESS;

EEE 102 Introduction to Digital Circuit Design

Alternative code for the state machine:

Signal y\_present corresponds to the current state  
Signal y\_next corresponds to the next state  
y\_present and y\_next are of the user defined TYPE State\_type

The **first PROCESS** describes the combinational circuit that produces the next state y\_next

The **second PROCESS** describes the flip-flops that hold the present state y\_present

PROCESS (Clock, Resetn)

BEGIN

IF Resetn = '0' THEN

y\_present <= A;

ELSIF (Clock'EVENT AND Clock = '1') THEN

y\_present <= y\_next;

END IF;

END PROCESS;

z <= '1' WHEN y\_present = C ELSE '0';

END Behavior;

VOLKAN KURSUN

Note: although statements within a process are evaluated and executed sequentially, all processes within the model are executed concurrently

## Sequential Circuit Design Steps

1. Obtain the specification of the desired circuit
2. Derive a state diagram
3. Derive the corresponding state table
4. Reduce the number of states if possible
5. Decide on the number of state variables
6. Choose the type of flip-flops to be used
7. Derive the logic expressions needed to implement the circuit

asynchronous reset  
asynchronous reset

## FSM for Register Transfers

- Registers hold data for various operations in a computer system
- Sometimes it is necessary to swap the contents of two registers: a third register to store temporary data is used for the swap operation
- Example: swap the contents of registers R1 and R2

Step 1: transfer the contents of R2 to a temporary register R3,  $R3 \leftarrow R2$


Step 2: transfer the contents of R1 to R2,  $R2 \leftarrow R1$

Step 3: transfer the contents of the temporary register R3 to R1,  $R1 \leftarrow R3$



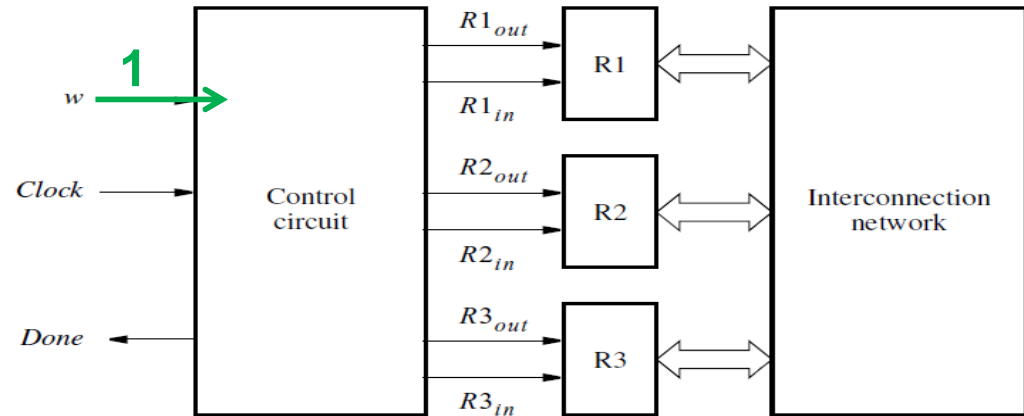
# Register Interconnection

- Registers in a computer system are interconnected via an interconnection network
- Control circuit (FSM) issues the control signals to swap the contents of R1 and R2 in response to an external signal  $w$ :  $w = 1$ , swap R1 and R2



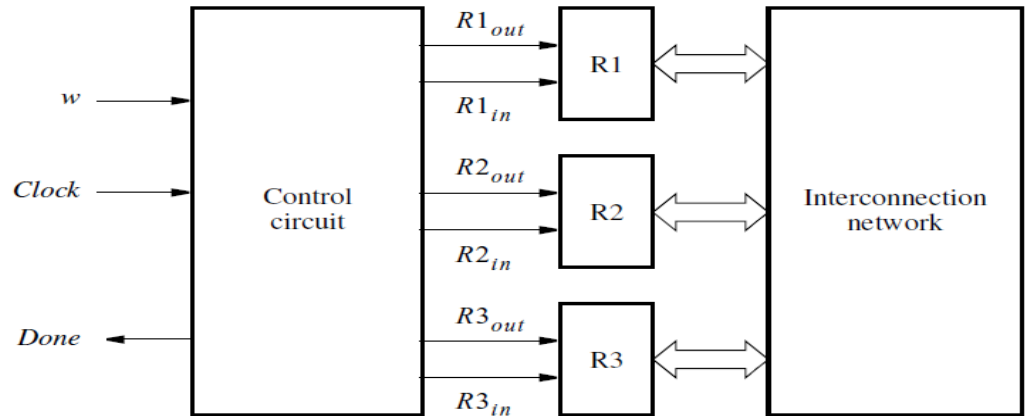
# Register Transfer Control

- $Rk_{out}$  and  $Rk_{in}$  signals are produced by the control circuit
- $Rk_{out}$  signal: causes the contents of register  $Rk$  to be placed into the interconnection network
- $Rk_{in}$  signal: causes the data from the network to be loaded into  $Rk$



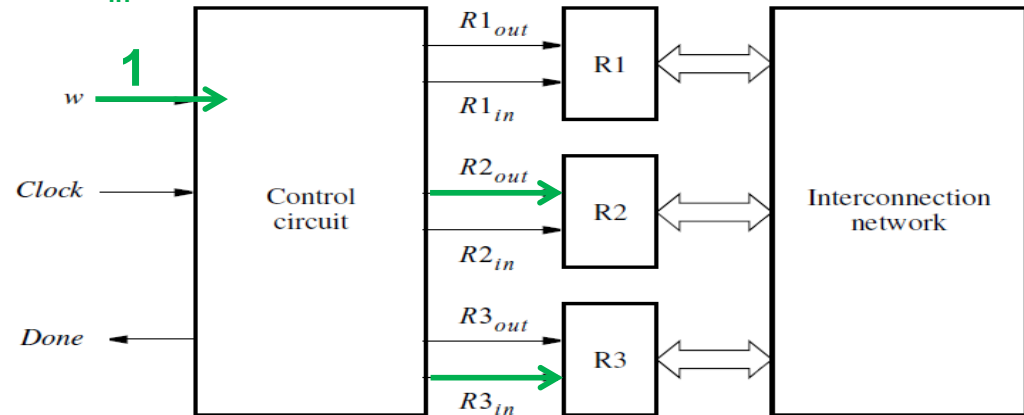
## Register Swap Step 1

- Step 1: transfer the contents of R2 to a temporary register R3,  $R3 \leftarrow R2$
- $R2_{out} = 1$ : place the contents of R2 into the interconnection network
- $R3_{in} = 1$ : data from the network loaded into R3



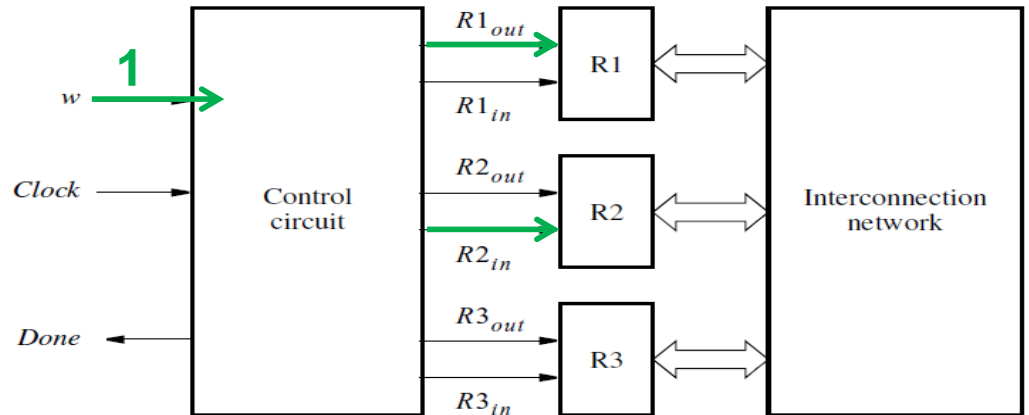
## Register Swap Step 2

- Step 2: transfer the contents of R1 to R2,  $R2 \leftarrow R1$
- $R1_{out} = 1$ : place the contents of R1 into the interconnection network
- $R2_{in} = 1$ : data from the network loaded into R2



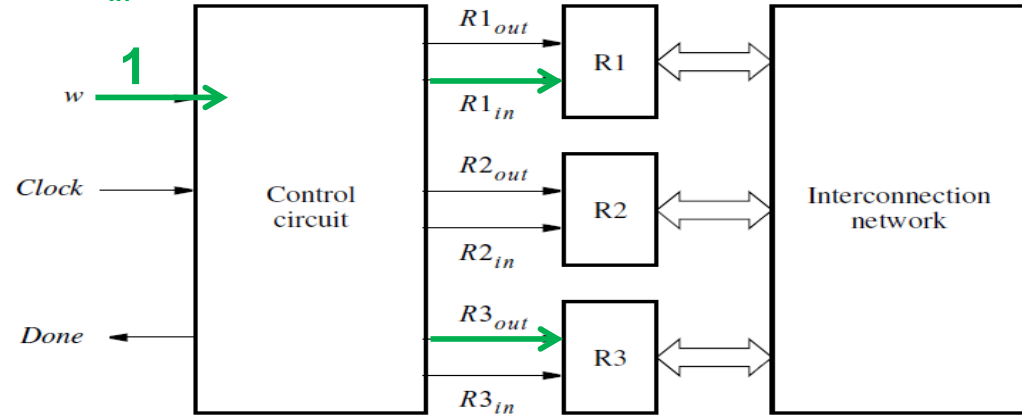
# Register Swap Step 3

- Step 3: transfer the contents of the temporary register R3 to R1,  $R1 \leftarrow R3$
- **$R3_{out} = 1$** : place the contents of R3 into the interconnection network
- **$R1_{in} = 1$** : data from the network loaded into R1



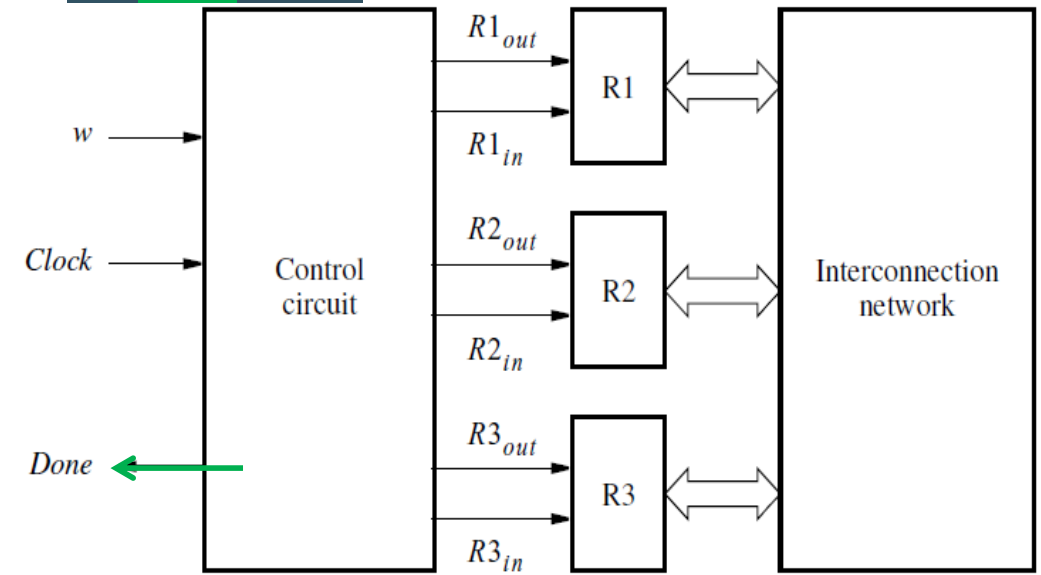
# Register Swap Done

- After the swap operation, control circuit asserts the **Done** signal



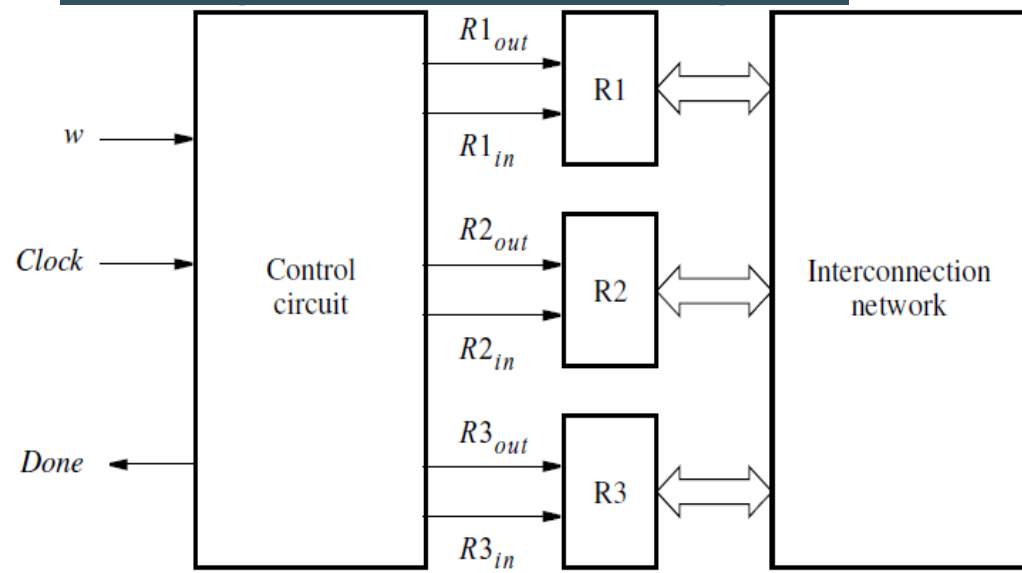
# Moore Machine Example-2

- Design the controller state machine for swapping the contents of two registers:


 
# Moore Machine State Diagram

- The state diagram for the swap machine:





VOLKAN KURSUN

# Moore Machine State Table

Bilkent University

Present state	Next state		Outputs						
	$w = 0$	$w = 1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	A	B	0	0	0	0	0	0	0
B	C	C	0	0	1	0	0	1	0
C	D	D	1	0	0	1	0	0	0
D	A	A	0	1	0	0	1	0	1

- To distinguish these 4 states, 2 state variables are sufficient:  $y_2$  and  $y_1$
- One possible set of assignments for A, B, C, and D are: A = 0b00, B = 0b01, C = 0b10, D = 0b11

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN


# Moore Machine State Assignments

Bilkent University


□ The state-assigned table is:

Present state	Next state		Outputs						
	$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0	0	0	0	0	0	0
B	01	10	0	0	1	0	0	1	0
C	10	11	1	0	0	1	0	0	0
D	11	00	0	1	0	0	1	0	1

□ Derive the next state expressions:

 

 EEE 102 Introduction to Digital Circuit Design



VOLKAN KURSUN

VOLKAN KURSUN

# Moore Machine Output Logic

Bilkent University

Present state	Next state		Outputs						
	$w = 0$	$w = 1$							
	$y_2y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	$Done$
A	00	00	0	0	0	0	0	0	0
B	01	10	0	0	1	0	0	1	0
C	10	11	1	0	0	1	0	0	0
D	11	00	0	1	0	0	1	0	1

- Derive the output expressions: **Moore machine outputs depend only on the present state variables**
- $R1_{out} = R2_{in} = y_2y_1'$
- $R1_{in} = R3_{out} = Done = y_2y_1$
- $R2_{out} = R3_{in} = y_2'y_1$

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN

# Moore Machine Circuit

Bilkent University

Next state expressions:

$$Y_1 = wy_1' + y_1'y_2$$


$$Y_2 = y_1y_2' + y_1'y_2$$

Output expressions:

$$R1_{out} = R2_{in} = y_1'y_2$$

$$R1_{in} = R3_{out} = Done = y_1y_2$$

$$R2_{out} = R3_{in} = y_1y_2'$$

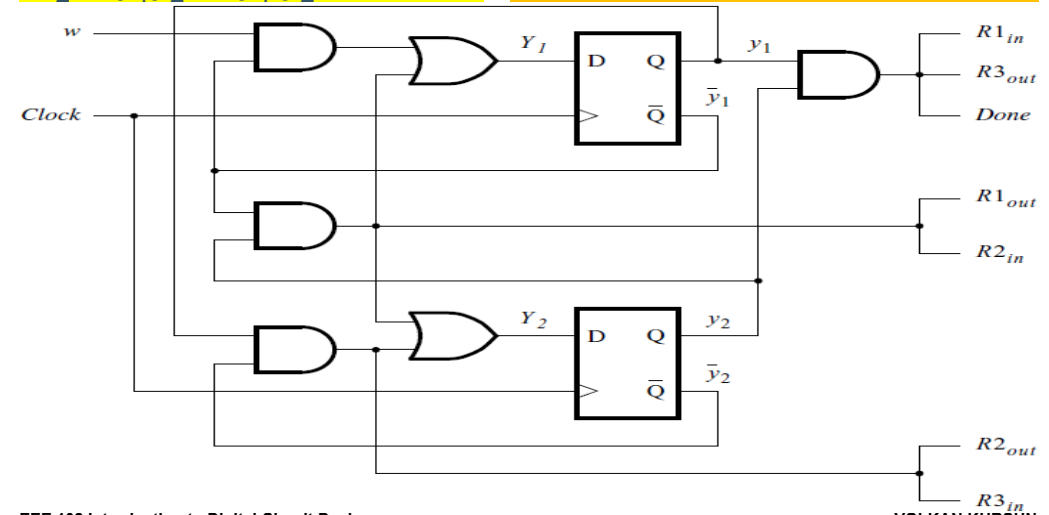

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

Outline

- Finite State Machines
- Moore State Model
- State Assignment
- Mealy State Model

State Assignment

- Some state assignments may lead to simpler circuits than others
- Example: revisit the car decelerator design. Re-assign the states A, B, and C to 0b00, 0b01, and 0b11

	Present state $y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	$dd$	$dd$	$d$

Next State and Output Logic

$Y_2 = wy_1$

$y_2y_1$	00	01	11	10
w				
0	0	0	0	d
1	0	1	1	d

$Y_1 = w$

$y_2y_1$	00	01	11	10
w				
0	0	0	0	d
1	1	1	1	d

$z = y_2$


$y_1$	0	1
$y_2$		
0	0	0
1	d	1

	Present state $y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	$dd$	$dd$	$d$

State Assignments Comparison

- Draw the circuit and compare to the first design:

$Y_1 = w, Y_2 = wy_1, z = y_2$

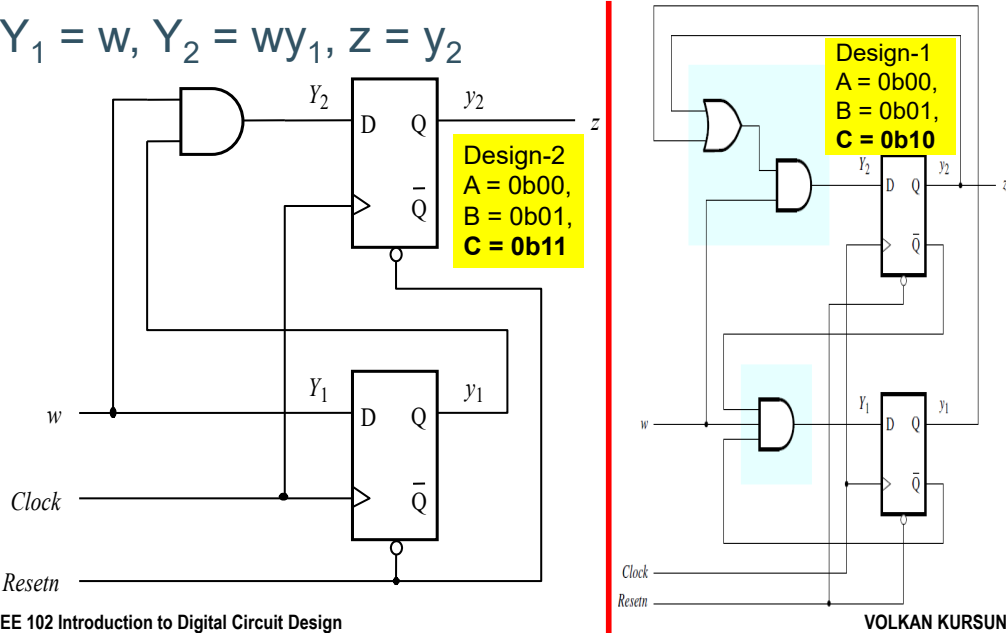

# State Assignment VHDL

- It is possible to specify the state assignments in VHDL code

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY simple IS
    PORT ( Clock, Resetn, w : IN    STD_LOGIC ;
          z : OUT    STD_LOGIC ) ;
END simple ;

ARCHITECTURE Behavior OF simple IS
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);
    CONSTANT A : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00" ;
    CONSTANT B : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01" ;
    CONSTANT C : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11" ;
BEGIN
    PROCESS ( w, y_present )
    BEGIN
        CASE y_present IS
            WHEN A =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= B ;
                END IF ;
            WHEN B =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= C ;
                END IF ;
            WHEN C =>
                IF w = '0' THEN y_next <= A ;
                ELSE y_next <= C ;
                END IF ;
        END CASE ;
        y_present <= y_next ;
    END PROCESS ;
    z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;
```

y\_present is a 2-bit STD\_LOGIC\_VECTOR  
The CASE statement must cover all possible values of y\_present (note that the first process is for the next state logic which is a combinational circuit). WHEN OTHERS clause is used to cover y\_present = 0b10. The state 0b10 would normally never happen. However, if it occurs due to noise, the state machine transitions back to the initial reset state A in case of such an error.

In an alternative design, y\_next could be assigned don't care WHEN y\_present = 0b10: y\_next <= "-".

```
END IF ;
WHEN OTHERS =>
    y_next <= A ;
END CASE ;
END PROCESS ;
PROCESS ( Clock, Resetn )
BEGIN
    IF Resetn = '0' THEN
        y_present <= A ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next ;
    END IF ;
END PROCESS ;
z <= '1' WHEN y_present = C ELSE '0' ;
END Behavior ;
```

# State Assignment Example-2



- Redesign the swap controller by re-assigning the states: interchange the binary numbers assigned to states C and D

	Present state $y_2y_1$	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	Done
A	00	00	01	0	0	0	0	0	0	0
B	01	11	11	0	0	1	0	0	1	0
C	11	10	10	1	0	0	1	0	0	0
D	10	00	00	0	1	0	0	1	0	1

# State Assignment Example-2

	Present state $y_2y_1$	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	Done
A	00	00	01	0	0	0	0	0	0	0
B	01	11	11	0	0	1	0	0	1	0
C	11	10	10	1	0	0	1	0	0	0
D	10	00	00	0	1	0	0	1	0	1

- Derive the next-state expressions:

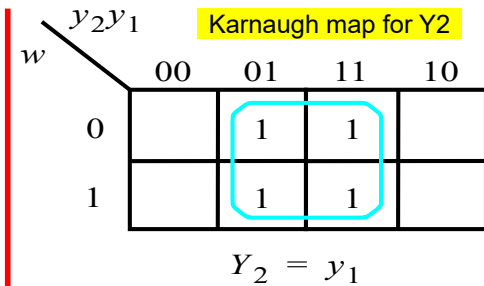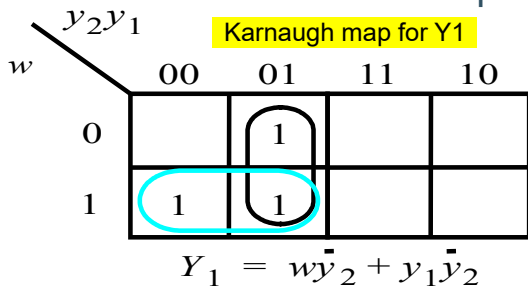

# State Assignment Example-2

	Present state $y_2y_1$	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		$Y_2Y_1$	$Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	Done
A	00	00	01	0	0	0	0	0	0	0
B	01	11	11	0	0	1	0	0	1	0
C	11	10	10	1	0	0	1	0	0	0
D	10	00	00	0	1	0	0	1	0	1

- Derive the output expressions:

$$R1_{out} = R2_{in} = y_2y_1$$

$$R1_{in} = R3_{out} = \text{Done} = y_2y_1'$$

$$R2_{out} = R3_{in} = y_2'y_1$$

- The resulting circuit is simpler as compared to the first design based on a different state assignment

# One-Hot Encoding

- In the previous examples, minimum number of flip-flops were used to represent the states
- An alternative state assignment method is to use as many state variables as there are states
- For each state, only one state variable is 1 (hot) while the other state variables are all 0s
- **Goal: simplify the combinational circuits** that produce the next state and outputs
- Simpler combinational circuits **may** lead to higher clock frequency
- **Tradeoff: increased number of flip-flops**

# One-Hot Encoding Example

- Revisit the swap controller design: for the 4 states, use 4 state variables (treat the unused bit combinations as don't cares to simplify the logic circuits)

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$ $Y_4Y_3Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	Done
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

# One-Hot Encoding Example

- Derive the next state expressions:

$$Y_1 = w'y_1 + y_4, Y_2 = wy_1, Y_3 = y_2, Y_4 = y_3$$

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$ $Y_4Y_3Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	Done
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

# One-Hot Encoding Example

- Derive the output expressions:

$$R1_{out} = R2_{in} = y_3, R1_{in} = R3_{out} = \text{Done} = y_4$$

$$R2_{out} = R3_{in} = y_2$$

	Present state	Nextstate		Outputs						
		$w = 0$	$w = 1$							
		$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$ $Y_4Y_3Y_2Y_1$	$R1_{out}$	$R1_{in}$	$R2_{out}$	$R2_{in}$	$R3_{out}$	$R3_{in}$	Done
A	0 001	0001	0010	0	0	0	0	0	0	0
B	0 010	0100	0100	0	0	1	0	0	1	0
C	0 100	1000	1000	1	0	0	1	0	0	0
D	1 000	0001	0001	0	1	0	0	1	0	1

### 3 Swap Controllers: Comparison

#### Design-1) Original design (minimum number of flip-flops):

Next state expressions:

$$Y_1 = wy_1' + y_1'y_2$$

$$Y_2 = y_1y_2' + y_1'y_2$$

Output expressions:

$$R1_{out} = R2_{in} = y_1'y_2$$

$$R1_{in} = R3_{out} = \text{Done} = y_1y_2$$

$$R2_{out} = R3_{in} = y_1y_2'$$

#### Design-2) Simplified design with state reassignment (minimum number of flip-flops):

$$Y_1 = wy_2 + y_1\bar{y}_2 \quad Y_2 = y_1$$

$$R1_{out} = R2_{in} = y_2y_1, R1_{in} = R3_{out} = \text{Done} = y_2y_1', R2_{out} = R3_{in} = y_2'y_1$$

#### Design-3): with one-hot encoding

The next state expressions :

$$Y_1 = w'y_1 + y_4, Y_2 = wy_1, Y_3 = y_2, Y_4 = y_3$$

The output expressions with one-hot encoding:

$$R1_{out} = R2_{in} = y_3, R1_{in} = R3_{out} = \text{Done} = y_4$$

$$R2_{out} = R3_{in} = y_2$$

### One-Hot Encoding Observations

□ The next state expressions with one-hot encoding:

$$Y_1 = w'y_1 + y_4, Y_2 = wy_1, Y_3 = y_2, Y_4 = y_3$$

□ The output expressions with one-hot encoding:

$$R1_{out} = R2_{in} = y_3, R1_{in} = R3_{out} = \text{Done} = y_4$$

$$R2_{out} = R3_{in} = y_2$$

- These output expressions are simpler than the previous two designs that used minimum number of flip-flops for the state assignment
- However, the number of flip-flops increased from 2 to 4 with the one-hot state assignment

## Outline


- Finite State Machines
- Moore State Model
- State Assignment
- Mealy State Model

## Mealy State Model

- Mealy-type machines: the outputs are generated based on both the present state of the circuit and the present values of the inputs
- Provides additional flexibility in the design of sequential circuits (number of states can be reduced but the circuit behavior also changes)
- Example: re-design the register swap controller as a Mealy-machine
- The Mealy implementation requires 3 states: although 2 flip-flops are still needed, the control signals are generated one cycle sooner than the Moore machine which requires 4 states


# Mealy State Model Example

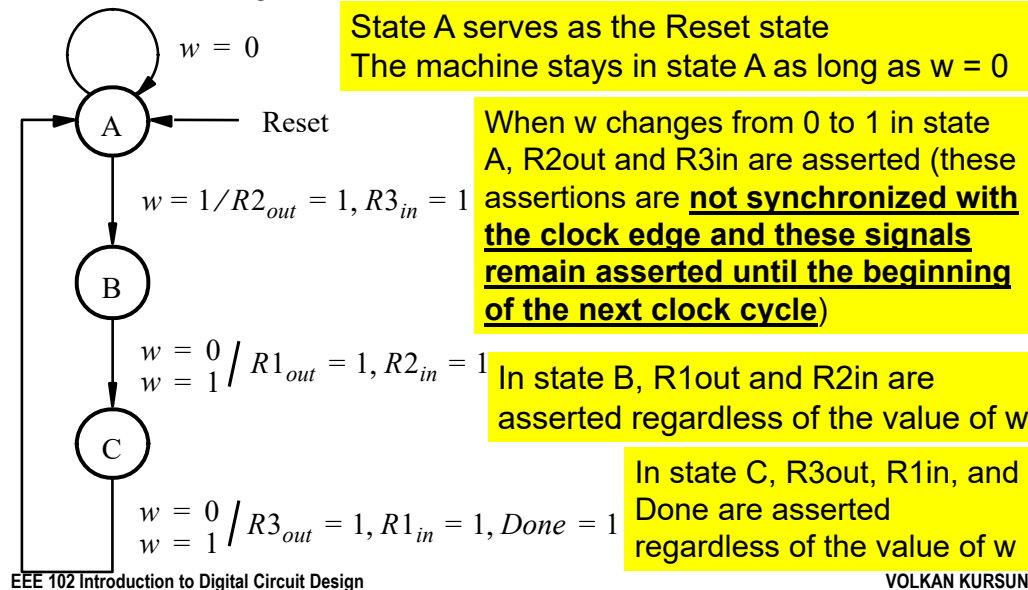- Example: re-design the register swap controller as a Mealy-machine


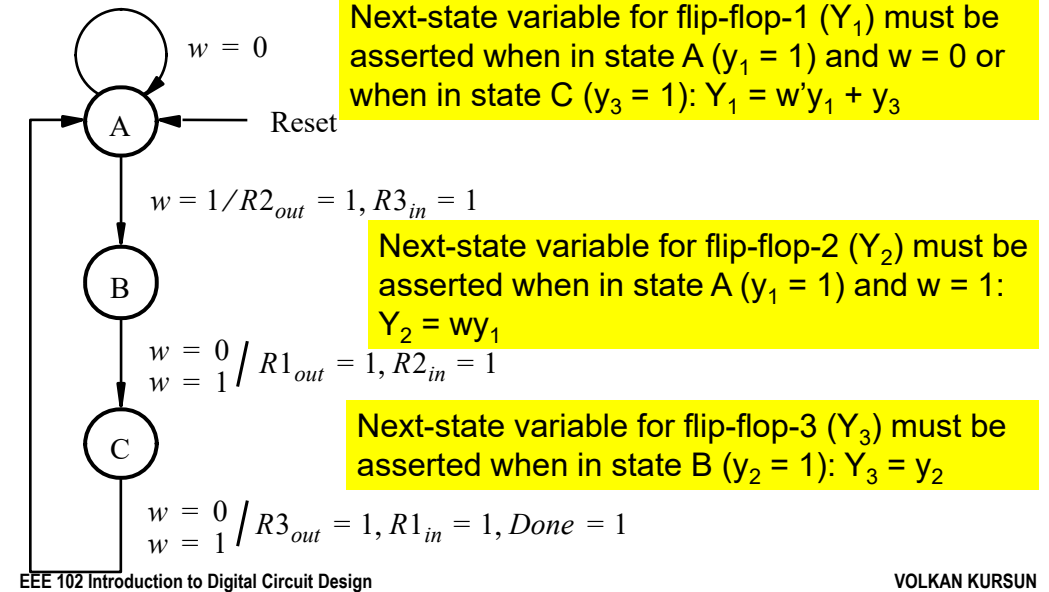
# Mealy State Model Example

- Implement the Mealy machine with one-hot encoding:  $A = 0b001$ ,  $B = 0b010$ , and  $C = 0b100$



# Mealy State Model Example

- Implement the Mealy machine with one-hot encoding:  $A = 0b001$ ,  $B = 0b010$ , and  $C = 0b100$

