

Q1

Find binary equivalents of the following decimal numbers (in 2's complement)

a) $9.2_{10} = ?$

b) $-12.7_{10} = ?$


a) $9_{10} = 01001$

(is complement!)

$0.2 \Rightarrow$

0.4	0
0.8	0
1.6	1
1.2	1
0.4	0

$= \overline{0011}$

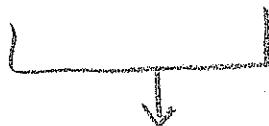

$9.2_{10} = 01001.\overline{0011}_2$

b) $-12.7 = -13 + 0.3$


$-13 = -(01101_2) = 2's \text{ complement } \{ 01101_2 \}$

$= 10011$

$0.3 \Rightarrow$

0.6	0
1.2	1
0.4	0
0.8	0
1.6	1

$= \overline{10010}$

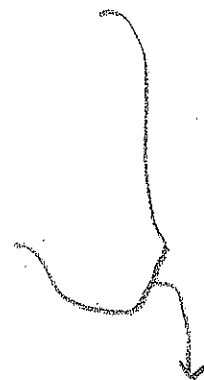

$-12.7 = 10011.\overline{01001}_2$

Q2

Do the calculations for the binary numbers given in 2's complement form. State whether there is overflow or not.

$$\begin{array}{r} 01101 \quad (13) \\ 01011 \quad (11) \\ \hline \end{array}$$

$$\begin{array}{r} 10011 \quad (-13) \\ 11101 \quad (-3) \\ \hline \end{array}$$

$$\begin{array}{r} 00111 \quad (7) \\ 01100 \quad (-12) \\ \hline \end{array}$$



$$\begin{array}{r} 01101 \\ 01011 \\ \hline 11000 \end{array}$$

overflow



$$\begin{array}{r} 10011 \\ 11101 \\ \hline 10000 \end{array}$$

diff. core
No overflow



write as an addition

$$\begin{array}{r} 00111 \\ 10100 \\ \hline 11011 \end{array}$$

No overflow

SOP? POS?

03

SOP

xy	00	01	11	10
00	1	0	0	1
01	d	1	d	d
11	0	1	0	0
10	1	0	0	1

$x' y' w$

$$F = y' w' + x' y w$$

Minimal sum \Rightarrow Sum of prime implicants.

POS (two ways)

POS

xy	00	01	11	10
00	1	0	0	1
01	d	1	d	d
11	0	1	0	0
10	1	0	0	1

$(y' + w)$

$(y + w')$

$(x' + w')$

Essential prime implicants must be included in every minimal sum.

\Rightarrow Start with including essential prime implicants! (after finding distinguished 1 cell)

$$F = (x' + w')(y' + w)(y + w')$$

xy	00	01	11	10
00	0	1	1	0
01	d	0	d	d
11	1	0	1	1
10	0	1	1	0

$y w'$

$x w$

$y w$

$$F' = x w + y w' + y' w$$


$$F = (x' + w')(y' + w)(y + w')$$

write F' first And SOP first

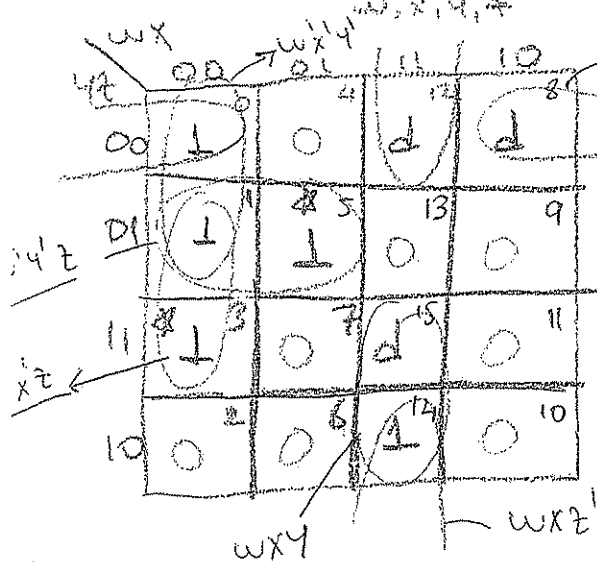Q4

Find minimal SOP expressions

$$F = \sum_{w,x,y,z} (0, 1, 3, 5, 14) + \text{2 essential}$$



$$F_1 = w'y'z + w'x'y'z + w'x'yz + wx'y'z$$

$$F_2 = w'y'z + w'x'y'z + w'x'yz + wx'y'z$$

$$F_3 = w'y'z + w'x'y'z + w'x'yz + wx'y'z$$

$$F_4 = w'y'z + w'x'y'z + w'x'yz + wx'y'z$$

Distinguished ones! Prime implicants including them are essential prime implicants


You should take them in any case!

After taking essential prime implicants, if there still remains 1s that are not covered, take also the prime implicants (the largest ones) that cover these 1s.

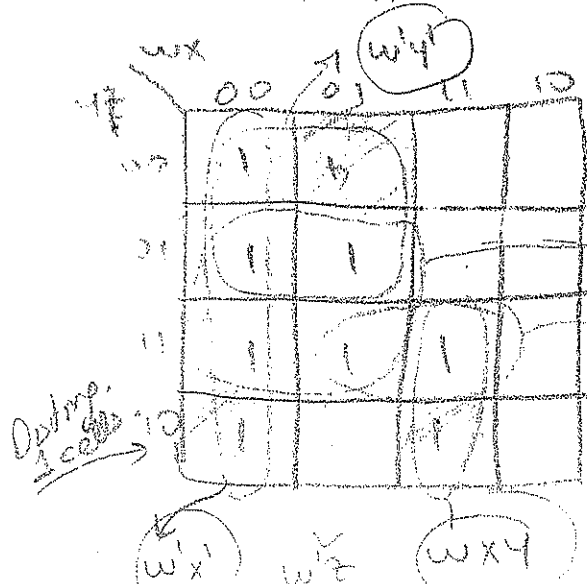Q5

Find minimal SOP of,

$$F = \sum_{w,x,y,z} (0, 1, 2, 3, 4, 5, 7, 14, 15)$$



Find prime implicants first.

Open the distinguished 1 cells

Choose the essential prime implicants.

Choose the largest!



x y z

Minimal!



$$F = w'y'z + w'x'y'z + w'x'yz + wx'y'z$$


$$\text{OR } w'x'y'z + w'x'yz + wx'y'z + wx'yz$$

Q6

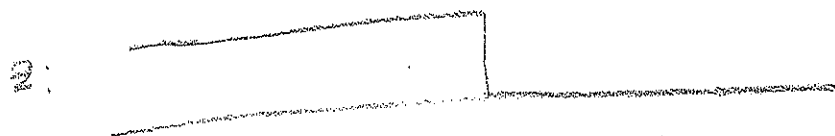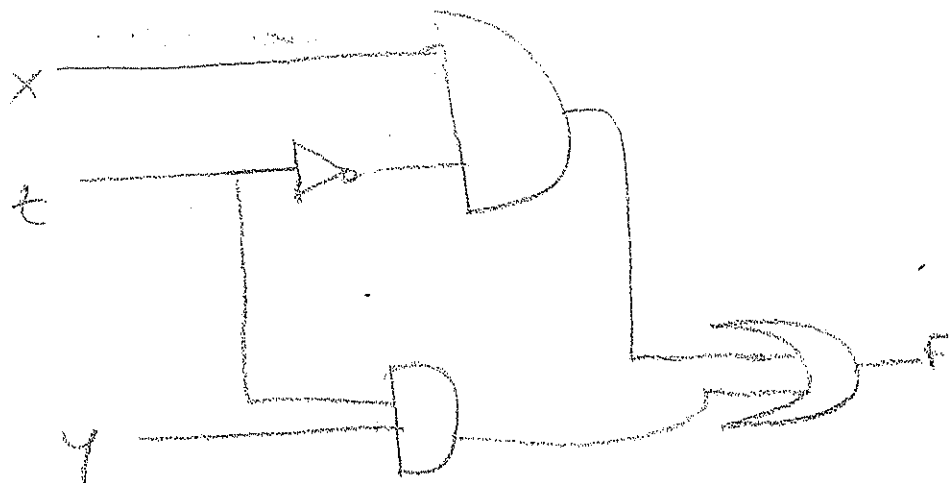

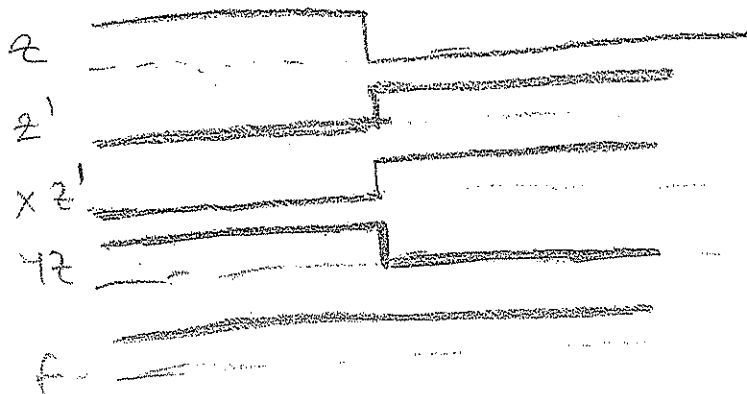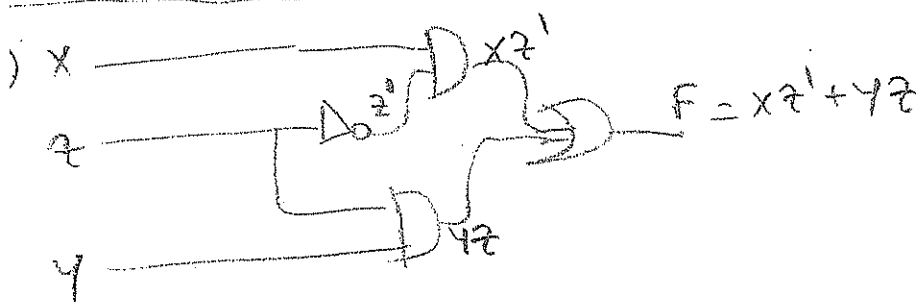- a) Draw the time waveform of F if the gates do not have any delays for the given z
- b) Draw the time waveform of F if each gate has 10 ns delay. Assume $X = Y = 1$ throughout.



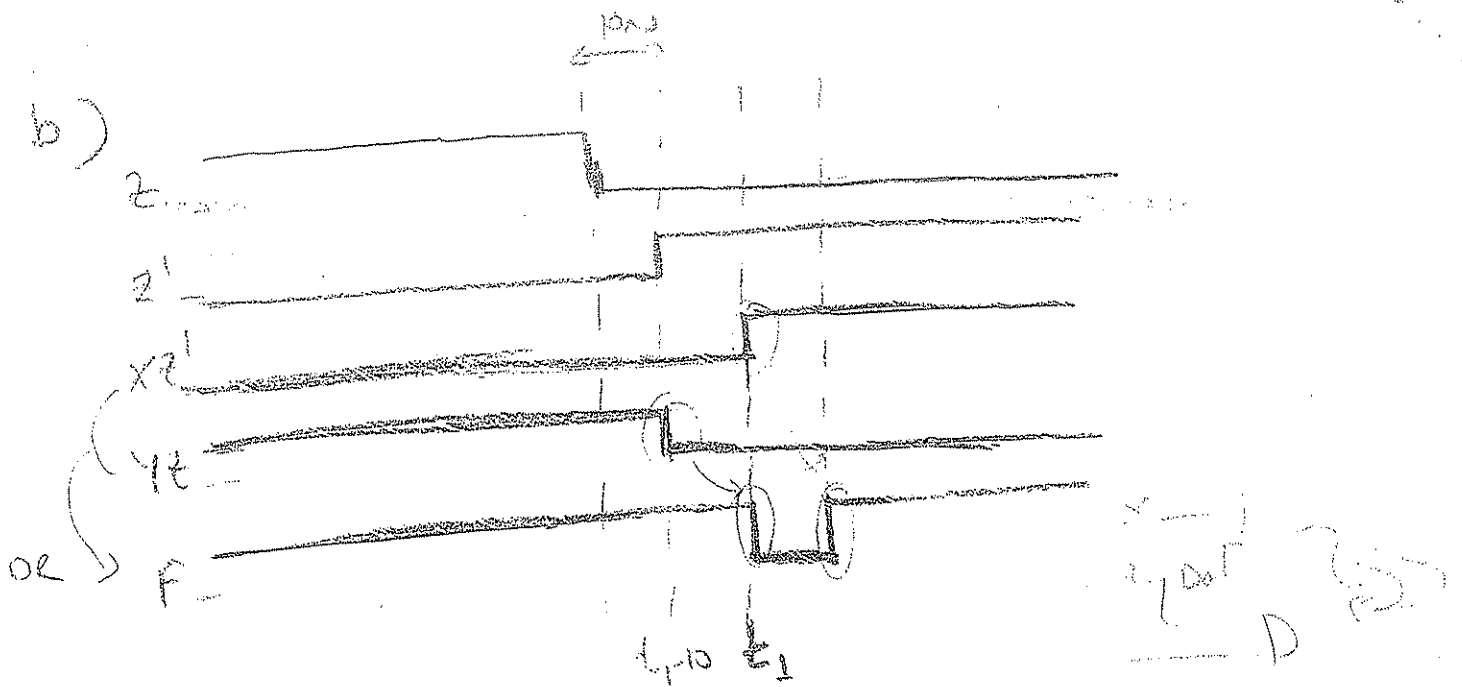

observation

$$F = xz' + yz = 1z' + 1z = z' + z = 1$$


F must be 1 always. looking at expression of F
 However such expressions are steady state expressions.

F expression \Rightarrow implies steady state \approx no delay of gates.
 (if inputs are fixed for a long time)



Q7) Draw the schematics of

$$F = (w' + x)(w' + y)(y + z) \text{ using}$$



NOR gates only

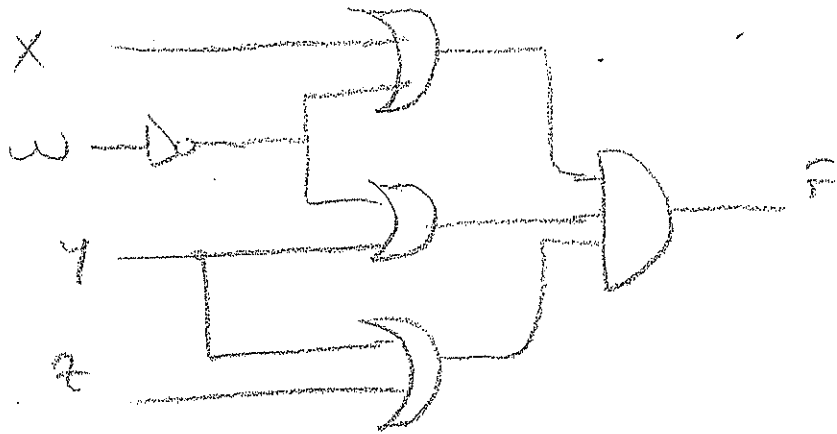

NOR

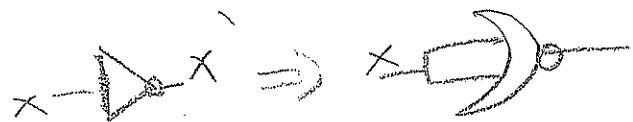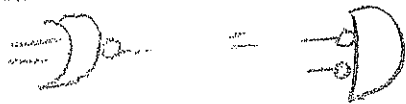

$$\left(\frac{x + x}{x} \right)' = x'$$

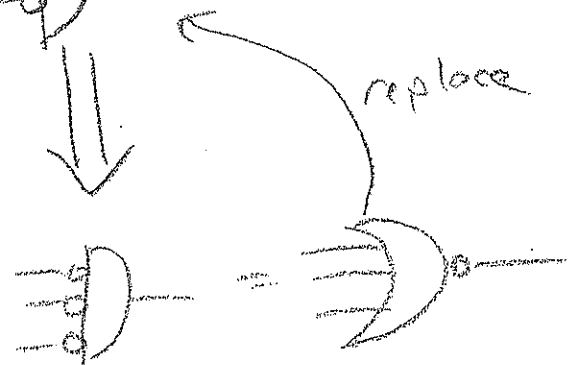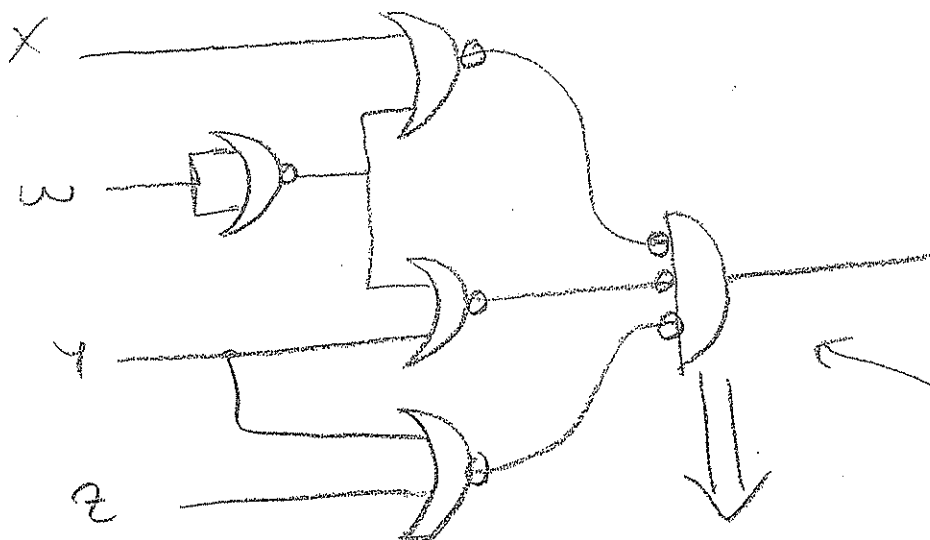

$$x' y' z' = (x + y + z)'$$