 



## Chapter 7 - Sequential Circuits Part 2
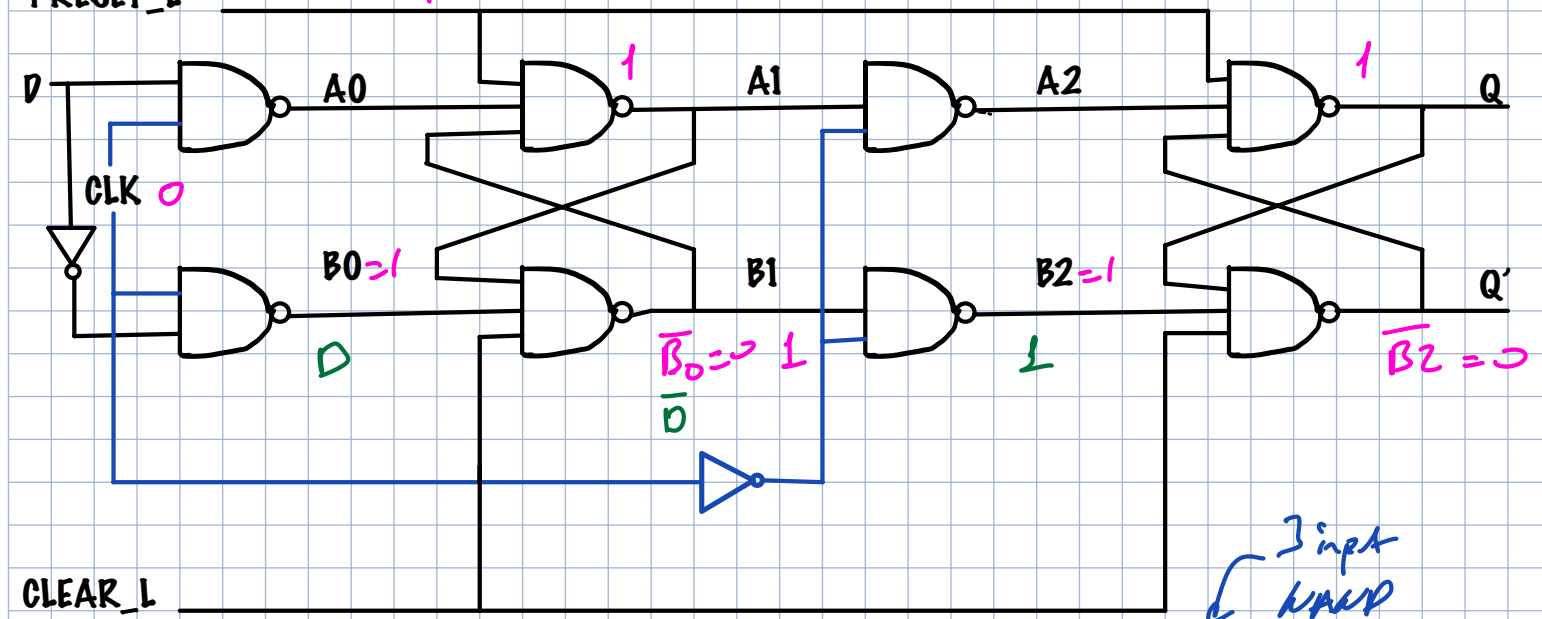
### D-FF with asynchronous clear and preset

*reset* *set*  
*not following the CLK*




- $\text{PRESET\_L} = 0 \rightarrow Q = 1$
- $\text{CLEAR\_L} = 0 \rightarrow Q = 0$
- both cannot be zero at the same time



- $\text{CLK} = 0$ :  $A_0 = 1, B_0 = 1$ 
  - $\text{PRESET\_L} = 0, \text{CLEAR\_L} = 1$ :  $A_1 = 1, B_1 = 0$ 
    - $A_2 = 0, B_2 = 1$ :  $Q = 1, Q' = 0$

- $\text{CLK} = 1$ :  $A_2 = 1, B_2 = 1$ 
  - $\text{PRESET\_L} = 0, \text{CLEAR\_L} = 1$ :  $Q = 1, Q' = 0$

symbol:

 

preset-l or clear-l		a	b	atpt
active	0	0	0	1
	0	0	1	1
	0	1	0	1
	0	1	1	1
inactive	1	0	0	1
	1	0	1	1
	1	1	0	1
	1	1	1	0

*output = a.b*

## VHDL code for D-FF with asynchronous clear and preset

since these operations are asynchronous.


```
process (CLK, CLEAR_L, PRESET_L)
begin
    if PRESET_L = '0' then
        Q <= '1';
    elsif CLEAR_L = '0' then
        Q <= '0';
    elsif falling_edge(CLK) then
        Q <= D;
    end if;
end process;
```

implied  
memory

## VHDL code for negative edge triggered D-FF

```
process (CLK) begin
    if falling_edge(CLK) then
        Q <= D;
        Qn <= not D;
    end if;
end process;
```

otherwise

 


~~Qsyn~~

Can we construct this using D-FF and a few other gates?

only at active  
edge of CLK


D-FF with  
synchronous  
clear

(positive edge triggered)

 


don't plug in CLK

synchronous active low preset

 


both?

 

clear. (D + preset\_L)


clear has higher  
priority than preset

 

clk

Characteristic table:

T	Q(t+1)
0	Q(t)
1	Q'(t)

 


Can we make T-FF from D-FF?

Midterm 11.11.2023

15:00-17:00

compare with D-FF.

T "Toggle" FF (positive edge triggered)

 


$$D = f(T, Q)$$

$$Q(t+1) = D = f(T, Q)$$

T	Q(t)	D
0	0	0
0	1	1
1	0	1
1	1	0

$$D = T \oplus Q = \bar{T}Q + T\bar{Q}$$

symbol:

 

VHDL code for T-FF

inside architecture

```
process(CLK) begin
    if rising_edge(CLK) then
        Q <= D;
    endif;
end process;
D <= Q when T = '0' else not Q;
```

D-FF

XOR

Note: Q & D has to be signal because they appear both at the input & output of this code

architecture ...

signal Q, D: std\_logic;

begin

Qout <= Q;

...

declared as output in entity part of the code

## Characteristic table:


J K	Q(t+1)	
0 0	Q(t)	no change
0 1	0	reset
1 0	1	set
1 1	Q'(t)	toggle

Can we make JK-FF from D-FF?

We know that  $Q(t+1) = D$

What should be D as a function of inputs and output?

JK FF (Jack Kilby)

 

Q/JK

	J			
	00	01	11	10
Q	1		1	1
0				
1	1			
	K			

$$D = f(J, K, Q), \quad Q(t+1) = D$$

J	K	Q	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

## VHDL code for JK-FF

inside architecture

```

process(CLK) begin
    if rising_edge(CLK) then
        Q <= D;
    end if;
end process;
D <= Q when J = '0' and K = '0' else
    '1' when J = '1' and K = '0' else
    '0' when J = '0' and K = '1' else
    not Q;


```

Alternatively, we can use the concatenation operator


```

JK <= J & K;
with JK select
    D <= Q when "00",
    '1' when "10",
    '0' when "01",
    not Q when others;

```

 

## 4-bit register

 

input:  $I = (I3, I2, I1, I0)$

output:  $Q = (Q3, Q2, Q1, Q0)$

How many states?  $2^4 = 16$  *flip-flop outputs*

Number of input combinations?  $2^4 = 16$

Number of output combinations?  $2^4 = 16$

For an n-bit register:

How many states?  $2^n$

Number of input combinations?  $2^n$

Number of output combinations?  $2^n$


Can this register memorize the past?

*Output changes (follows input) at every rising edge of CLK*

VHDL code for 4-bit register

```
entity reg4 is
    port(I: in std_logic_vector(3 downto 0);
         CLK: in std_logic;
         Q: out std_logic_vector(3 downto 0));
end reg4;
```
 
```
architecture reg4arch of reg4 is
begin
    process(CLK) begin
        if rising_edge(CLK) then
            Q<=I;
        end if;
    end process;
end reg4arch;
```



**L=0** hold current values  
**L=1** load new input values

**VHDL code for 3-bit register with load**

```
process (CLK) begin
    if rising_edge (CLK) then
        if L='1' then
            Q<=I;
        end if;
    end if;
end process;
```



*} implied memory*

## Registers

### 4-bit register

### 3-bit register with load

*defined*

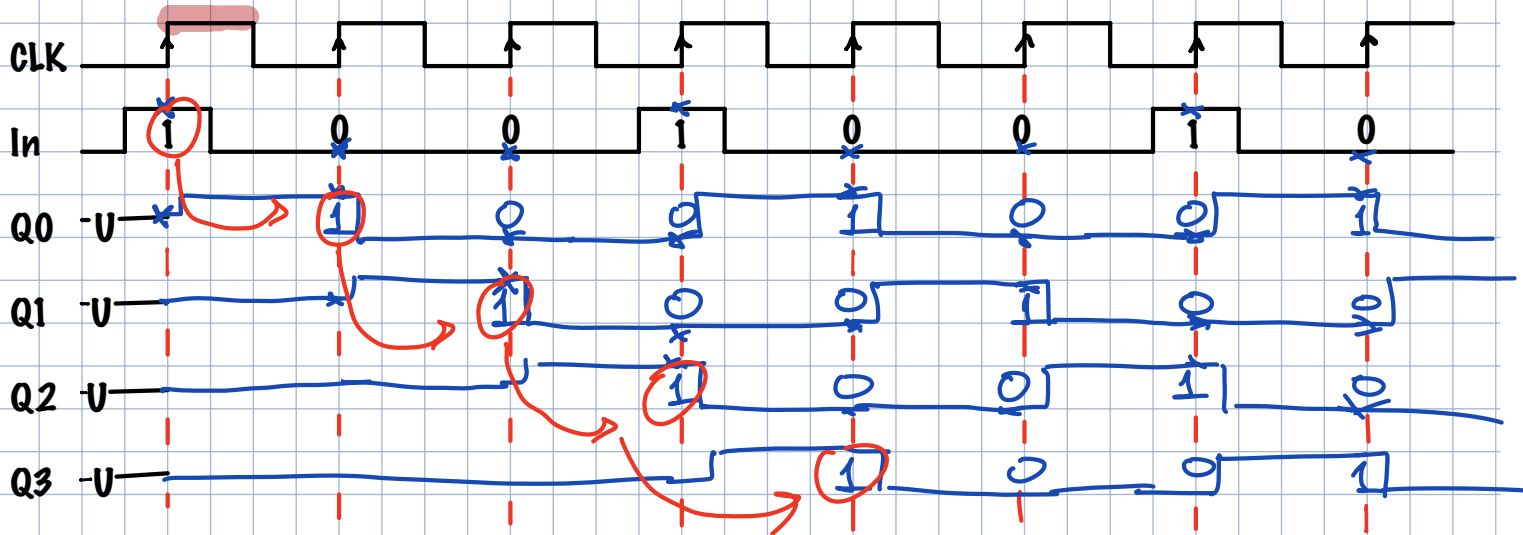 

## 4-bit shift register

### VHDL code for 4-bit shift register

```
architecture shift_arch of shift4 is
    signal Q: std_logic_vector(3 downto 0);
begin
    process(CLK) begin
        if rising_edge(CLK) then
            Q(3) <= Q(2);
            Q(2) <= Q(1);
            Q(1) <= Q(0);
            Q(0) <= In;
        end if;
    end process;
    Qout <= Q(3);
end shift_arch;
```

$Q_3 Q_2 Q_1 Q_0$   
 $Q = 1100, I = 1$

ordering here does not matter

$Q(0) \leftarrow In$   
 $Q(1) \leftarrow Q(0)$   
 $Q(2) \leftarrow Q(1)$   
 $Q(3) \leftarrow Q(2)$

## Alternative VHDL code for 4-bit shift register

```
architecture shift_arch of shift4 is
    signal Q: std_logic_vector(3 downto 0);
begin
    process(CLK) begin
        if rising_edge(CLK) then
            Q<=Q(2 downto 0)&In;  $\rightarrow Q_1^+ Q_2^+ Q_3^+ \leftarrow Q_2^- Q_1^- Q_0^- I_n$ 
        end if;
    end process;
    Qout<=Q(3);
end shift_arch;
```

## What does the following VHDL code represent?

```
entity mystery is
    port(Din: in std_logic_vector(3 downto 0);
          CLK: in std_logic;
          LS,Sin: in std_logic;
          Sout: out std_logic;
          Qout: out std_logic_vector(3 downto 0));
end mystery;
```

```
architecture mystery_arch of mystery is
    signal Q: std_logic_vector(3 downto 0);
begin
    process(CLK) begin
        if rising_edge(CLK) then
            if LS='1' then
                Q<=Din;
            else
                Q<=Q(2 downto 0)&Sin;
            end if;
        end if;
    end process;
    Qout<=Q;
    Sout<=Q(3)
end mystery_arch;
```

