

Number Representation and Arithmetic Circuits

VOLKAN KURSUN

Some material from McGraw Hill

EEE 102 Introduction to Digital Circuit Design


VOLKAN KURSUN

VOLKAN KURSUN

Bilkent University

One-Bit Addition

 - Four possible input combinations and three possible results



(a) The four possible cases

x	y	Carry	Sum
		c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN

Bilkent University

Outline

- Addition of Unsigned Numbers
- Arithmetic Overflow (Unsigned)
- Signed Numbers
- Addition of Signed Numbers
- Subtraction of Signed Numbers
- Arithmetic Overflow (Signed)

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN


Bilkent University

Half Adder

- Half adder: the circuit used for adding two bits


x	y	Carry	Sum
		c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

 

 (c) Circuit

EEE 102 Introduction to Digital Circuit Design



(d) Graphical symbol

VOLKAN KURSUN

Multi-Bit Addition

- Example: add two 5-bit unsigned numbers
- With 5-bits, unsigned numbers in the range of 0 to 2^5-1 (31) can be represented

Generated carries $\rightarrow 1110$

$$\begin{array}{r}
 X = x_4x_3x_2x_1x_0 \quad 01111 \quad (15)_{10} \\
 + Y = y_4y_3y_2y_1y_0 \quad + 01010 \quad + (10)_{10} \\
 \hline
 S = s_4s_3s_2s_1s_0 \quad 11001 \quad (25)_{10}
 \end{array}$$

- At each bit position i , there may be a carry-in coming from the previous bit position $i-1$

Multi-Bit Addition

- At each bit position i , addition operation requires addition of three bits: x_i , y_i , and c_i
- For multi-bit addition, design a logic circuit that has 3 inputs (c_i , x_i , and y_i) and 2 outputs (c_{i+1} and s_i)

Generated carries $\rightarrow 1110$

$$\begin{array}{r}
 X = x_4x_3x_2x_1x_0 \quad 01111 \quad (15)_{10} \\
 + Y = y_4y_3y_2y_1y_0 \quad + 01010 \quad + (10)_{10} \\
 \hline
 S = s_4s_3s_2s_1s_0 \quad 11001 \quad (25)_{10}
 \end{array}$$

Full Adder

- 3 inputs (c_i , x_i , and y_i) and 2 outputs (c_{i+1} and s_i)

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$c_i \backslash x_i y_i$	00	01	11	10
0		1		1
1	1		1	


$$s_i = x_i \oplus y_i \oplus c_i$$

$c_i \backslash x_i y_i$	00	01	11	10
0			1	
1		1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$



Full Adder Implementation

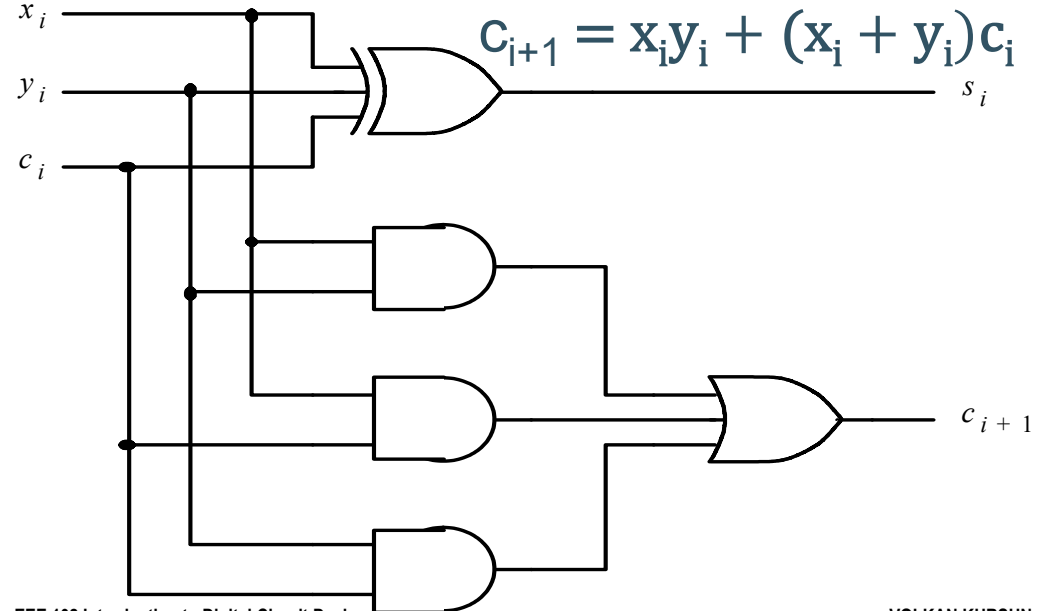- $s_i = x_i \oplus y_i \oplus c_i$, $c_{i+1} = x_i y_i + x_i c_i + y_i c_i$





Decomposed Full Adder Implementation

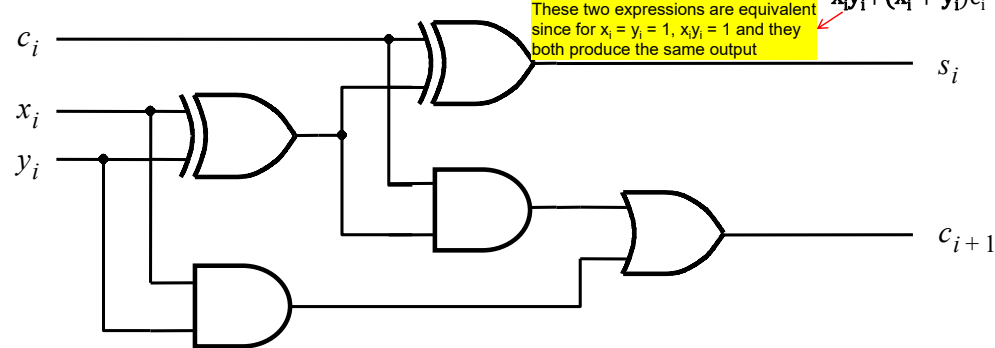 □ A full adder can be constructed using half adders




Decomposed Full Adder Implementation

  Prove $c_{i+1} = x_i y_i + x_i c_i + y_i c_i = x_i y_i + (x_i \oplus y_i) c_i$ using Karnaugh maps





Ripple Carry Adder

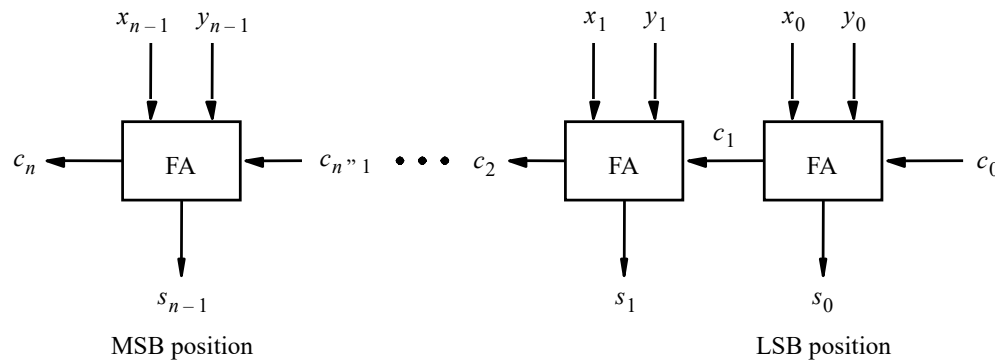□ An n-bit adder can be formed by using n full adders: the carry signals ripple through the full adder stages from right to left



□ Quite slow if n is high but a ripple carry adder is easy to design and compact

4-Bit Ripple Carry Adder

  

4-Bit Adder VHDL Code

```

library ieee;
use ieee.std_logic_signed.all;

entity addnibble is
    port(a,b: in std_logic_vector(3 downto 0);
         y: out std_logic_vector(3 downto 0));
end addnibble;

architecture addarch of addnibble is
begin
    y <= a + b;
end addarch;

```

std_logic_signed package: allows STD_LOGIC signals to be used with arithmetic operators

std_logic_vector type: array of STD_LOGIC data objects


std_logic_vector size: range of array indices

Outline

- Addition of Unsigned Numbers
- Arithmetic Overflow (Unsigned)
- Signed Numbers
- Addition of Signed Numbers
- Subtraction of Signed Numbers
- Arithmetic Overflow (Signed)

8-Bit Ripple Carry Adder

□ Can be designed with two 4-bit adders

 

Unsigned Integers: Addition

- Addition is just like in elementary school. Add bits in each position and carry 1s to more significant bit positions

$$\begin{array}{r}
 00111 \quad 7 \\
 + 00110 \quad 6 \\
 \hline
 01101 \quad 13
 \end{array}$$

- Assume an n-bit architecture with n-bit source operands provided by n-bit registers and the result will be stored in an n-bit register
- Range of unsigned integers that can be represented with n-bits: 0 to $+2^n - 1$
- **OVERFLOW:** if an addition operation produces a result that cannot be correctly represented with n-bits (**result** $> +2^n - 1$), an overflow occurs

Unsigned Integers: Addition

- Examples: **assume an architecture with 5-bit registers** and operands. **Range of unsigned integers** that can be represented with 5-bits: 0 to $+2^5-1 = 0$ to **+31**
- OVERFLOW:** if an unsigned addition operation produces a result that cannot be correctly represented with 5-bits (**result > +31**) an overflow occurs

Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal		Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal	
0	0	1	0	0	0	← Carry bits		1	1	1	1	1	0	← Carry bits	
	0	0	1	1	1	7			0	1	1	1	1	15	
	+ 1	0	1	0	0	+ 20			+ 1	0	0	0	1	+ 17	
0	1	1	0	1	1	27	Correct	1	0	0	0	0	0	Overflow	
Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal		Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal	
0	0	0	0	0	0	← Carry bits		1	1	1	1	0	0	← Carry bits	
	0	1	1	1	1	15			1	1	0	1	1	27	
	+ 1	0	0	0	0	+ 16			+ 0	1	1	1	0	+ 14	
0	1	1	1	1	1	31	Correct	1	0	1	0	0	1	Overflow	

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN

Outline

Bilkent University

- Addition of Unsigned Numbers
- Arithmetic Overflow (Unsigned)
- Signed Numbers
- Addition of Signed Numbers
- Subtraction of Signed Numbers
- Arithmetic Overflow (Signed)

Unsigned Integers: Addition

- OVERFLOW:** if an addition operation produces a result that cannot be correctly represented with 5-bits (**result > +31**) an overflow occurs
- OBSERVATION:** In unsigned addition overflow is captured by the carry output from the most significant bit position. **If Cout_4 = 1, there is an overflow. If Cout_4 = 0, there is NO overflow**
- Carry output from the most significant bit position** (Cout_(n-1)) can be used as the **overflow flag** for unsigned addition

Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal		Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal	
0	0	1	0	0	0	← Carry bits		1	0	1	1	0	0	← Carry bits	
	0	0	1	1	1	7			1	0	0	1	1	19	
	+ 1	0	1	0	0	+ 20			+ 1	0	1	1	0	+ 22	
0	1	1	0	1	1	27	Correct	1	0	1	0	0	1	Overflow	
Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal		Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal	
0	1	1	0	0	0	← Carry bits		1	1	1	1	0	0	← Carry bits	
	0	1	1	1	1	15			1	1	0	1	1	27	
	+ 0	1	1	0	0	+ 12			+ 0	1	1	1	0	+ 14	
0	1	1	0	1	1	27	Correct	1	0	1	0	0	1	Overflow	

EEE 102 Introduction to Digital Circuit Design

VOLKAN KURSUN

VOLKAN KURSUN

Bilkent University

Signed Integers (2's-Complement)

Most significant bit is the sign bit:

MSB = 0: positive integer

MSB = 1: negative integer

A number is negated by inverting all the bits and adding 1 to the inverted number: 2's complement representation

Signed Number Representation

- Two's complement representation
 - Used by modern computers
 - Example: 0b 101 = -3
- Properties
 - Only one zero
 - One more negative number than positive number
 - All negative numbers have a 1 in the **most significant bit** (MSB)

Two's Complement
000 = +0
001 = +1
010 = +2
011 = +3
100 = -4
101 = -3
110 = -2
111 = -1

Signed Integers (2s-Complement)

Decimal equivalent of an n-bit signed binary number:

$$x = -x_{n-1}2^{n-1} + x_{n-2}2^{n-2} + \dots + x_12^1 + x_02^0$$

Range: -2^{n-1} to $+2^{n-1} - 1$

- Range with 32 bits: -2^{31} to $+2^{31} - 1$
-2,147,483,648 to +2,147,483,647
- Example:
0b 1111 1111 1111 1111 1111 1111 1100
= $-1 \times 2^{31} + 1 \times 2^{30} + \dots + 1 \times 2^2 + 0 \times 2^1 + 0 \times 2^0$
= $-2,147,483,648 + 2,147,483,644 = (-4)_{10}$

Signed Negation

- To negate a number: complement all digits and add 1
Complement (or invert) means $1 \rightarrow 0, 0 \rightarrow 1$

$$x + \bar{x} = 0b1111\dots111 = -1$$

$$\bar{x} + 1 = -x$$

- Example: negate +2 (write -2 in binary)
+2 = 0b 0000 0000 ... 0010
-2 = 0b 1111 1111 ... 1101 + 0b 0000 0000 ... 0001
= 0b 1111 1111 ... 1110

Signed Binary ↔ Decimal Conversion

Signed Binary → Decimal

0b1001010 = ?_{ten}

Binary Digit	Decimal Value
0	0 x 2 ⁰ = 0
1	1 x 2 ¹ = 2
0	0 x 2 ² = 0
1	1 x 2 ³ = 8
0	0 x 2 ⁴ = 0
0	0 x 2 ⁵ = 0
1	-1 x 2 ⁶ = -64
$\Sigma = -54_{\text{ten}}$	

Decimal → Signed Binary

-54 = 0b?

Decimal	Binary Digit
-54/2 = -27	0
-27/2 = -14	1
-14/2 = -7	0
-7/2 = -4	1
-4/2 = -2	0
-2/2 = -1	0
-1/2 = -1	1
-1/2 = -1	1: repeats
Collect → remainder bits	0b1001010

Repeating sign bit

Decimal → Binary Conversion Notes

Positive Decimal → Binary Negative Decimal → Binary

Continue division until quotient and remainder both become 0 and repeat (sign bit 0 repeats)

Continue division until quotient becomes -1, remainder becomes 1, and they repeat (sign bit 1 repeats)

Decimal	Binary Digit	Decimal	Binary Digit
+15		-15	
+15/2 = +7	1	-15/2 = -8	1
+7/2 = +3	1	-8/2 = -4	0
+3/2 = +1	1	-4/2 = -2	0
+1/2 = 0	1	-2/2 = -1	0
0/2 = 0	0	-1/2 = -1	1
0/2 = 0	0	-1/2 = -1	1
Sign bit repeats		Sign bit repeats	
Collect → remainder bits	0b01111	Collect → remainder bits	0b10001
	Repeating sign bit		Repeating sign bit

Outline

- Addition of Unsigned Numbers
- Arithmetic Overflow (Unsigned)
- Signed Numbers
- Addition of Signed Numbers
- Subtraction of Signed Numbers
- Arithmetic Overflow (Signed)

2's Complement Addition

□ The carry output from the sign-bit position (MSB) is ignored

$\begin{array}{r} (+5) \\ + (+2) \\ \hline (+7) \end{array}$	$\begin{array}{r} 0101 \\ + 0010 \\ \hline 0111 \end{array}$	$\begin{array}{r} (-5) \\ + (+2) \\ \hline (-3) \end{array}$	$\begin{array}{r} 1011 \\ + 0010 \\ \hline 1101 \end{array}$
$\begin{array}{r} (+5) \\ + (-2) \\ \hline (+3) \end{array}$	$\begin{array}{r} 0101 \\ + 1110 \\ \hline 10011 \end{array}$	$\begin{array}{r} (-5) \\ + (-2) \\ \hline (-7) \end{array}$	$\begin{array}{r} 1011 \\ + 1110 \\ \hline 11001 \end{array}$
<p>Cin and Cout of the MSB position are identical (both are 1): therefore, Cout can be ignored</p>	<p>↑ ignore</p>	<p>Cin and Cout of the MSB position are identical (both are 1): therefore, Cout can be ignored</p>	<p>↑ ignore</p>

Outline

- Addition of Unsigned Numbers
- Arithmetic Overflow (Unsigned)
- Signed Numbers
- Addition of Signed Numbers
- Subtraction of Signed Numbers
- Arithmetic Overflow (Signed)

2's Complement Subtraction


- Take the 2's complement of the subtrahend (the second operator) and add it to the minuend (the first operator)

$$\begin{array}{r}
 (+5) \quad 0101 \\
 - (-2) \quad -1110 \\
 \hline
 (+7) \quad 0111
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 0010 \\
 \hline
 0111
 \end{array}$$

$$\begin{array}{r}
 (-5) \quad 1011 \\
 - (-2) \quad -1110 \\
 \hline
 (-3) \quad 1101
 \end{array}
 \Rightarrow
 \begin{array}{r}
 1011 \\
 + 0010 \\
 \hline
 1101
 \end{array}$$

Adder/Subtractor

 - Only difference between addition and subtraction: 2's complement of the second operand is added to the first operand in case of subtraction
- 2's complement: invert all bits and add 1



2's Complement Subtraction

- Take the 2's complement of the subtrahend (the second operator) and add it to the minuend (the first operator)
- The carry output from the sign-bit position (MSB) is **ignored**

$$\begin{array}{r}
 (+5) \quad 0101 \\
 - (+2) \quad -0010 \\
 \hline
 (+3) \quad 1001
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 1001
 \end{array}$$

Cin and Cout of the MSB position are identical (both are 1): therefore, Cout can be ignored

$$\begin{array}{r}
 (-5) \quad 1011 \\
 - (+2) \quad -0010 \\
 \hline
 (-7) \quad 1001
 \end{array}
 \Rightarrow
 \begin{array}{r}
 1011 \\
 + 1110 \\
 \hline
 1001
 \end{array}$$

Cin and Cout of the MSB position are identical (both are 1): therefore, Cout can be ignored

Outline

- Addition of Unsigned Numbers
- Arithmetic Overflow (Unsigned)
- Signed Numbers
- Addition of Signed Numbers
- Subtraction of Signed Numbers
- Arithmetic Overflow (Signed)

Signed Integers: Addition

Assume an architecture with n-bit signed source operands provided by n-bit registers and the signed result will be stored in an n-bit register

Range of signed integers that can be represented with n-bits: -2^{n-1} to $+2^{n-1} - 1$

1. POSITIVE OVERFLOW: if addition of **two positive numbers produces** a large positive result that cannot be correctly represented with n-bits (**result > $+2^{n-1}-1$**), a **positive overflow** occurs

2. NEGATIVE OVERFLOW: if addition of **two negative numbers produces** a small negative result that cannot be correctly represented with n-bits (**result < -2^{n-1}**), a **negative overflow** occurs

Signed Integers: Addition

- Examples: assume an architecture with 5-bit registers and operands: **range of signed integers** that can be represented with 5-bits: -2^4 to $+2^4-1 = -16$ to $+15$
- OVERFLOW:** if an addition operation produces a result that cannot be correctly represented with 5-bits (**result > +15** or **result < -16**) a **positive** or **negative overflow** occurs

Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal		Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal	
0	0	1	0	0	0	← Carry bits		1	0	1	1	0	0	← Carry bits	
		0	0	1	1	+7				1	0	0	1	-13	
		+1	0	1	0	+ -12				+1	0	1	1	+ -10	
0	1	1	0	1	1	-5	Correct	1	0	1	0	0	1	Negative Overflow	
Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal		Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal	
0	1	1	0	0	0	← Carry bits		1	1	1	1	0	0	← Carry bits	
		0	1	1	1	+15				1	1	0	1	-5	
		+0	1	1	0	+ +12				+0	1	1	1	+ +14	
0	1	1	0	1	1	Positive Overflow		1	0	1	0	0	1	+9	Correct

Signed Integers: Addition

- OBSERVATION: In signed addition **overflow** is captured by the carry output from and carry in to the most significant bit position. If **Cout_4Cin_4 = 0b01, there is positive overflow**. If **Cout_4Cin_4 = 0b10, there is negative overflow**. If **Cout_4Cin_4 = 0b00 or 0b11, there is NO overflow**
- Carry output from and carry in to the most significant bit position** (Cout_(n-1) and Cin_(n-1)) are used to identify the overflow conditions in signed addition

Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal		Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal	
0	0	1	0	0	0	← Carry bits		1	0	1	1	0	0	← Carry bits	
		0	0	1	1	+7				1	0	0	1	-13	
		+1	0	1	0	+ -12				+1	0	1	1	+ -10	
0	1	1	0	1	1	-5	Correct	1	0	1	0	0	1	Negative Overflow	
Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal		Cout_4	Cin_4	Cin_3	Cin_2	Cin_1	Cin_0	Decimal	
0	1	1	0	0	0	← Carry bits		1	1	1	1	0	0	← Carry bits	
		0	1	1	1	+15				1	1	0	1	-5	
		+0	1	1	0	+ +12				+0	1	1	1	+ +14	
0	1	1	0	1	1	Positive Overflow		1	0	1	0	0	1	+9	Correct

Signed Overflow Conditions

- Signed overflow** conditions can be captured by checking the carry output from and carry in to the most significant (sign) bit position during addition

$$\text{Overflow} = \text{Cout}_{(n-1)} \oplus \text{Cin}_{(n-1)}$$

Cout_(n-1)	Cin_(n-1)	Overflow
0	0	0 → NO overflow
0	1	1 → Positive overflow
1	0	1 → Negative overflow
1	1	0 → NO overflow

Signed Integers: Subtraction

- Subtraction (M-S): the second operand (subtrahend) is negated and added to the first operand (minuend)
 - $M - S = M + (-S) = M + (S' + 1)$: take the 2's complement of the subtrahend and add it to the minuend
- Add/subtract = 0: control signal for addition. Output = $A + B$
- Add/subtract = 1: control signal for subtraction. Output = $A + \bar{B} + 1 = A - B$

