
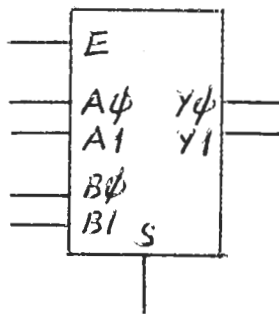


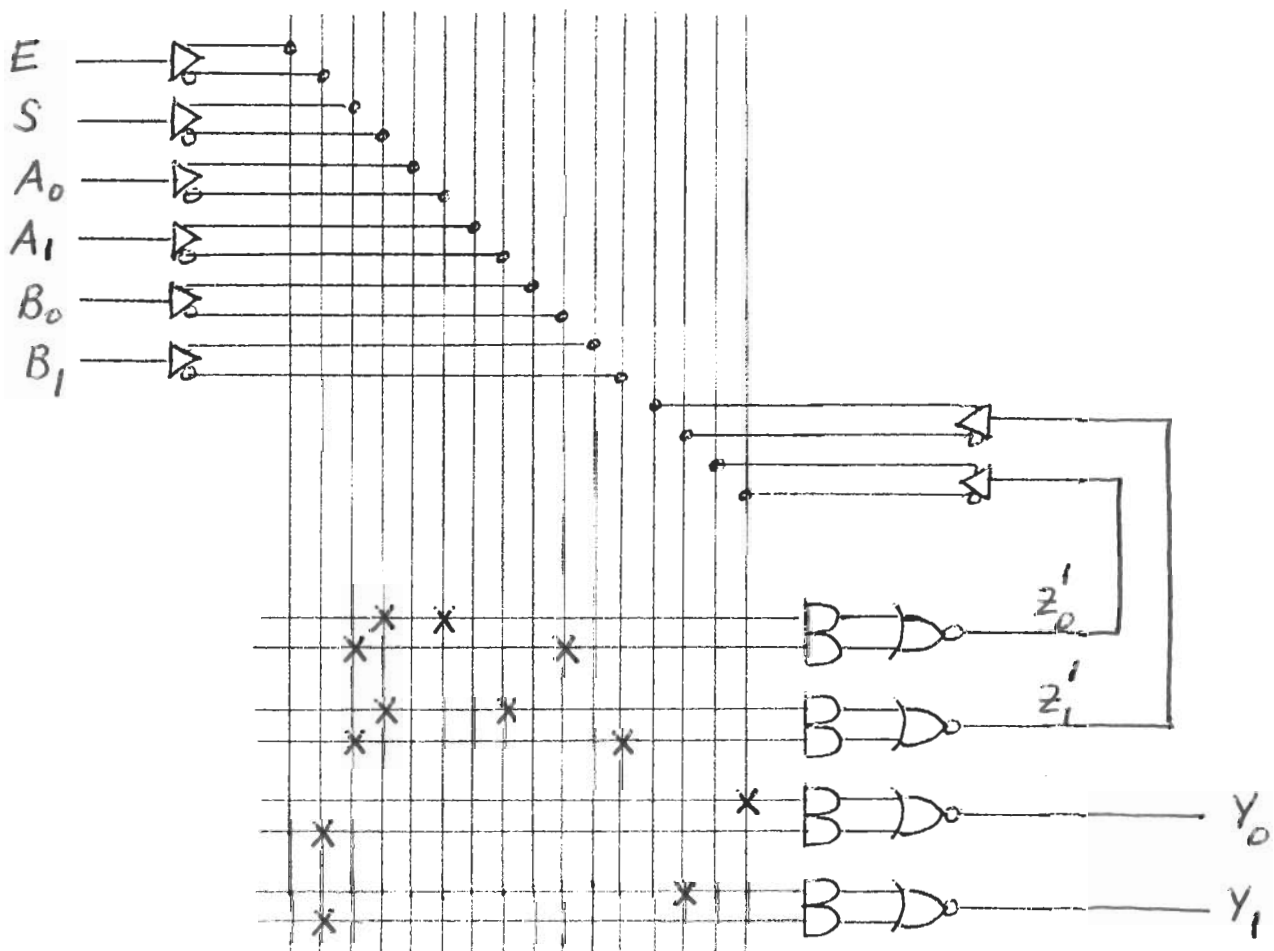1. Below is the block diagram and the function table of a 2-to-1 2-bit generic multiplexer with enable input.




E	S	Y1	Y0
0	x	0	0
1	0	A1	A0
1	1	B1	B0

Implement this multiplexer using the following PAL without using any additional gates. Note that PAL outputs are inverted.



SOLUTION :

$$Y_i = E_i (S' A_i + S B_i)$$

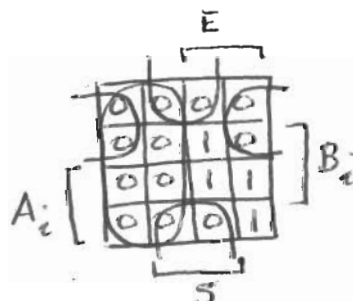

$$Y_i' = E' + S' A_i' + S B_i'$$

2. Implement a 1-bit full adder using a generic 4-to-1 2-bit multiplexer using no more than one additional gate.

SOLUTION

MUX :

S_1	S_0	F_0	F_1
0	0	A_0	A_1
0	1	B_0	B_1
1	0	C_0	C_1
1	1	D_0	D_1


FULL ADDER :

X	Y	C_{IN}	Z	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Let $XY = S_1 S_0$, $Z = F_0$, $C_{OUT} = F_1$.

FULL ADDER :

S_1	S_0	F_0	F_1
0	0	C_{IN}	0
0	1	C_{IN}	C_{IN}
1	0	C_{IN}	C_{IN}
1	1	C_{IN}	1

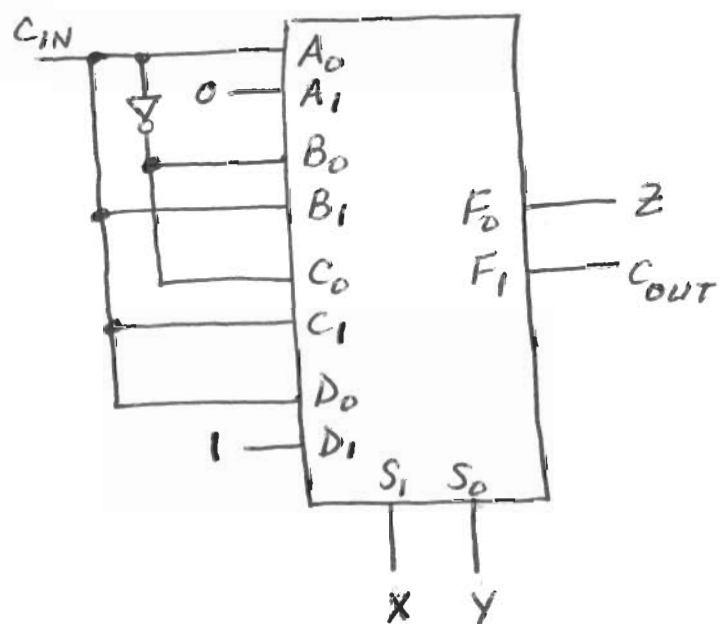


3. Consider the following synchronous machine.

a) Draw the state diagram with the following state assignment

Q_1	Q_0	State
0	0	A
0	1	B
1	0	C
1	1	D

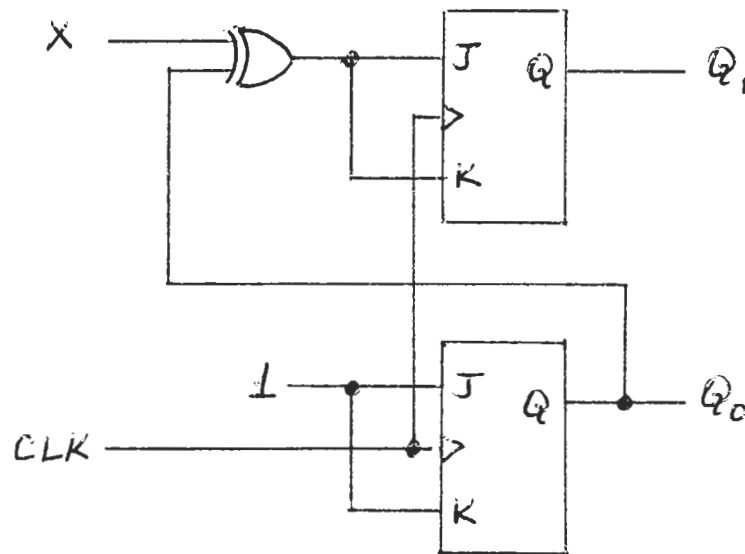
b) Assuming $Q_1 = Q_0 = 0$ initially, find the state sequence corresponding to the following input sequence.

X : 0 0 0 0 0 1 1 1 0 0 1 0
 State: A B C D A D C B C D C D



SOLUTION:

Q_1	Q_0	X	$J_1 = K_1$	$J_0 = K_0$	Q_1^*	Q_0^*
0	0	0	0	1	0	1
0	0	1	1	1	1	1
0	1	0	1	1	1	0
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	1	1	0	1
1	1	0	1	1	0	0
1	1	1	0	1	1	0

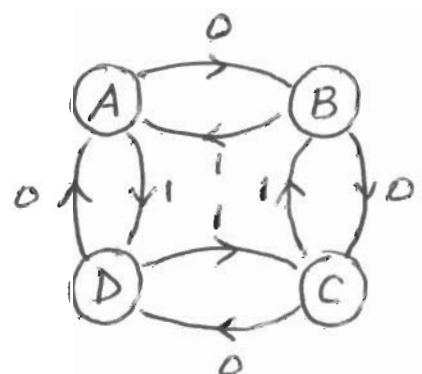

4. Design a Mealey machine with one input X and one output Y such that $Y=1$ if the present input is the same as the input two clock periods before, and $Y=0$ otherwise. Use only two D-flip flops. Assume that the initial state is $Q_1=Q_0=0$. A typical input, output sequence is given below.

$X: 0\ 0\ 0\ 1\ 0\ 0\ 1\ 0\ 1\ 1\ 1\ 0\ 1\ 0\ 0\ 0$


$Y: *\ * \ 1\ 0\ 1\ 0\ 0\ 1\ 1\ 0\ 1\ 0\ 1\ 1\ 0\ 1$

SOLUTION :

States :

S_{00} : Prev. two inputs are 00	} Use as state codes
S_{01} : " " " " 01	
S_{10} : " " " " 10	
S_{11} : " " " " 11	

State Diagram :

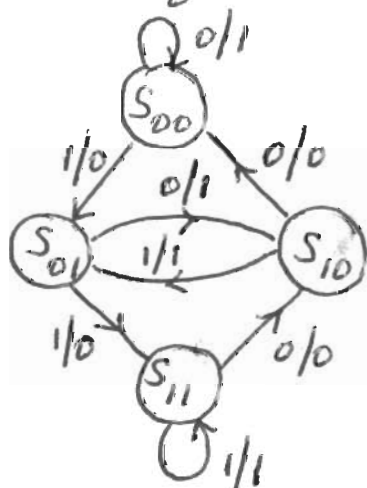

Next State/Output Table :

Q_1	Q_0	X	Q_1^*	Q_0^*	Y
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	1	1

$$D_0 = Q_0^* = X$$

$$D_1 = Q_1^* = Q_0$$

$$Y = (X \oplus Q_1)'$$

