

15-12-2009
BILKENT UNIVERSITY
Department of Electrical and Electronics Engineering
EEE102 Introduction to Digital Circuit Design
Midterm Exam II
SOLUTION

Surname: _____

Name: _____

ID-Number: _____

Section Number: _____


Signature: _____

Duration is 120 minutes. Solve all 5 questions. Show all your work.
No books, notes, or calculators.

Q1 (20 points)	
Q2 (20 points)	
Q3 (20 points)	
Q4 (20 points)	
Q5 (20 points)	
Total	











Question 1-(20 pts):

 (a) (10 pts) The pin diagram and function description of a 4-bit comparator is given below.



Use five of the above 4-bit comparator modules to design one 16-bit comparator.

Solution:

          


$G = 1$ if $A > B$
 $= 0$ otherwise
 $E = 1$ if $A = B$
 $= 0$ otherwise
 $S = 1$ if $A < B$
 $= 0$ otherwise

Question 1-(20 pts) - Continued:


(b) (5 pts) Using a positive edge-triggered JK flip-flop and one or more additional gates, show how to implement a negative edge-triggered T flip-flop with Enable.

Solution:

 


(c) (5 pts) Show how to implement a D latch using one or more additional simple gates and an SR latch with enable.

Solution:

 

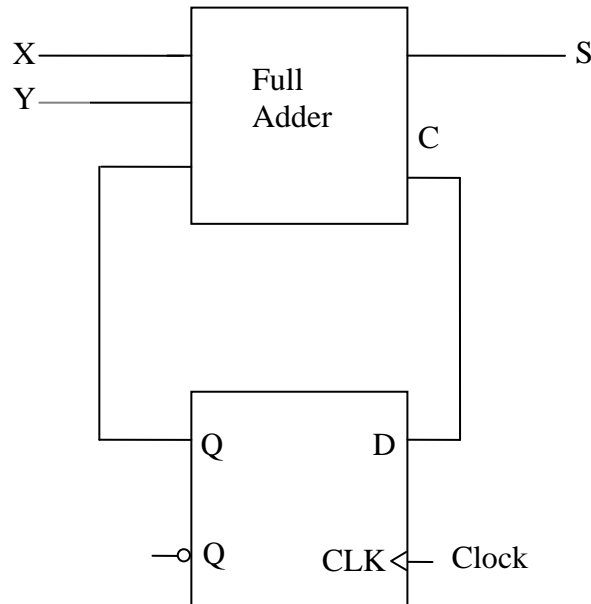Question 2-(20 pts):

A sequential circuit (FSM) has one flip-flop Q, two inputs X and Y, and one output S. It consists of a full-adder circuit connected to a D flip-flop, as shown below. Draw the state/output diagram, and write the next state table and output table of this sequential circuit. Assume that at Power ON Q is '0'. (Note: This circuit is a serial adder. S is equal to the sum of present X, present Y, and the carry at the last clock tick)



What is the value of Q between the 6th and 7th clock ticks, if the values of X and Y at the first 6 clock ticks are as given in the following table. Explain.

Clock tick	1	2	3	4	5	6
X	0	0	1	0	1	1
Y	1	1	1	0	1	1

Solution:

This is a serial adder which keeps the carry in its memory Q.


State of this FSM is the value of the carry. It has 2 states.

S0 = carry is '0'

S1 = carry is '1'

State encoding

State	Q
S0	0
S1	1

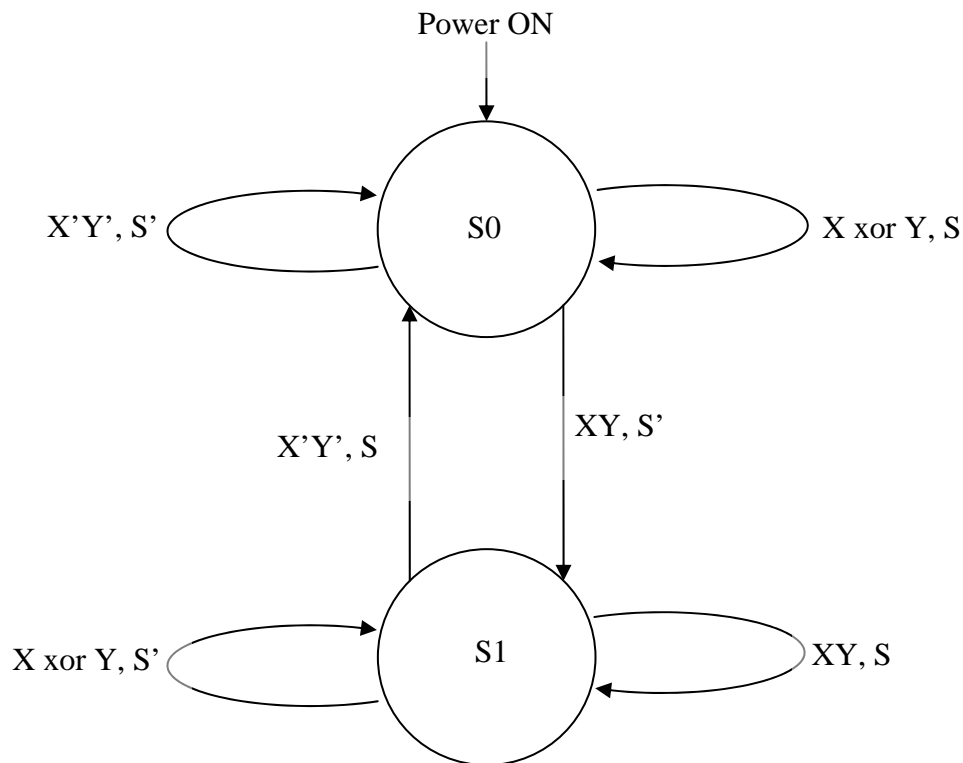

Next state and excitation table

Q	X (tick)	Y (tick)	$Q^* = D$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Optionally one can just write $D = XY + XQ + YQ$

Output table

Q	X (present)	Y (present)	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Optionally one can just write $S = X \oplus Y \oplus Q$

Clock tick	1	2	3	4	5	6
X	0	0	1	0	1	1
Y	1	1	1	0	1	1
Q right after the tick (carry)	0	0	1	0	1	1

Therefore between 6th and 7th ticks $Q = 1$.

Question 3-(20 pts):


Design and draw a synchronous FSM with two D flip-flops which has one input X, such that, when X = '0' the state of the FSM stays the same, and when X = '1' the FSM goes through the state transitions from "00" to "01", to "11", to "10", back to "00" and repeats. Output, F, is '1' if X = '0' and the state is "10", otherwise output is '0'. At Power ON the state should be "00". Is this FSM self-starting? Explain.

(Write state encoding, draw the state/output diagram, write next state table, excitation table, and output table, minimize the circuits, draw the circuit including initialization).

Solution:



State encoding

State	Q1	Q0
S0	0	0
S1	0	1
S2	1	0
S3	1	1

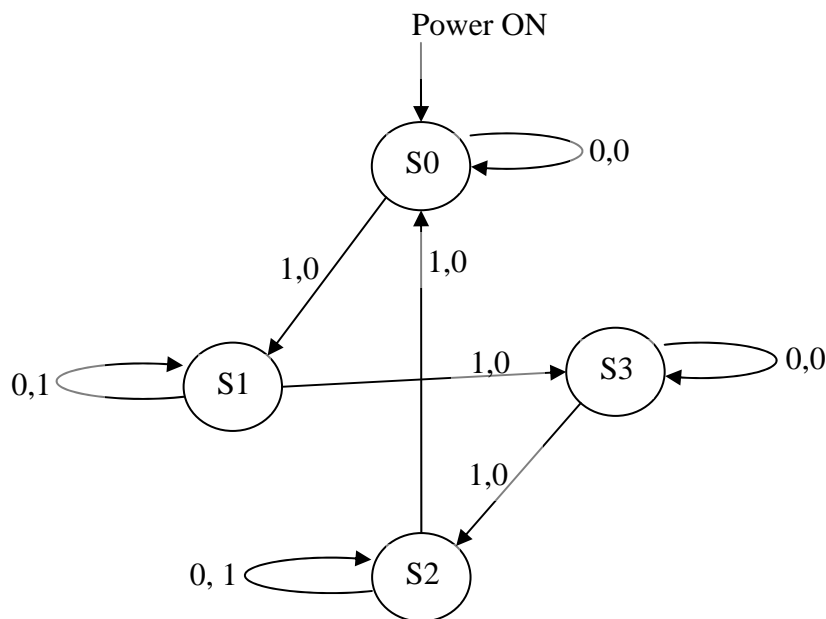

Next state and excitation table

Q ₁	Q ₀	X (tick)	Q ₁ * = D ₁	Q ₀ * = D ₀
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

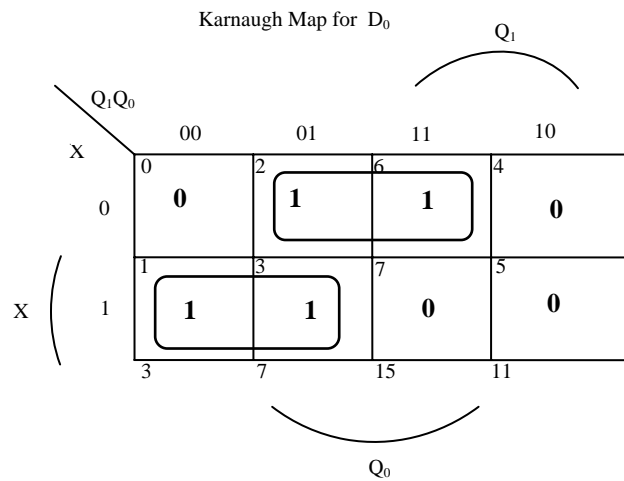 


Output table

Q_1	Q_0	X (present)	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

No need for a karnaugh map. $F = Q_1Q_0'X$

Circuit including initialization

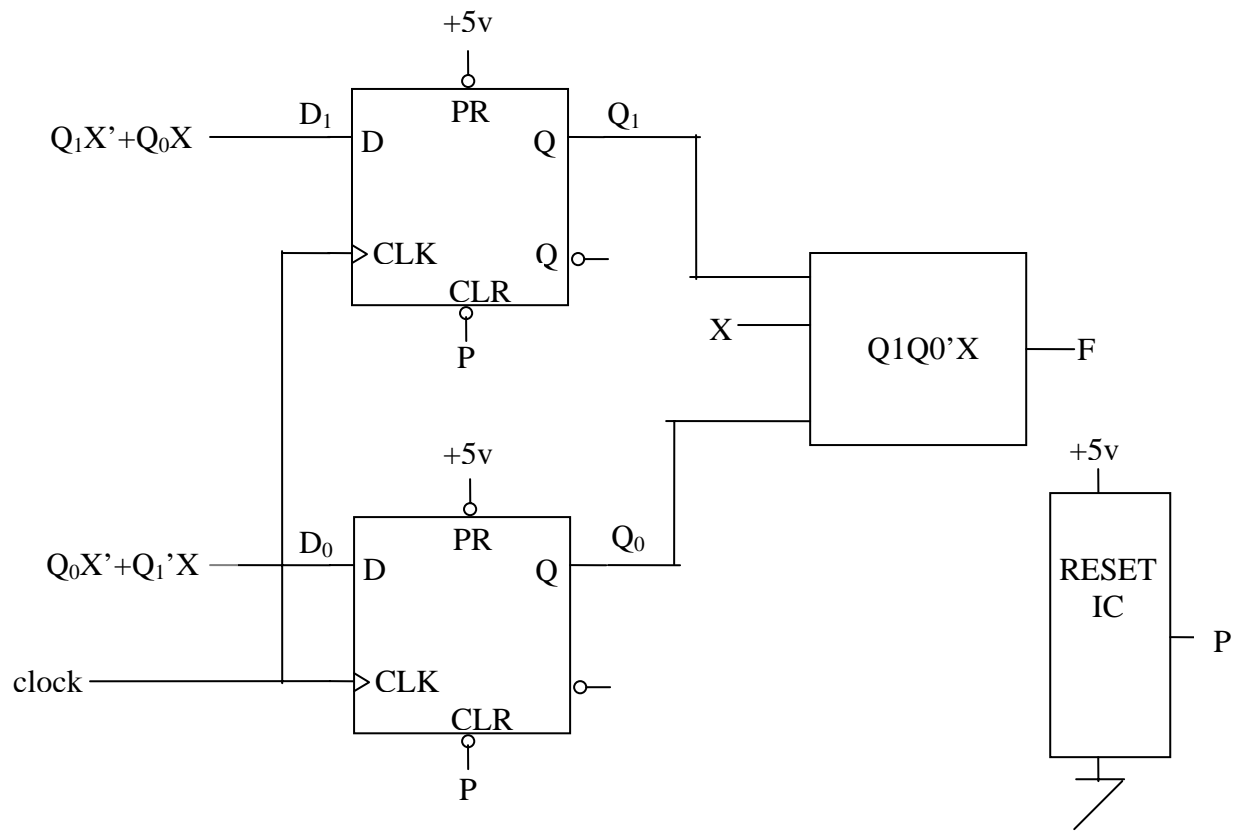

Question 4 (20 pts):

Write VHDL code to implement the 74x148-like 8-input priority encoder. The entity is provided to you below. All of the signals have “_L” indicating their active-low operations.

entity V74x148 is

```
port( E_L: in STD_LOGIC;
      I_L: in STD_LOGIC_VECTOR(7 downto 0);
      A_L: out STD_LOGIC_VECTOR(2 downto 0);
      EO_L: out STD_LOGIC;
      GS_L: out STD_LOGIC);
```

end V74x148;

-- Write the architecture of your code below --

Solution:

-- The architecture is provided on page 416 of the textbook.--

architecture V74x148p of V74x148 is

```
signal EI: std_logic;           -- active-high version of input
signal I: std_logic_vector(7 downto 0); -- active-high version of inputs
signal EO, GS: std_logic;      -- active-high version of outputs
signal A: std_logic_vector(2 downto 0); -- active-high version of outputs
```

begin

```
process (EI_L, I_L, EI, EO, GS, I, A)
```

```
variable j: INTEGER range 7 downto 0;
```

```
begin
```

```
    EI <= not EI_L;    -- convert inputs
```

```
    I <= not I_L;      -- convert inputs
```

```
    EO <= '1'; GS <= '0'; A <= "000";
```

```
    if (EI) = '0' then EO <= '0';
```

```
    else for j in 7 downto 0 loop
```

```
        if I(j) = '1' then
```

```
            GS <= '1'; EO <= '0'; A <= CONV_STD_LOGIC_VECTOR(j,3);
```

```
            exit;
```

```
        endif;
```

```
    end loop;
```

```
    end if;
```

```
    EO_L <= not EO; -- convert output
```

```
    GS_L <= not GS; -- convert output
```




```
    A_L <= not A;    -- convert outputs
```

```
end process;
```

```
end V74x148p;
```

Question 5 (20 pts):**Implement $F = (A \oplus B).C' + AB$** **a) (4 pts) using a generic 8-to-1 multiplexer and minimum number of additional simple gates,****Solution:**


A	B	C	$(A \oplus B).C' + AB$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

   **b) (4 pts) using a generic 4-to-1 multiplexer and minimum number of additional simple gates,****Solution:****c) (4 pts) using a generic 2-to-1 multiplexer and minimum number of additional simple gates,****Solution:**

Question 5-(20 pts) - Continued:


d) (4 pts) using one 74X138 decoder and minimum number of additional simple gates.
(note that 74X138 is a 3-to-8 binary decoder with active low outputs and with three enables, one active high and two active low),

Solution:

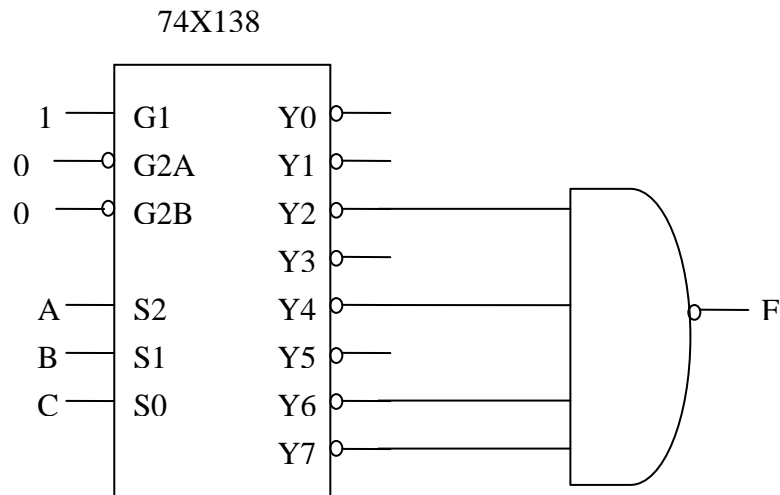

e) (4 pts) using two 2-to-4 generic decoders and minimum number of additional simple gates.

Solution:

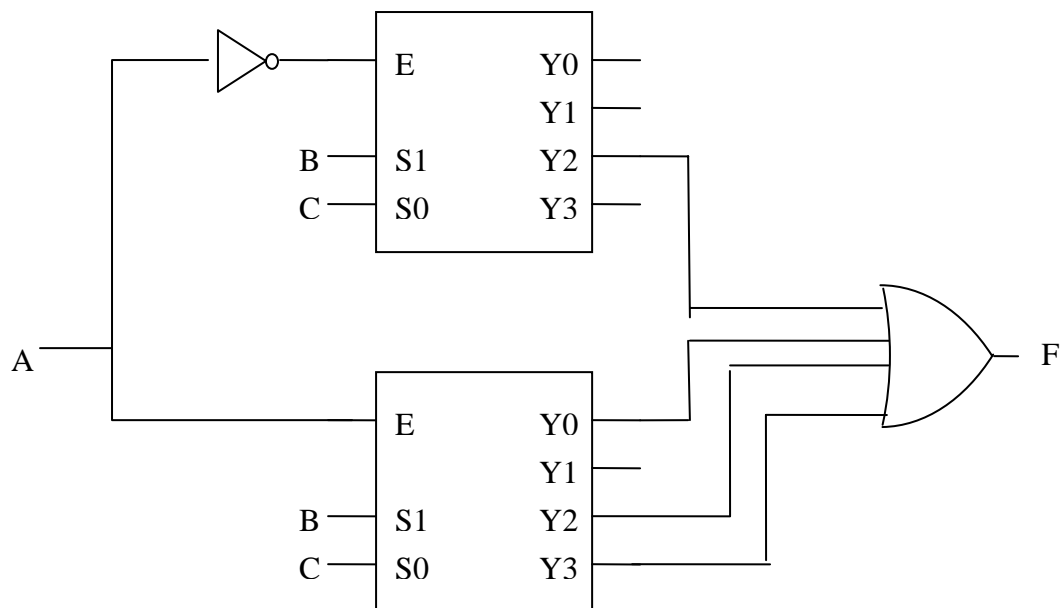

ENTITY DECLARATION

```
entity entity_name is
    generic ( constant_names : constant type;
              constant_names : constant type;
              ...
              constant_names : constant type);
    port ( signal_names : mode signal_type;
           signal_names : mode signal_type;
           ...
           signal_names : mode signal_type);
end entity_name;
```

ARCHITECTURE DEFINITIONS

```
architecture architecture-name of entity-name is
    type declarations
    signal declarations
    constant declarations
    function definitions
    procedure definitions
    component declarations
begin
    concurrent statement
    ...
    concurrent statement
end architecture-name;
```

COMPONENT DECLARATION

```
component component_name
    port ( signal_names : mode signal type;
           signal_names : mode signal type;
           ...
           signal_names : mode signal type);
end component;
```

COMPONENT INSTANTIATION

```
label: component_name port map (signal1, signal2, ..., signaln);
or,
label: component_name port map (port1 => signal1, port2 => signal2, ..., portn => signaln);
```

DATAFLOW TYPE STATEMENTS:**Simple concurrent assignment statement**

```
signal_name <= expression;
```

Conditional concurrent assignment statement

```
signal_name <=
    expression when boolean-expression else
    expression when boolean-expression else
    ...
    expression when boolean-expression else
    expression;
```

with-select statement

```
with expression select
    signal_name <= signal_value when choices,
    signal_name <= signal_value when choices,
    ...
    signal_name <= signal_value when choices;
```

Note that **conditional concurrent assignment statement** and **with-select statement** cannot be used in a process statement. Instead, in a process, one can use the sequential conditional assignment statements **if** and **case**.

BEHAVIORAL TYPE STATEMENTS:**process statement**

```
process(signal_name, signal_name, ..., signal_name)
    type_declarations
```

```

        variable declarations
        constant declarations
begin
    sequential-statement
    ...
    sequential-statement
end process;
Simple sequential assignment statement
signal_name <= expression;
Simple variable assignment statement
variable_name := expression;
if statement in its general form
if boolean_expression then sequential_statements
elsif boolean_expression then sequential_statements
...
elsif boolean_expression then sequential_statements
else sequential_statements
end if;
Note that you may not use the else and/or the elsif.
case-when statement
case expression is
    when choices => sequential_statements
    ...
    when choices => sequential_statements
end case;
loop statement
loop
    sequential_statement
    ...
    sequential_statement
end loop;
for-loop statement
for identifier in range loop
    sequential_statement
    ...
    sequential_statement
end loop;
while statement
while boolean_expression loop
    sequential_statement
    ...
    sequential_statement
end loop;

```

Note that the **if**, **case**, **loop**, **for**, and **while** statements are called sequential statements and they can only be used in a process statement. Also note that each **process** is one concurrent statement.

If the “ieee.std_logic_arith.all” and “ieee.std_logic_unsigned.all” packages are included then + and – operators for addition and subtraction can be used for UNSIGNED binary, SIGNED binary, and STD_LOGIC_VECTOR types.

Concatenation operator & is used as follows: If A and B are 2 bit numbers then A&B is a four bit number with A being more significant.