

Bilkent University

EEE 102 Digital Design Midterm Exam

12 November 2020, 14:30-16:30

Student Name:

Signature:

I hereby declare that this exam is written by me and is a result of my own work. I am aware of the fact that violation of these clauses is regarded as cheating and can result in annulment of the examination in accordance with the regulations of Bilkent University.

Grade:

1.

2.

3.

4.

1. (15 pts) Short answer questions

What are the binary equivalents of the following decimal numbers?

$$19 = 10011$$

$$1023 = 1111111111$$

$$0.5 = 0.1$$

$$2.3 = 10.01001$$

$$0.3$$

$$0.6$$

$$1.2$$

$$0.4$$

$$0.8$$

$$1.6$$

What are the decimal equivalents of the following signed (two's complement) numbers?

$$001101 = 13$$

$$010001 = 17$$

$$110001 = -32 + 17 = -15$$

What are the hexadecimal equivalents of the following binary numbers?

$$0010101 = 15$$

$$00111100 = 3C$$

$$0110.1100 = 6.C$$

What are the binary equivalents of the following hexadecimal numbers?

$$E2 = 11100010$$

$$F92 = 111110010010$$


What is the result of the following 4-bit signed (two's complement) addition? (3 pts)

$$1100 + 1111 = 1011$$

$$(-4) + (-1) = (-5) \quad \text{result is correct}$$

no overflow

 2. (25 pts) For the CMOS circuit below, fill in the table. Your table should display whether NMOS and PMOS transistors are ON or OFF for each of the states of inputs and write down the state of output F. One incorrect answer cancels one correct answer.



H: high Z: high impedance
L: low 1: ON 0: OFF

A	B	C	N1	P1	N2	P2	N3	P3	N4	P4	F
L	L	L	0	1	0	1	0	1	0	0	Z
L	L	H	0	1	1	0	0	1	0	0	Z
L	H	L	0	1	0	1	1	0	0	1	H
L	H	H	0	1	1	0	1	0	1	0	L
H	L	L	1	0	0	1	0	1	0	0	Z
H	L	H	1	0	1	0	0	1	0	0	Z
H	H	L	1	0	0	1	1	0	1	0	L
H	H	H	1	0	1	0	1	0	1	0	L

3. (35 pts) **Draw** the minimum the sum-of-product and minimum product-of-sum solutions for the digital circuit described by the VHDL code. In your drawing, you can use not-gates, and- and or-gates with any number of inputs.

entity q3 is

Port (x : in STD_LOGIC_VECTOR (3 downto 0);

s : out STD_LOGIC_VECTOR (1 downto 0));

end q3;

architecture q3_arch of q3 is

begin

with x select

s <= "11" when "0000",

"10" when "0001",

"11" when "0010",

"11" when "0011",

"01" when "0100",

"10" when "0101",

"10" when "0110",

"11" when "0111",

"11" when "1000",

"11" when "1001",

"--" when others; -- this is DON'T CARE

end q3_arch;

$x_3 \backslash x_2 x_1 x_0$	00	01	11	10
0	1	1	1	1
1	0	1	1	1
2	1	1	1	1
3	1	1	1	1

$x_3 \backslash x_2 x_1 x_0$	00	01	11	10
0	1	0	1	1
1	1	0	1	0
2	1	0	1	0
3	1	0	1	0


$$S_1 = (\bar{x}_2 + x_1 + x_0) \text{ SOP and } (\bar{x}_2 + x_1 + x_0) \text{ POS solutions are the same}$$

$$S_0 = x_3 + \bar{x}_1 \cdot \bar{x}_0 + x_1 \cdot x_0 + \bar{x}_2 \cdot \bar{x}_0$$

min SOP

$$S_0 = (x_3 + x_1 + \bar{x}_0) \cdot (\bar{x}_2 + \bar{x}_1 + x_0)$$

min POS

 

4. (25 pts) Design a circuit that performs the following operation using only full adders. No other gates or components are allowed.

Inputs: Three 4-bit numbers $A = a_3a_2a_1a_0$, $B = b_3b_2b_1b_0$, $C = c_3c_2c_1c_0$

Output: One 4-bit number $D = d_3d_2d_1d_0$

We want $D = A + (-1)^{V(C)} \times B$, where all numbers A, B, C, D are in two's complement representation, and $V(C)$ represents the decimal equivalent of C .

if $V(C)$ is odd $D = A - B$
 is even $D = A + B$

0	0000	even	4	0100	even
1	0001	odd	5	0101	odd
2	0010	even	6	0110	even
3	0011	odd	7	0111	odd
-1	1111	odd	-5	1011	odd
-2	1110	even	-6	1010	even
-3	1101	odd	-7	1001	odd
-4	1100	even	-8	1000	even

if C_0 is 1 $\Rightarrow C$ is odd
 C_0 is 0 $\Rightarrow C$ is even

