

4-5-2008

BILKENT UNIVERSITY

Department of Electrical and Electronics Engineering

EEE102 Introduction to Digital Circuit Design

Midterm Exam II SOLUTION

Surname: _____

Name: _____


ID-Number: _____

Signature: _____

Duration is 120 minutes. Solve all 5 questions. Show all your work.

Q1 (20 points)	
Q2 (20 points)	
Q3 (20 points)	
Q4 (20 points)	
Q5 (20 points)	
Total	

 Q1. A synchronous FSM, with one input X and one output Y, has 4 states A, B, C, and D and has the following State/Output diagram. Design and draw this FSM using D flip flops with active low Preset and Clear controls. What does this FSM do?



Solution:



State encoding

State	Q ₁	Q ₀
A	0	0
B	0	1
C	1	0
D	1	1

Next state and excitation table

Q ₁	Q ₀	X	Q ₁ *=D ₁	Q ₀ *=D ₀
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

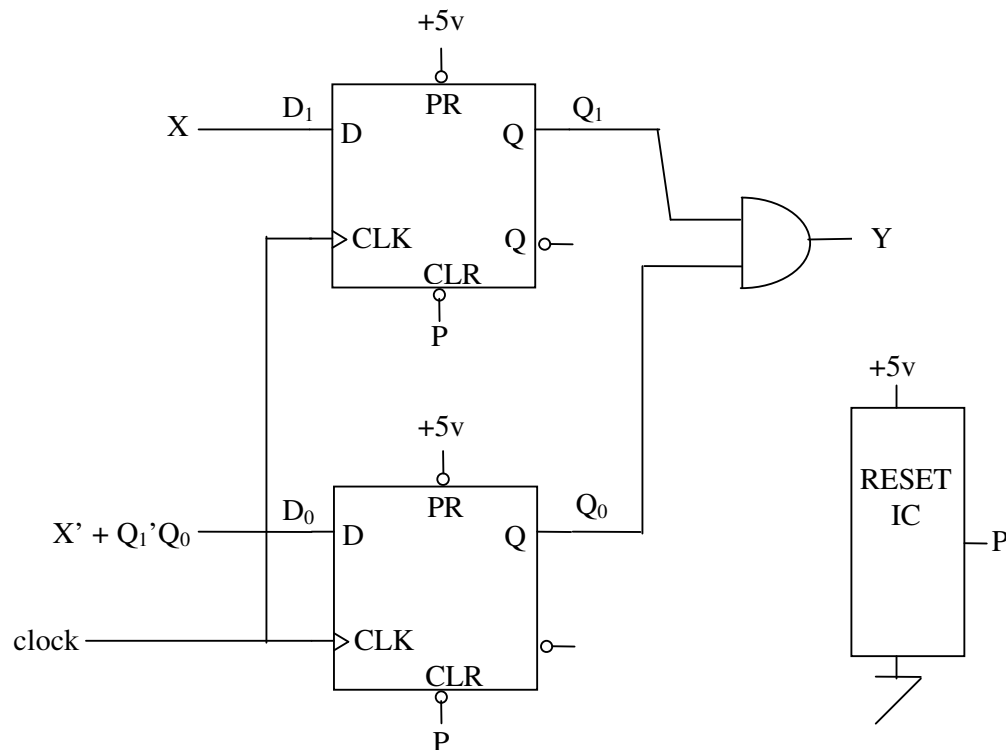 
Minimized functions for the next state logic



This FSM makes its output 1 when the last received X is 1 and the previously received X is 0. Thus it detects the “01” sequence in the input.

Alternative solution:

 It is observed that states A and C are equivalent. Therefore we can draw the State/Output diagram again.




Minimized functions: $D_1 = Q_0X$, $D_0 = X$, $Y = Q_1$

Q2. A circuit, shown below as a block, realizes the following functions:

 - (i) At the rising edge of the CLOCK signal
it loads A to X and B to Y if $S = 0$, and
it loads B to X and A to Y if $S = 1$.
- (ii) If the asynchronous CLR input is 1 then it makes $X = 0$ and $Y = 0$.

“Asynchronous” means “independent of CLOCK edges”. Write VHDL code to describe this circuit.



Solution:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity AdvancedDff is
  Port ( CLOCK : in std_logic;
        CLR : in std_logic;
        A : in std_logic;
        B : in std_logic;
```

```

    S : in std_logic;
    X : out std_logic;
    Y : out std_logic);
end AdvancedDff;

```

architecture Behavioral of AdvancedDff is

```

begin
process (CLOCK,CLR)
    begin
        if CLR='1' then X<='0';Y<='0';
        elsif CLOCK'event and CLOCK='1' then
            case S is
                when '0' => X<=A;Y<=B;
                when '1' => X<=B;Y<=A;
                when others => X<=A;Y<=B;
            end case;
        end if;
    end process;
end Behavioral;


```

Q3. a) Draw how you can obtain a D flip flop using a single JK flip flop and minimum number of additional simple gates.


b) Draw how you can obtain a JK flip flop using a single D flip flop and minimum number of additional simple gates.

Solution:

a)

 

b)

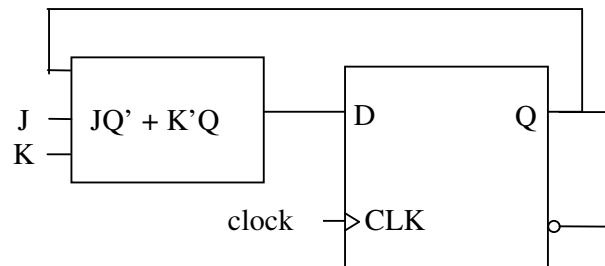

Q4. Implement $F = AB + C'$


- using a generic 8-to-1 multiplexer and minimum number of additional simple gates,
- using a generic 4-to-1 multiplexer and minimum number of additional simple gates,
- using a generic 2-to-1 multiplexer and minimum number of additional simple gates,

- d) using one 74XX138 decoder and minimum number of additional simple gates.
 (note that 74XX138 is a 3-to-8 binary decoder with active low outputs and with three enables, one active high and two active low),
 and
 e) using two 2-to-4 generic decoders and minimum number of additional simple gates.


Solution:

A	B	C	$AB+C'$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


- a) using a generic 8-to-1 multiplexer

 


- b) using a generic 4-to-1 multiplexer

 


- c) using a generic 2-to-1 multiplexer

 

d) using a 74XX138 decoder.

 


e) using two 2-to-4 generic decoders.

 

Q5. We need to design a comparator (called BIG) which has two 2-bit binary numbers as input, A and B, and two outputs EQ (meaning “equal”) and GT (meaning “greater”) such that the following table is implemented:

Condition	EQ	GT
A = B	1	0
A > B	0	1
A < B	0	0

 
We have already designed a simple comparator (called SMALL) which receives two 1-bit numbers, X and Y, and gives outputs E and G such that



Condition	E	G
X = Y	1	0
X > Y	0	1
X < Y	0	0

- (5 points) Use two SMALLs and minimum number of additional simple gates to design one BIG. Draw your circuit.
- (15 points) Assume now that the VHDL code for SMALL has already been written and included in the library. Write VHDL code for BIG using two SMALLs as components.

Solution:

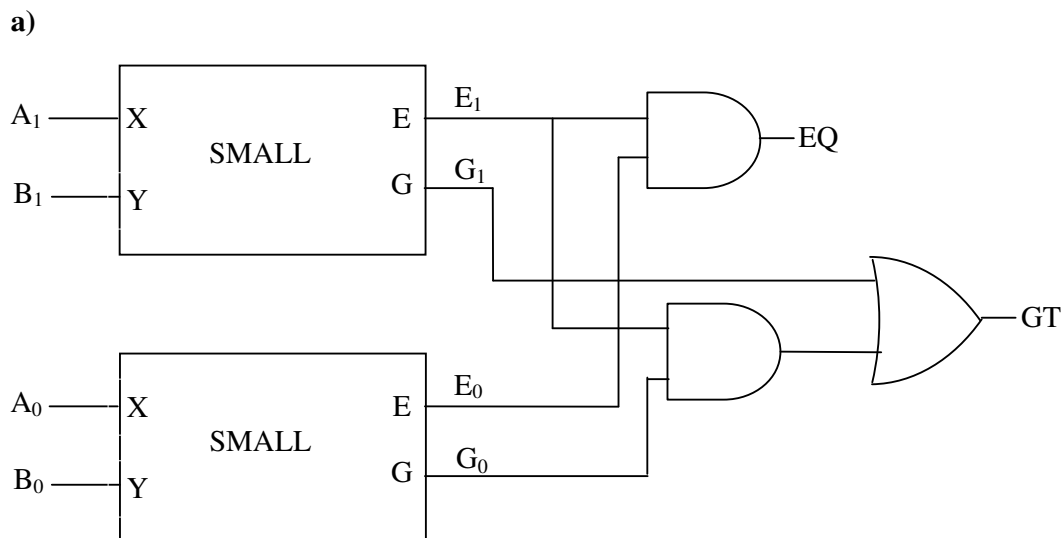

The logic behind this solution is as follows: EQ is 1 if and only if $A_1 = B_1$ and $A_0 = B_0$.

GT is 1 if $A_1 > B_1$ (in this case we do not have to compare A_0 and B_0),

or $A_1 = B_1$ and $A_0 > B_0$.


Thus $GT = G_1 + E_1 G_0$

More systematic solution:

A1	B1	A0	B0	E1	E0	G1	G0	GT
0	0	0	0	1	1	0	0	0
0	0	0	1	1	0	0	0	0
0	0	1	0	1	0	0	1	1
0	0	1	1	1	1	0	0	0
0	1	0	0	0	1	0	0	0
0	1	0	1	0	0	0	0	0

0	1	1	0		0	0	0	1		0
0	1	1	1		0	1	0	0		0
1	0	0	0		0	1	1	0		1
1	0	0	1		0	0	1	0		1
1	0	1	0		0	0	1	1		1
1	0	1	1		0	1	1	0		1
1	1	0	0		1	1	0	0		0
1	1	0	1		1	0	0	0		0
1	1	1	0		1	0	0	1		1
1	1	1	1		1	1	0	0		0

E1	E0	G1	G0	GT
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	d
0	1	1	0	1
0	1	1	1	d
1	0	0	0	0
1	0	0	1	1
1	0	1	0	d
1	0	1	1	1
1	1	0	0	0
1	1	0	1	d
1	1	1	0	d
1	1	1	1	d

 

b)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BIG is
    Port ( A : in std_logic_vector(1 downto 0);
          B : in std_logic_vector(1 downto 0);
          EQ : out std_logic;
          GT : out std_logic);
end BIG;
```

```
architecture Behavioral of BIG is
    component SMALL
    Port ( X : in std_logic;
          Y : in std_logic;
          E : out std_logic;
          G : out std_logic);
    end component;
    signal E1,E0,G1,G0:std_logic;
begin
    C1:SMALL port map(A(1),B(1),E1,G1);
    C2:SMALL port map(A(0),B(0),E0,G0);
    EQ <= E1 and E0;
    GT <= G1 or (E1 and G0);
end Behavioral;
```

You do not have to write the code for SMALL but I have included it below for your information:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity SMALL is
    Port ( X : in std_logic;
          Y : in std_logic;
          E : out std_logic;
          G : out std_logic);
end SMALL;
architecture Behavioral of SMALL is
begin
    process(X,Y)
    begin
        if X=Y then E<='1';G<='0';
        elsif X>Y then E<='0';G<='1';
        else E<='0';G<='0';
        end if;
    end process;
end Behavioral;
```