

BILKENT UNIVERSITY  
 Department of Electrical and Electronics Engineering  
 EEE102 Introduction to Digital Circuit Design  
 MidTerm Exam II  
 SOLUTION  
 2-5-2005


**Q1. (12 points)** Implement the function  $F = AB' + CD'$  using

- a) a generic 8-to-1 multiplexer using extra inverters only, if necessary.
  - b) a generic 4-to-1 multiplexer using extra inverters and one extra AND or OR gate only, if necessary.
  - c) two 2-to-4 generic decoders, using one extra OR gate, if necessary.
- In your solutions label all terminals and all internal and external signals.

**Solution:**


a)

There are other solutions

 


b)

There are other solutions

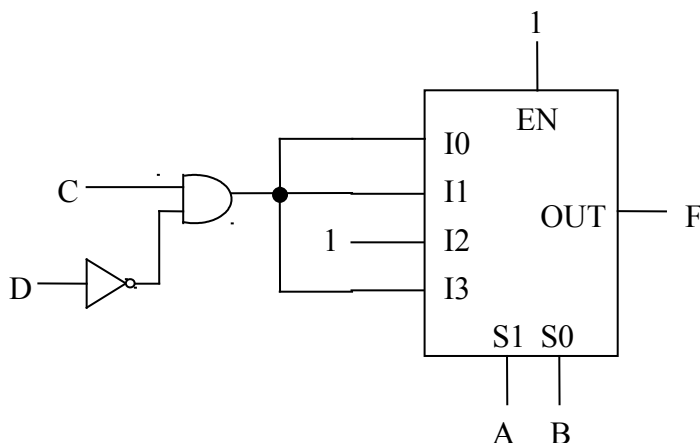


c)

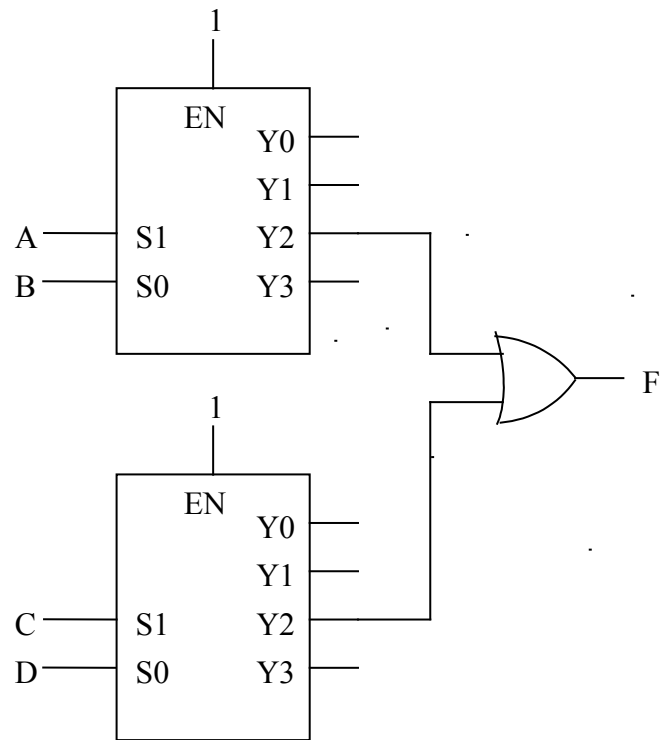


**Q2. (13 points)** Design and draw a 16-to-1 multiplexer using two 8-to-1 multiplexers and one 2-to-4 decoder. The 8-to-1 multiplexers and the 2-to-4 decoder are generic in the sense that they have one enable each and all of their signals are active high. The 16-to-1 multiplexer that you will design will also be generic with one enable and active high signals. You can use minimum number of additional simple gates.

**Solution:**

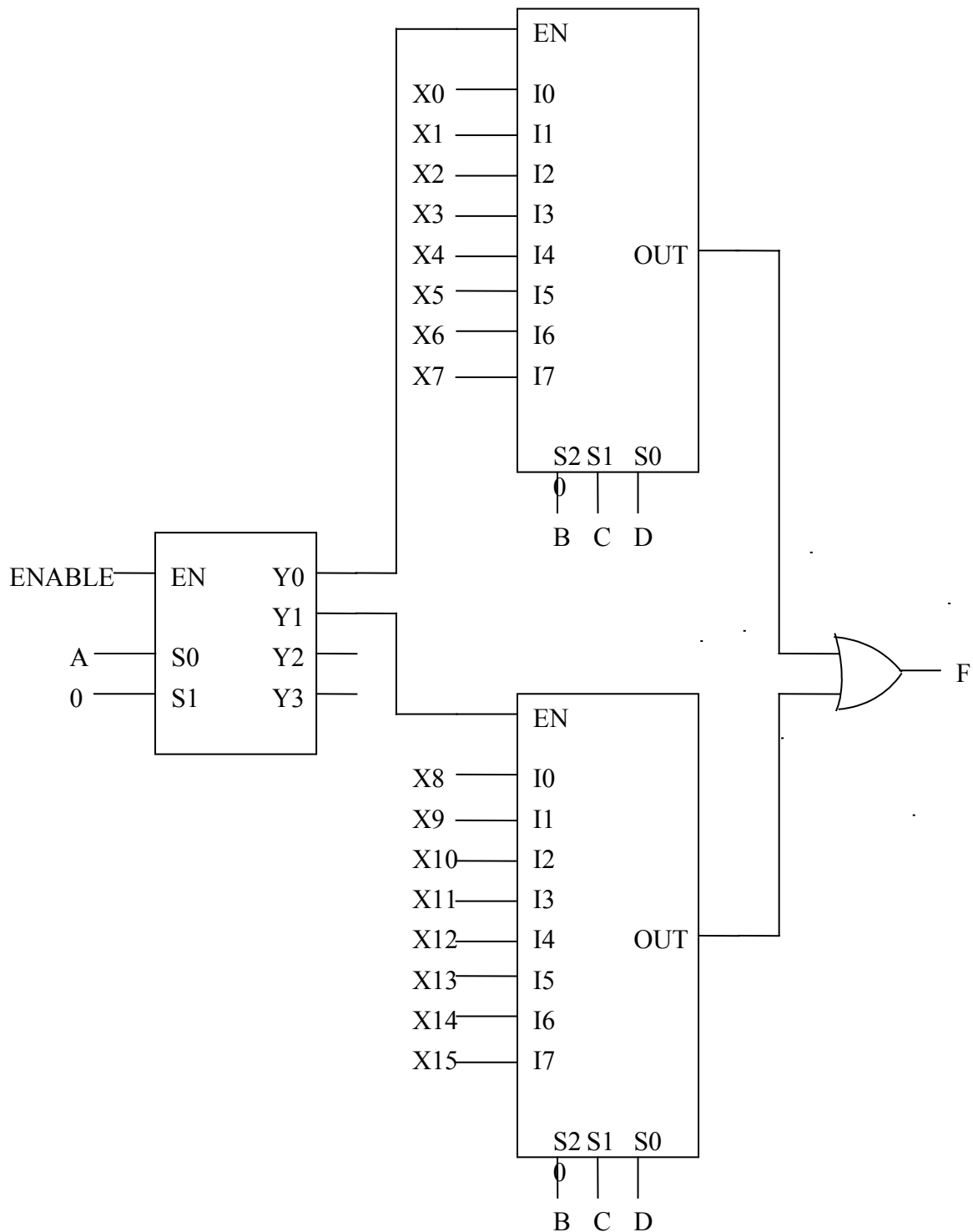


**Solution:**

 

$$G = AB + C'D \Rightarrow F = G + ABD'$$

**Q4. (15 points)** A synchronous clocked FSM has 3 states called A, B and C. The machine starts with state A at Power ON. This FSM has an input called HOLD. IF HOLD = '1' at a clock tick then the machine does not change state. If HOLD = '0' however, with the positive edge of the clock signal it goes to B if it is in A, goes to C if it is in B, and goes to B if it is in C. It has 2 outputs  $Y_1$  and  $Y_0$ .  $Y_1Y_0$  is "00" if the FSM is in state A, is "01" if in state B and is "10" if in state C. Design and draw this FSM using D ffs. Show all your design steps including state/output diagram, state encoding, next state table, output table, excitation table and minimization of the combinatorial circuits. Draw your circuit. Use RESET IC for initialization. (By proper labeling you need not draw long lines, but draw the gates.)

**Solution:**

 

3 states => 2 flip flops. Call their output Q1 and Q0.

**State Encoding**


	Q1	Q0
A	0	0
B	0	1
C	1	0

Next State Table. X is for HOLD


	Q1	Q0	X	Q1*	Q0*
A	0	0	0	0	1
A	0	0	1	0	0
B	0	1	0	1	0
B	0	1	1	0	1
C	1	0	0	0	0
C	1	0	1	1	0
	1	1	0	d	d
	1	1	1	d	d

Excitation table is the same with Q1\* replaced by D1 and Q0\* by D0.

### Minimized Next State Logic

 

$$D_1 = Q_0X' + Q_1X$$

 

$$D_0 = Q_1'Q_0'X' + Q_0X$$


### Output Table

	Q1	Q0		Y1	Y0
A	0	0		0	0
B	0	1		0	1
C	1	0		1	0
	1	1		d	d


Therefore

$$Y1 = Q1 \text{ and } Y0 = Q0$$

### Circuit including initialization

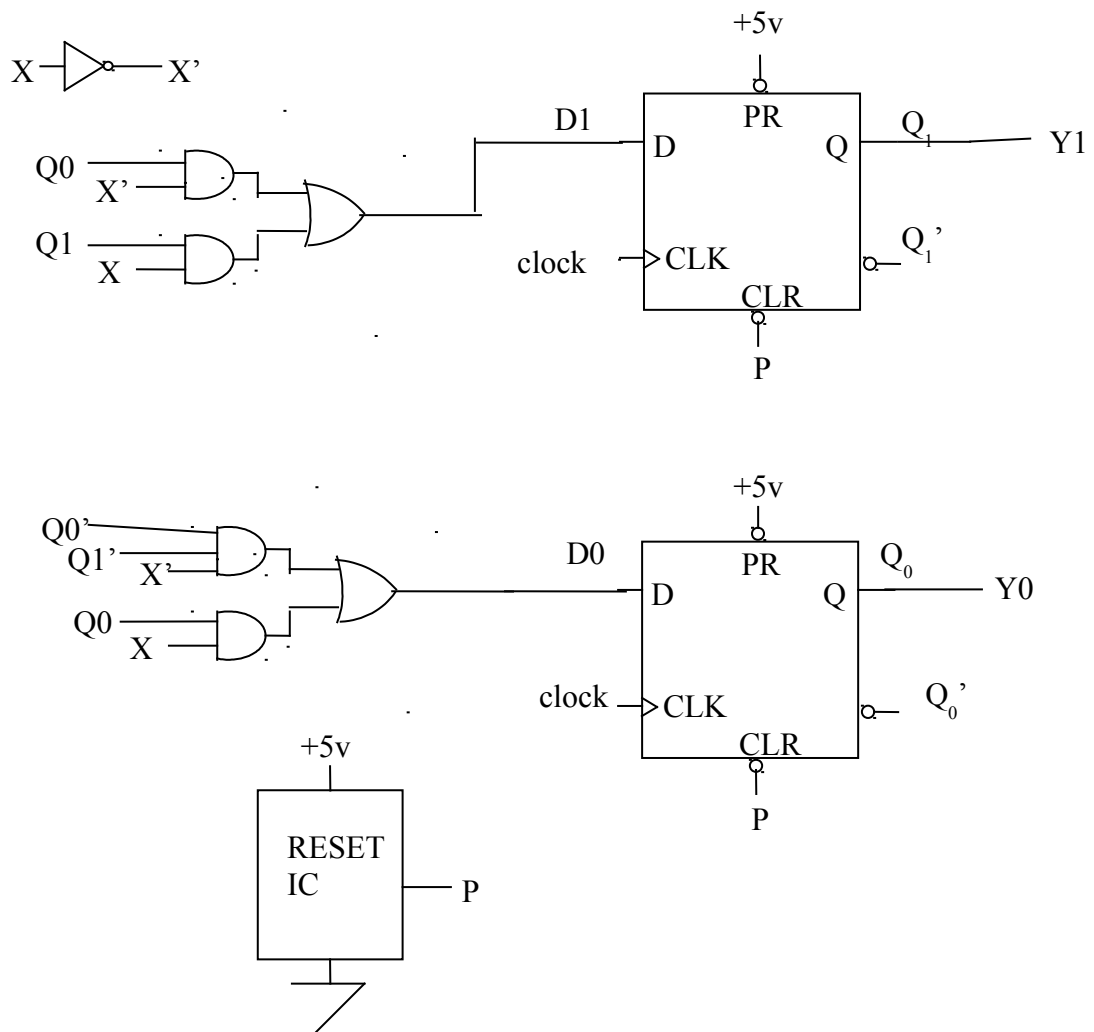

 **Q5. (15 points)** A Mealy FSM has the following state/output diagram. This FSM has two inputs X and Y, and a single output Z. On each arrow there are two expressions separated by a comma. The first expression is about the inputs and the second expression is about the output. These expressions are used to express the values of X, Y and Z in compact form. For example XY means  $X=1$  and  $Y=1$ . In other words these are the values of X and Y which make the expression XY TRUE, that is, 1. Similarly  $Z'$  means the output is 0 because if  $Z=0$  then the expression  $Z'$  is TRUE, that is 1.



Design and draw this FSM using JK ffs. Show all your design steps including state encoding, next state table, output table, excitation table and minimization of the combinatorial circuits. Draw your circuit. Use RESET IC for initialization. (By proper labeling you need not draw long lines, but draw the gates.)

**Solution:**

2 states . 1 ff. Call its output Q.

**State Encoding**



	Q
S0	0
S1	1



Next State and Excitation Table together.

	Q	X	Y	Q*	J	K
S0	0	0	0	0	0	d
S0	0	0	1	0	0	d
S0	0	1	0	0	0	d
S0	0	1	1	1	1	d
S1	1	0	0	0	d	1
S1	1	0	1	0	d	1
S1	1	1	0	0	d	1
S1	1	1	1	1	d	0

Minimized Next state Logic

  


Output Table

	Q	X	Y	Z
S0	0	0	0	0
S0	0	0	1	0
S0	0	1	0	0
S0	0	1	1	0
S1	1	0	0	0
S1	1	0	1	0
S1	1	1	0	0
S1	1	1	1	1

$Z = QXY$


Circuit with initialization:

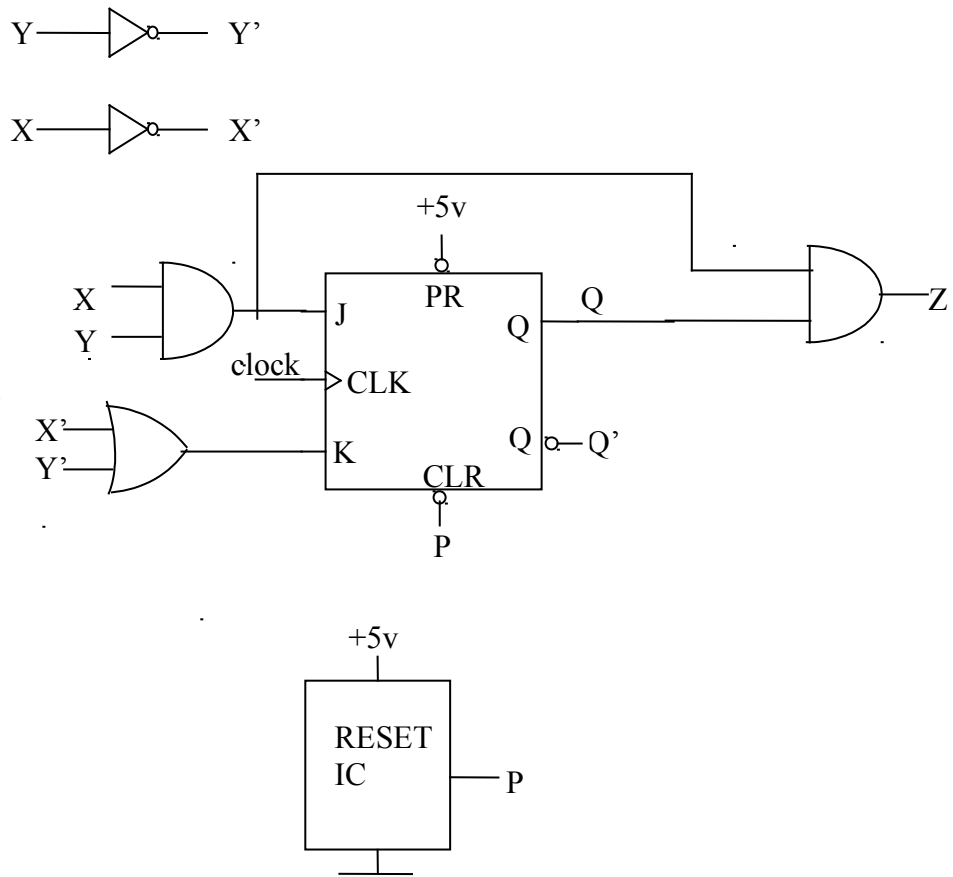

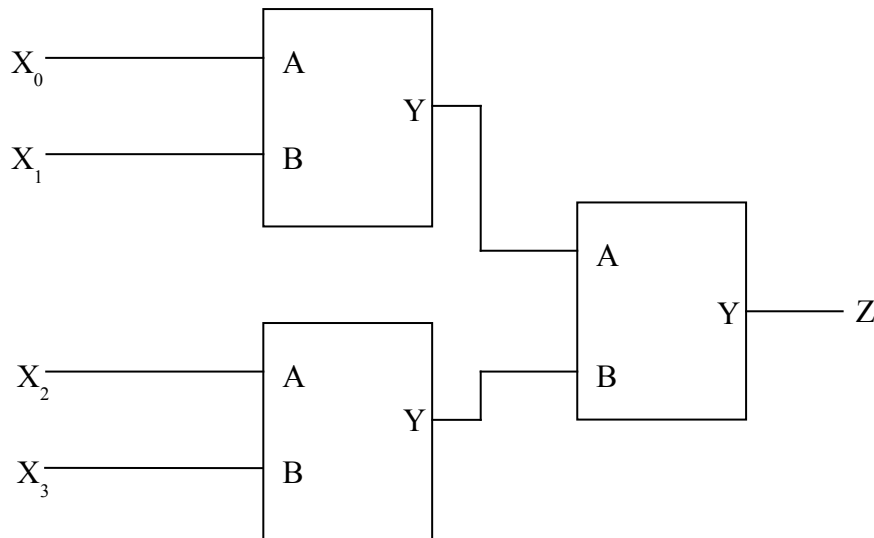**Q6. (15 points)** The VHDL code for an entity called BRICK is already written and included in the library. The entity definition for BRICK is as follows.

```
entity BRICK is
    port(A,B:in std_logic;
          Y:out std_logic );
end BRICK;
```

Write VHDL code for the circuit below. Some VHDL language templates are given in the Appendix.



**Solution:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity top is
    Port ( X : in std_logic_vector(3 downto 0);
          Z : out std_logic);
end top;
```

```
architecture Structural of top is
    component BRICK
        Port ( A,B: in std_logic;
              Y : out std_logic);
    end component;
    signal U,V:std_logic;
begin
    label1:BRICK port map(X(0),X(1),U);
    label2:BRICK port map(X(2),X(3),V);
    label3:BRICK port map(U,V,Z);
end Structural;
```

**Q7. (15 points)** Write VHDL code for a 2-to-4 decoder which has two enables, one active low and one active high, and active low outputs. Some VHDL language templates are given in the Appendix.

**Solution:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity dec2to4 is
    Port ( EN : in std_logic;
          EN_L : in std_logic;
          S : in std_logic_vector(1 downto 0);
          Y : out std_logic_vector(3 downto 0));
end dec2to4;

architecture Behavioral of dec2to4 is
    signal TEMP: std_logic_vector(3 downto 0);
begin
    with S select
        TEMP<="1110" when "00",
              "1101" when "01",
              "1011" when "10",
              "0111" when "11",
              "1111" when others;
        Y<=TEMP when EN='1' and EN_L='0' else "1111";

end Behavioral;
```

**Another solution:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity dec2to4_another is
    Port ( EN : in std_logic;
          EN_L : in std_logic;
          S : in std_logic_vector(1 downto 0);
          Y : out std_logic_vector(3 downto 0));
end dec2to4_another;

architecture Behavioral of dec2to4_another is
begin
    process(EN,EN_L,S)
    begin
        if EN='1' and EN_L = '0' then
            case S is
                when "00" => Y<="1110";
                when "01" => Y<="1101";
```

```

        when "10" => Y<="1011";
        when "11" => Y<="0111";
        when others => Y<="1111";
    end case;
    else Y<= "1111";
    end if;
end process;
end Behavioral;

```

**Yet another solution:**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity dec2to4_yet_another is
    Port ( EN : in std_logic;
          EN_L : in std_logic;
          S : in std_logic_vector(1 downto 0);
          Y : out std_logic_vector(3 downto 0));
end dec2to4_yet_another;

architecture Behavioral of dec2to4_yet_another is
begin
    process(EN,EN_L,S)
    begin
        if EN='1' and EN_L = '0' then
            if S="00" then Y<="1110";
            elsif S="01" then Y<="1101";
            elsif S="10" then Y<="1011";
            elsif S="11" then Y<="0111";
            else Y<="1111";
            end if;
        else Y<="1111";
        end if;
    end process;
end Behavioral;

```

## Appendix: Some VHDL language templates are given below:

### COMPONENT DECLARATION

```
component component_name
  port ( signal_names : mode signal type;
         signal_names : mode signal type;
         ...
         signal_names : mode signal type);
end component;
```

---

### COMPONENT INSTANTIATION

```
label: component_name port map (signal1, signal2, ..., signaln);
      or
label: component_name port map (port1 => signal1, port2 => signal2, ..., portn => signaln);
```

---

### for-generate LOOP

```
label: for identifier in range generate
      concurrent-statement
end generate;
```

---

### ENTITY DECLARATION

```
entity entity_name is
  generic ( constant_names : constant type;
            constant_names : constant type;
            ...
            constant_names : constant type);
  port ( signal_names : mode signal_type;
         signal_names : mode signal_type;
         ...
         signal_names : mode signal_type);
end entity_name;
```

---

### CONCURRENT SIGNAL-ASSIGNMENT STATEMENT

```
signal_name <= expression;
      or
signal_name <= expression when boolean-expression else
               expression when boolean-expression else
               ...
               expression when boolean-expression else
               expression;
```

---

### with-select STATEMENT

```
with expression select
  signal_name <= signal_value when choices,
                 signal_value when choices,
                 ...
                 signal_value when choices;
```

---

### process STATEMENT

```
process(signal_name, signal_name, ..., signal_name)
  type_declarations
  variable_declarations
  constant_declarations
begin
  sequential-statement
  ...
  sequential-statement
end process;
```

---

**if STATEMENTS**

if *boolean\_expression* then *sequential\_statement*  
end if;

if *boolean\_expression* then *sequential\_statement*  
else *sequential\_statement*  
end if;

if *boolean\_expression* then *sequential\_statement*  
elsif *boolean\_expression* then *sequential\_statement*  
...  
elsif *boolean\_expression* then *sequential\_statement*  
else *sequential\_statement*  
end if;

---

**case-when STATEMENT**

case *expression* is  
    when *choices* => *sequential\_statements*  
    ...  
    when *choices* => *sequential\_statements*  
end case;

---

**loop STATEMENT**

loop  
    *sequential\_statement*  
    ...  
    *sequential\_statement*  
end loop;

---

**for-loop STATEMENT**

for *identifier* in range loop  
    *sequential\_statement*  
    ...  
    *sequential\_statement*  
end loop;

---

**while STATEMENT**

while *boolean\_expression* loop  
    *sequential\_statement*  
    ...  
    *sequential\_statement*  
end loop;

---