

## Bilkent University, EEE 102 Final Exam, Spring 2020


### Question 1 [20 pts] – Time: 30 minutes

Implement the Boolean function


$$F(A, B, C, D, E) = \bar{A} D (\bar{B} \bar{C} \bar{E} + B \bar{C} E) + CE$$

using ONLY one 2-to-4 decoder with ENABLE and one 4-to-1 multiplexer. Logic levels 0 and 1 are available (i.e., you can use them as inputs). Complements of the variables are NOT available.

2-to-4  
Decoder with Enable

 

4-to-1  
Multiplexer

 

**Question 2 [30 pts] – Time: 40 minutes**

Design a Moore machine that has a single input X and a single output Y that works as follows.

- Machine is always in one of the two modes: **free** and **blocked**.
- If machine is **free** and  $X=0$ , then in the next three CLKs, it will emit sequence 101 as output. It will be **blocked** until the entire sequence is emitted.
- If machine is **free** and  $X=1$ , then in the next three CLKs, it will emit sequence 010 as output. It will be **blocked** until the entire sequence is emitted.
- Inputs that arrive when the machine is **blocked** do not affect the output.

An example input-output sequence is given below:

Time →

X	0	1	1	1	0	1	1	0	1	0
Y	d	1	0	1	0	1	0	0	1	0


(i) Draw the state diagram with minimum number of states.  
**[15 pts]**

(ii) What is the minimum number of flip-flops needed to implement this circuit? Will there be any unused flip-flop states? If so, how many? **[5 pts]**

(iii) **[This part is not related to (i) and (ii)]** Implement the state table given below using minimal number of JK flip-flops. X is the input, Y is the output. Find minimal sum-of-products forms for flip-flop input equations and output equation. Note: d represent don't care. **[10 pts]**


Present State Q <sub>1</sub> Q <sub>0</sub>	Next State		Output Y
	X=0 Q <sub>1</sub> +Q <sub>0</sub> +	X=1 Q <sub>1</sub> +Q <sub>0</sub> +	
00	10	0d	1
01	01	dd	0
11	dd	dd	1
10	d0	d1	0

Question 3 [30 pts] – Time: 40 minutes

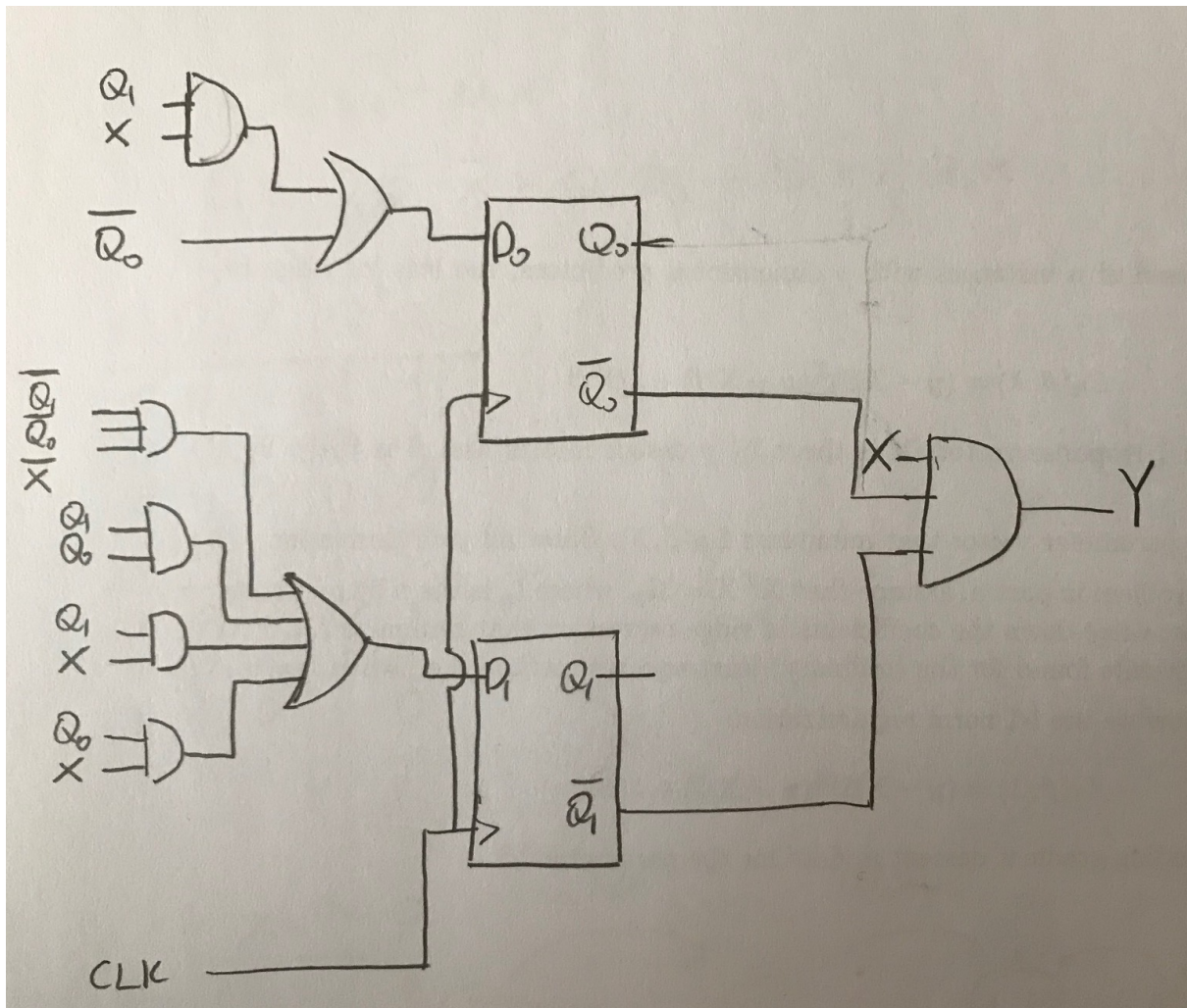

(i) Consider the sequential circuit above made up of 2 type D flip-flops with input  $X$  and output  $Y$ . Draw the state diagram for this circuit. [15 pts]

 
(ii) Complete the timing diagram for this Mealy FSM, given below starting from initial state 11. Is this FSM working as expected? Identify if there is a problem with the output and propose a way to solve this problem. [15 pts]




**Question 4 [20 pts] – Time: 30 minutes**

You have access to the following components:

(1) 2-to-4 decoders with enable input:

 

 (2) 16 nibble ROMs with 4-bit address  $a = a_3a_2a_1a_0$ , chip select 'CS' and output enable 'OE' inputs:



**Using ONLY these components, design a 64 nibble ROM that also has chip select 'CS' and output enable 'OE' inputs. Draw its diagram, showing all connections.**